

$$\textcircled{1} \quad T = 300 \text{ K}, \quad V_A = 100 \text{ V}, \quad V_{GS} - V_{TH} = 500 \text{ mV}, \quad \lambda = 0.1 \text{ V}^{-1}, \quad C_L = 10 \text{ pF} \quad \& \quad I_C = I_O = 1 \text{ mA}$$

$$\textcircled{a} \quad a_V = ? \quad \frac{g_m}{I_C} = ? \quad \frac{g_m}{I_0} = ?$$

Bipolar

$$g_m = \frac{I_C}{V_T} = \frac{1 \text{ mA}}{25.87 \text{ mV}} = \frac{2}{207} \text{ A/V}$$

$$r_o = \frac{V_A}{I_C} = \frac{100}{1 \text{ mA}} = 100 \text{ k}\Omega$$

$$\text{DC Voltage gain} = -g_m r_o \\ = -\underline{\underline{3864.7343 \text{ V/V}}}$$

$$\frac{g_m}{I_C} = \underline{\underline{38.647}}$$

MOS


$$g_m = \frac{2I_0}{V_{GS} - V_T} = \frac{2 \text{ mA}}{500 \text{ mV}} = \frac{1}{250} \text{ A/V}$$

$$r_o = \frac{1}{\lambda I_0} = \frac{1}{0.1 \times 1 \text{ mA}} = 10 \text{ k}\Omega$$

$$\text{DC Voltage gain} = -g_m r_o \\ = -\underline{\underline{40 \text{ V/V}}}$$

$$\frac{g_m}{I_0} = \underline{\underline{4}}$$
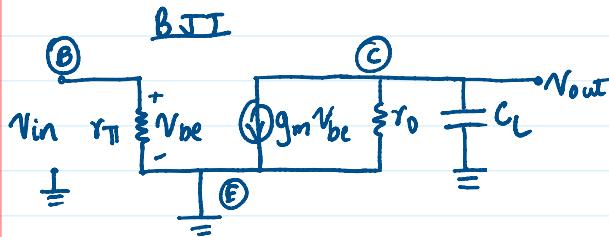
$$\textcircled{b} \quad a_V = \frac{V_{out}}{V_{in}} = ?$$




$$V_{be} = V_{in} \quad \textcircled{1}$$

$$g_m V_{be} + \frac{V_{out}}{r_o} + V_{out} (sC_L)$$

$$V_{out} \left(\frac{1}{r_o} + sC_L \right) = -g_m V_{in}$$
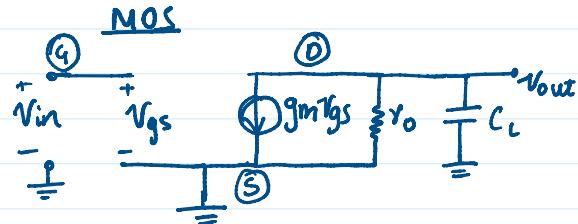
$$a_V = \frac{V_{out}}{V_{in}} = -\frac{g_m r_o}{1 + s r_o C_L} \quad \textcircled{2}$$



$$V_{gs} = V_{in} \quad \textcircled{3}$$

$$g_m V_{gs} + \frac{V_{out}}{r_o} + V_{out} (sC_L)$$

$$V_{out} \left(\frac{1}{r_o} + sC_L \right) = -g_m V_{in}$$

$$a_V = \frac{V_{out}}{V_{in}} = -\frac{g_m r_o}{1 + s r_o C_L} \quad \textcircled{4}$$

$$|V_{out}| = |V_{in}| \quad @ f = f_T$$

$$|g_m r_o| = |1 + s r_o C_L|$$

$$(g_m r_o)^2 = 1^2 + r_o^2 C_L^2 (2\pi)^2 f_T^2$$

$$(3864.7343)^2 = 1 + (10^5 \times 10 \times 10^{12})^2 (2\pi)^2 f_T^2$$

$$f_T = 615.09155 \text{ MHz}$$

$$|V_{out}| = |V_{in}|$$

$$|g_m r_o| = |1 + s r_o C_L|$$

$$(g_m r_o)^2 = 1^2 + r_o^2 C_L^2 (2\pi)^2 f_T^2$$

$$(10)^2 = 1^2 + (10^4 \times 10 \times 10^{12})^2 (2\pi)^2 f_T^2$$



$$f_T = 63.64208 \text{ MHz}$$

BJT response



MOSFET response



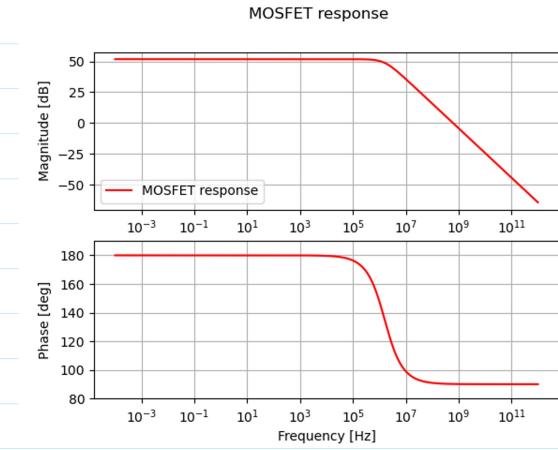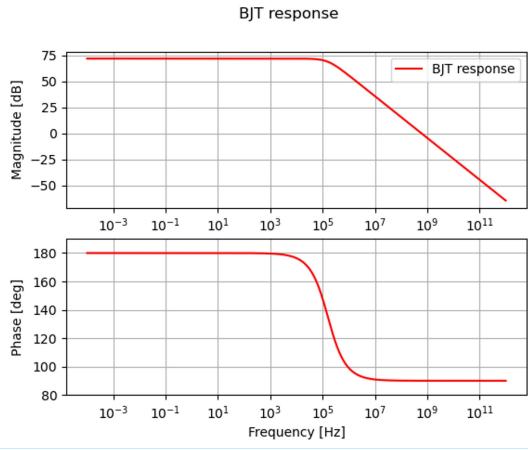

$$I_{D0} = I_S e^{V_{GS}/nV_T} \quad \& \quad n=1.5$$

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{1}{nV_T} I_S e^{V_{GS}/nV_T}$$

$$g_m = \frac{I_D}{nV_T} \quad \text{--- ①}$$

$$\frac{g_m}{I_{D0}} = \frac{1}{nV_T} = \frac{1}{1.5 \times 25.875m} = \underline{25.765}$$

In Subthreshold region, we observe that the transistor provides better g_m & gain

a) $N=8$
 $I_{C1} = I_{C2} = 50\mu A \quad T = 300K$



$$\begin{aligned} \Delta V_{BE} &= V_{BE1} - V_{BE2} \\ &= V_T \ln \frac{I_C1}{I_S} - V_T \ln \frac{I_C2}{N I_S} \end{aligned}$$

$$\begin{aligned} \Delta V_{BE} &= V_T \ln \left(\frac{I_C1 \cdot N}{I_C2} \right) \Rightarrow \Delta V_{BE} = V_T \ln N \\ &= 25.86m \cdot \ln 8 \\ &= 53.774mV \end{aligned}$$

$$R_1 = \frac{\Delta V_{BE}}{I_{C2}} = \frac{53.774mV}{50\mu A}$$

$$R_1 = 1075.48 \Omega$$

b) Slope=? & M=?

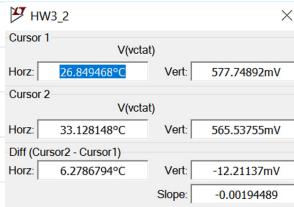
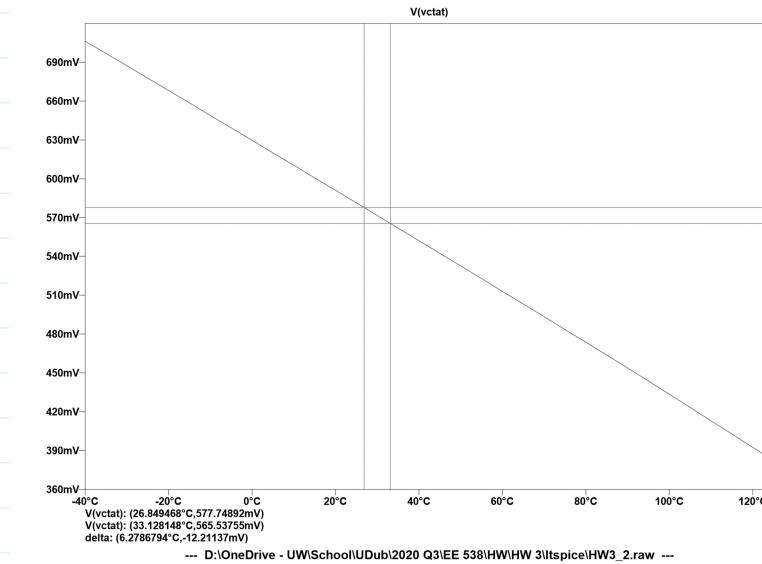


$$\text{Slope} = -1.944 \text{ mV/}^{\circ}\text{C}$$

$$R_2 = \frac{V_{CC} - V_{CE}}{I_C} = \frac{5 - 1}{50\mu} = 80 \text{ k}\Omega$$

$$\frac{dV_{BE1}}{dt} = -M \frac{d}{dt} \Delta V_{BE}$$

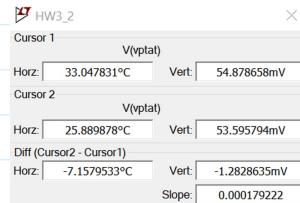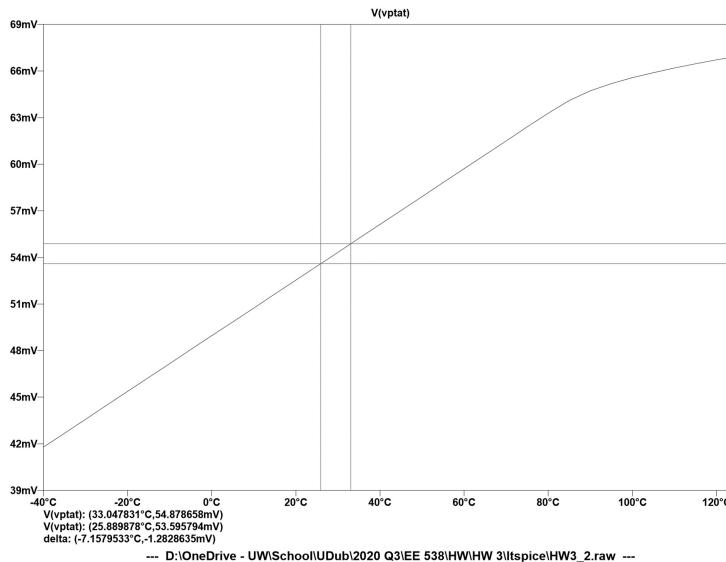To operate in Forward active region
 $V_{CE} \geq V_{BE}$
 $V_{CE} \geq 0.523 \text{ V}$
 Say $V_{CE} = 1 \text{ V}$



$$\text{Slope} = 0.17922 \text{ mV/}^{\circ}\text{C}$$


$$M = \frac{1.94489}{0.17922}$$

$$\Rightarrow M = 10.85$$

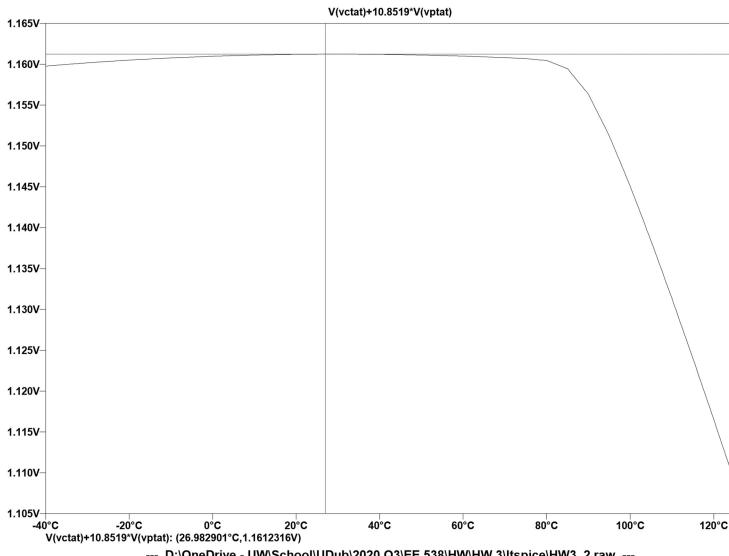(c) 1. Value of BG at room temperature


$$\begin{aligned} V_{BG} &= V_{CTAT} + V_{PTAT} \\ &= V_{BE} + M \Delta V_{BE} \\ &= 1.94489 + 10.85 \times 0.00194489 \dots \end{aligned}$$

$$\begin{aligned}
 V_{BG} &= V_{CTAT} + V_{PTAT} \\
 &= V_{BE} + M \Delta V_{BE} \\
 &= [577.45802 + 10.85 (53.7948)] \text{ mV} \\
 V_{BG} &= \underline{\underline{1.1611 \text{ V}}} \text{ at } 27^\circ\text{C}
 \end{aligned}$$



HW3_2	
Cursor 1	$V(vctat) + 10.8519 \cdot V(vptat)$
Horz	26.982901°C
Vert	1.1612316V
Cursor 2	
Horz	-- N/A --
Diff (Cursor2 - Cursor1)	
Horz	-- N/A --
Vert	-- N/A --
Slope	-- N/A --

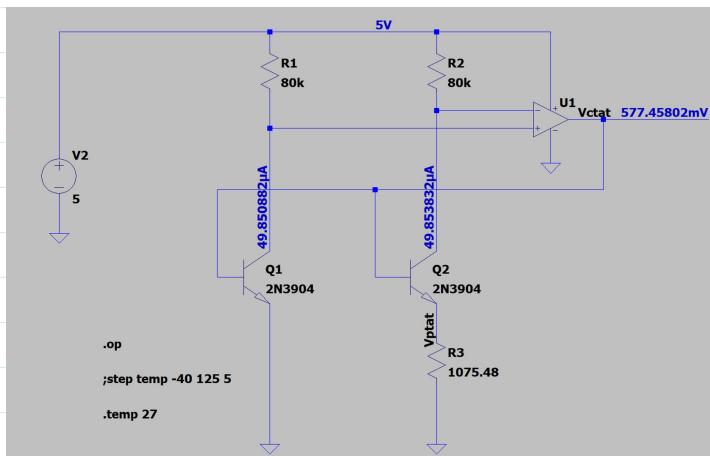2. Maximum deviation occurs at $T = 125^\circ\text{C}$
% error = $\frac{1.1611 - 1.1089}{1.1611} = 4.49\%$ deviation



Bonus:

Need to add a resistor R_4 . $V_{R4} = I_L R_4 = (2I_C) R_4$


$$V_{BG} = V_{R4} + V_{BE1}$$

$$V_{BG} = R_4 \left(2 \frac{\Delta V_{BE}}{R_1} \right) + V_{BE1}$$

$$V_{BG} = R_4 \left(2 \frac{\Delta V_{BE}}{R_1} \right) + V_{BEI}$$

$$1.1611 = R_4 \left[\frac{2 \times 53.49m}{1075.48} \right] + 577.458m$$

$$R_4 = 5.834 \text{ k}\Omega$$

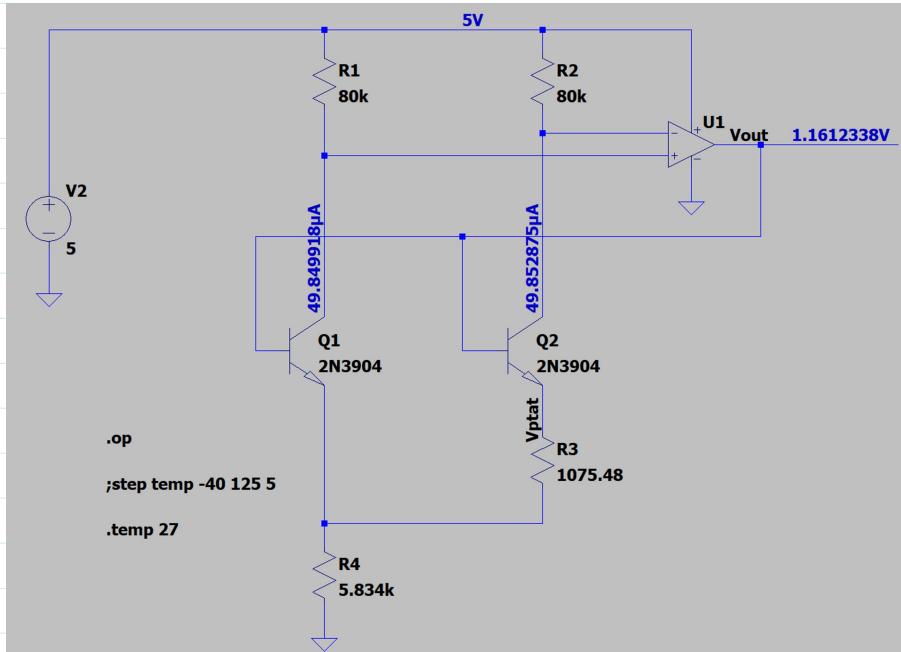

③

$$V_{out} = V_{DD} - K(V_{in} - V_{th})^2 R_o$$

$$a) \quad V_{in} = a_{in} \sin(2\pi f_o t) + V_{OC}$$

$$V_{OC} - V_{th} = 500 \text{ mV}$$

$$V_{out} = V_{DD} - K [a_{in} \sin(2\pi f_o t) + V_{OC} - V_{th}]^2 R_o$$

$$V_{out} = V_{DD} - K [a_{in}^2 \sin^2(2\pi f_o t) + 0.25 + a_{in} \sin(2\pi f_o t)] R_o$$

$$V_{out} = V_{DD} - K \left[\frac{a_{in}^2}{2} (1 - \cos(4\pi f_o t)) + 0.25 + a_{in} \sin(2\pi f_o t) \right] R_o$$

$$V_{out} = V_{DD} - \frac{K a_{in}^2}{2} R_o - 0.25 K R_o - K a_{in} \sin 2\pi f_o t R_o + \frac{K a_{in}^2}{2} \cos 4\pi f_o t R_o$$

$$a_1 = -K a_{in} R_o$$

$$a_2 = \frac{K a_{in}^2 R_o}{2}$$

(b) $a_{in} = 1mV$, $a_{in} = 10mV$

$$\frac{a_2}{a_1} = \frac{1}{2} a_{in}$$

$$\boxed{\frac{a_2}{a_1} = 0.5m}$$

$$, \quad \frac{a_2}{a_i} = \frac{1}{2} a_{in}$$

$$, \quad \boxed{\frac{a_2}{a_i} = 5m}$$