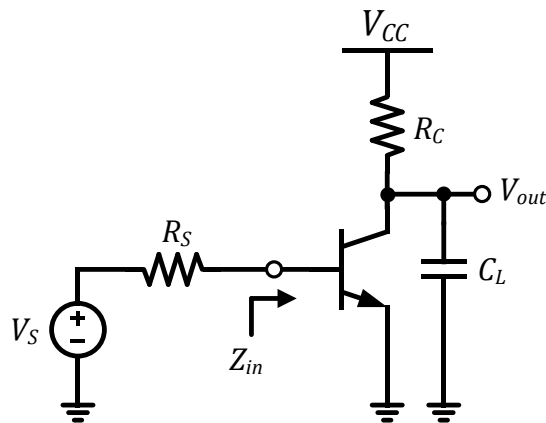


EE 538 Spring 2020
Analog Circuits for Sensor Systems
University of Washington Electrical & Computer Engineering

Instructor: Jason Silver
Midterm


Please show your work.

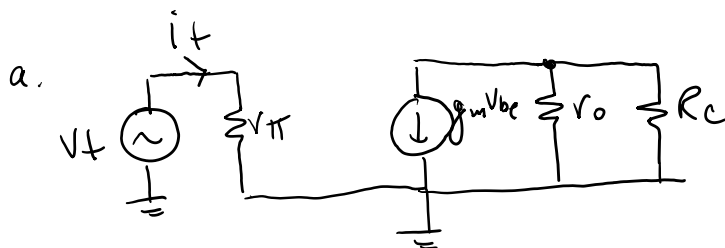Problem 1: Common-emitter amplifier



For the following, $V_{CC} = 5V$, $V_S = 1V$, $R_S = 1k\Omega$, $I_{bias} = 100\mu A$, $R_C = 10k\Omega$, $C_L = 10pF$, $\beta = 100$, $V_A = 100V$, $V_T = 25mV$, and $I_S = 10^{-16}A$.

- (10 points) Calculate the input impedance of the amplifier, Z_{in} . *Note: This does not include R_S .*
- (10 points) Find an expression for the transfer function, V_{out}/V_S . Be sure to account for attenuation due to Z_{in} .
- (10 points) Calculate the DC gain and transit frequency f_T .



DC small-signal
model

$$Z_{in} = \frac{V_t}{i_t} = r_{\pi} = \frac{\beta}{g_m}$$

$$g_m = \frac{100\mu A}{25mV} = 4mS$$

$$Z_{in} = \frac{100}{4mS} = 25k\Omega$$

$$\begin{aligned}
 \text{b. } \frac{V_{in}}{V_s} &= \frac{Z_{in}}{R_s + Z_{in}} ; \quad \frac{V_{out}}{V_{in}} = -g_m (R_c \parallel r_o \parallel \frac{1}{sC_L}) \\
 &= \frac{-g_m R_c \parallel r_o \cdot \frac{1}{sC_L}}{R_c \parallel r_o + \frac{1}{sC_L}} \\
 &= \frac{-g_m R_c \parallel r_o}{sC_L R_c \parallel r_o + 1}
 \end{aligned}$$

$$\boxed{\frac{V_o}{V_s} = \frac{Z_{in}}{Z_{in} + R_s} \cdot \frac{-g_m R_c \parallel r_o}{sC_L R_c \parallel r_o + 1}}$$


$$\begin{aligned}
 \text{c. } \frac{V_o}{V_s}(s=0) &= \frac{Z_{in}}{Z_{in} + R_s} \cdot (-g_m R_c \parallel r_o) & Z_{in} &= 25k\Omega \\
 &\approx \frac{Z_{in}}{Z_{in} + R_s} (-g_m R_c) & r_o &= \frac{V_A}{I_C} = 1M\Omega \\
 &= \boxed{-38.5 \text{ V/V}} & R_c &= 10k\Omega
 \end{aligned}$$

$$f_T \approx \frac{Z_{in}}{Z_{in} + R_s} (g_m \cdot R_c) \cdot \frac{1}{2\pi R_c \cdot C_L}$$

$$= \frac{25}{26} \cdot (40) \cdot \frac{1}{2\pi \cdot 10k\Omega \cdot 10pF}$$

$$\approx \boxed{61.2 \text{ MHz}}$$

Problem 2: Opamp nonidealities

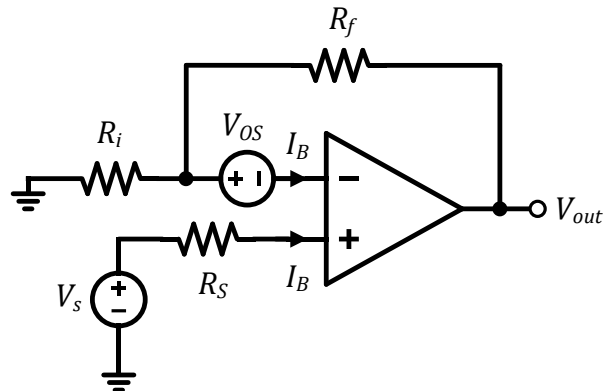

Assume the opamp has infinite gain and bandwidth. $V_{OS} = 1\text{mV}$, and $I_B = -1\text{nA}$. $R_f = 10R_i$.

- (15 points) Determine an expression for the output offset voltage, including the contributions from both V_{OS} and I_B .
- (10 points) Assuming $R_S = 0$, calculate values for R_i and R_f that result in zero output offset.
- (10 points) Assuming $R_S = 1\text{k}$ and $V_{OS} = 0$, calculate values for R_i and R_f that result in zero output offset.

a. V_{OS} :

$$V_{out, V_{OS}} = \left(1 + \frac{R_f}{R_i}\right) V_{OS}$$

I_B^+ :

$$V^+ = 0V - I_B \cdot R_S$$

$$V_{out, I_B^+} = -I_B R_S \left(1 + \frac{R_f}{R_i}\right)$$

I_B^- :

$$V_{out, I_B^-} = 0V + I_B \cdot R_f$$

$$V_{out, OS} = \left(1 + \frac{R_f}{R_i}\right) V_{OS} + I_B \left[R_f - R_S \left(1 + \frac{R_f}{R_i}\right) \right]$$

$$b. R_s = 0$$

$$V_{out,os} = \left(1 + \frac{R_f}{R_i}\right) V_{os} + I_B \cdot R_f = 0$$

$$= 11 \cdot V_{os} - 1 \mu A \cdot R_f = 0$$

$$11 V_{os} = 1 \mu A \cdot R_f$$

$$R_f = \frac{11 \cdot 1 \mu V}{1 \mu A} = \boxed{11 k\Omega}$$

$$R_i = \frac{R_f}{10} = \boxed{1.1 k\Omega}$$

$$c. V_{out,os} = I_B \left[R_f - R_s \left(1 + \frac{R_f}{R_i}\right) \right] = 0$$

$$R_f = R_s \left(1 + \frac{R_f}{R_i}\right)$$

$$R_s = \frac{R_f \cdot R_i}{R_f + R_i} = \frac{10 R_i^2}{11 R_i} = \frac{10}{11} R_i$$

$$\boxed{\begin{array}{l} R_i = 1.1 k\Omega \\ R_f = 11 k\Omega \end{array}}$$

Problem 3. Opamp AC and transient analysis

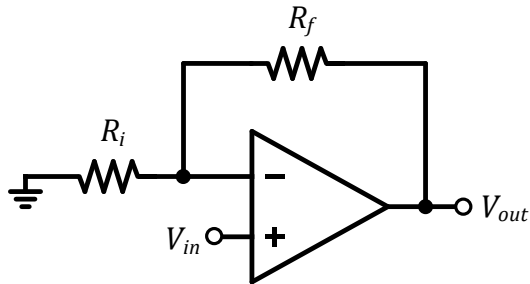


Figure 3a. Non-inverting amplifier

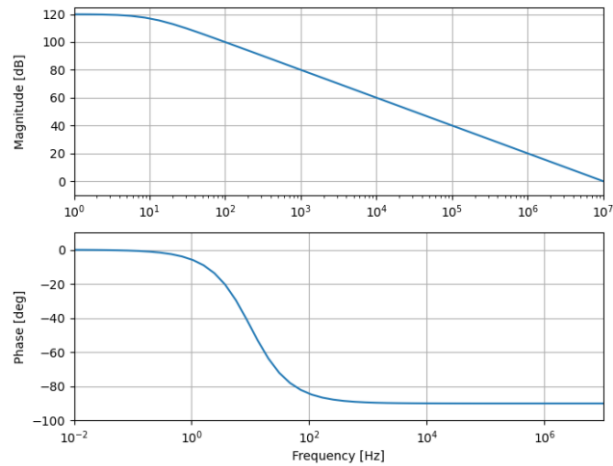


Figure 3b. Opamp open-loop frequency response

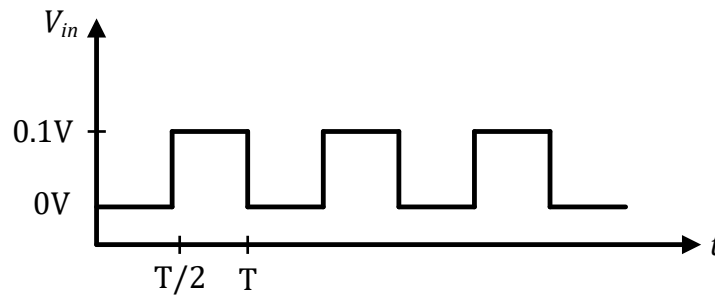


Figure 3. Input waveform for c) and d)


Assume ideal input/output resistances (R_{in} and R_o) for the opamp. Let $R_f = 10R_{in}$.

- (10 points) Determine the DC gain and the 3dB frequency of the closed loop transfer function (V_{out}/V_{in}).
- (7.5 points) Provide an expression for the transient response of the amplifier for a voltage step input of 0 to 100mV. Sketch the response and label all relevant times/voltages.
- (10 points) Assume the amplifier is driven by the input waveform shown in Fig 3c. Determine the minimum period T for which 0.1% settling is achieved during each half-period (integer multiples of $T/2$). Sketch the output waveform.
- (7.5 points) Calculate the total worst-case error in the output voltage (at the end of each half-period) if the resistors have a tolerance of 0.1%.

$$a. \quad \beta = \frac{R_i}{R_f + R_i} = \frac{1}{11} \quad ; \quad f_{3dB,CL} = \beta \cdot f_T = \beta \cdot 10MHz = \boxed{909kHz}$$


$$A_{CL} = \frac{A_{OL}}{1 + \beta A_{OL}} \approx \boxed{10.9999 V/V}$$
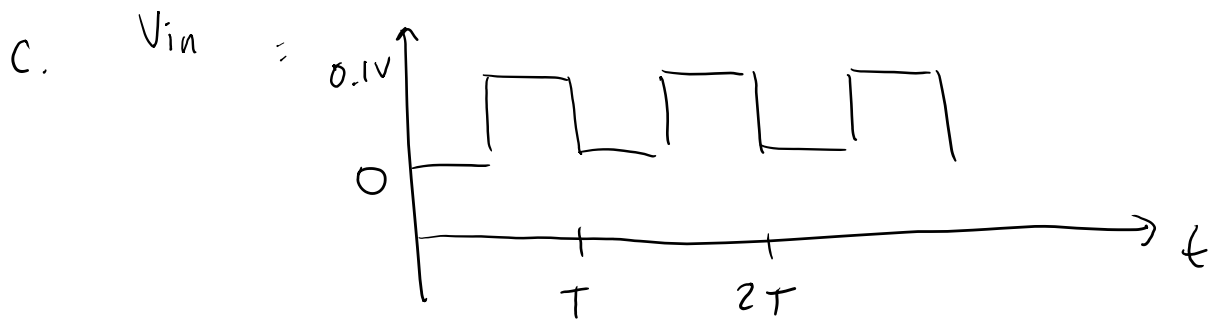
$$b. \quad V_{out} = 0.1V \cdot (1 - e^{-t/\tau}), \quad \text{where } \tau = \frac{1}{2\pi f_{3dB}}$$



$$T/2 = -\ln(0.001) \cdot \tau \approx 1.21 \mu s$$

$$\boxed{T = 2.4 \mu s}$$

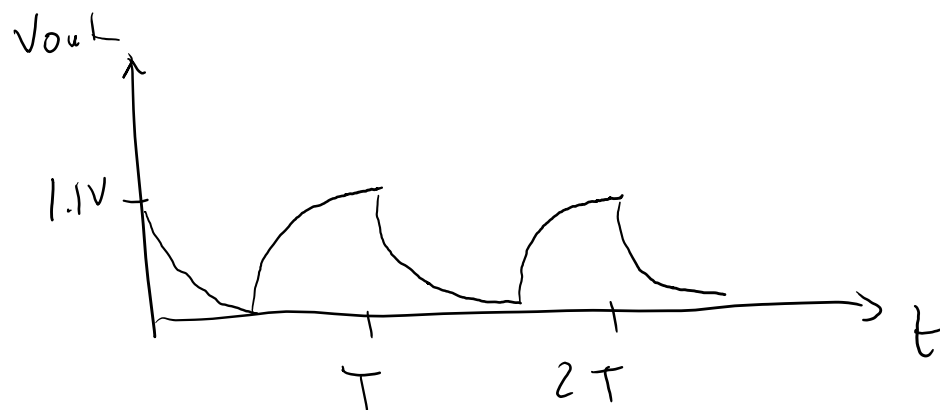

d. Worst-case error for $R_f(1 - 0.001)$
and $R_i(1 + 0.001)$

$$A'_{CL} = 1 + \frac{10(1 - 0.001)}{1 + 0.001} \approx 10.98 \text{ V/V}$$

$$\text{@ } t = T/2, V_{out}(T/2) = 10.98 \cdot \left(1 - e^{-\frac{T/2}{\tau}}\right) \cdot 0.1 \text{ V}$$

$$\approx 1.097 \text{ V}$$

$$E_{error} = \frac{1.1 - 1.097}{1.1} \times 100\% = \boxed{0.27\%}$$