

Last time: Laplace transform for circuit analysis.

1. Find the Laplace transforms of an important functions and build a table for future reference.

ALMOST DONE


2. Develop technique to go from s -domain back to time-domain.

**EXAMPLES WERE
CONSIDERED**

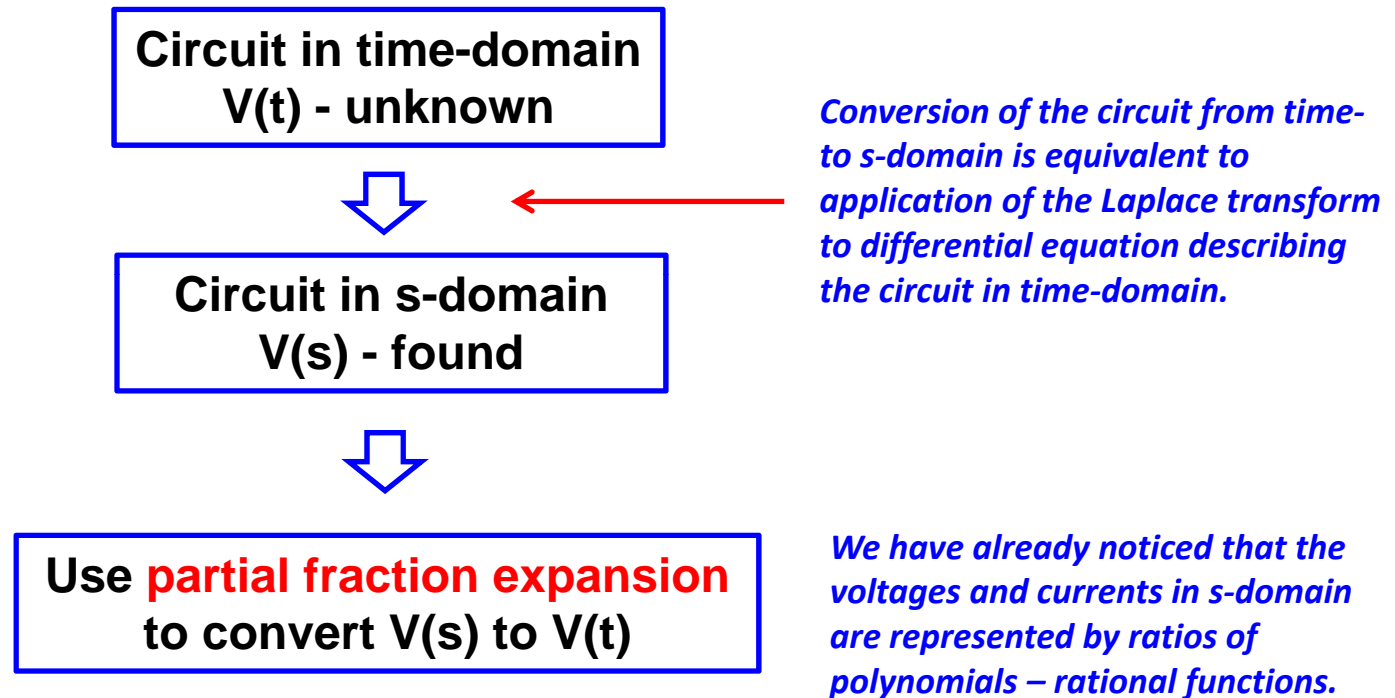3. Develop circuit analysis techniques in s -domain.

STILL WORKING

Let's discuss again how to get back to time domain



Partial fraction expansion of proper rational functions.

$$\tilde{V}(s) = \text{Const.} \cdot \frac{s^m + a_{m-1} \cdot s^{m-1} + \dots + a_1 \cdot s + a_0}{s^n + b_{n-1} \cdot s^{n-1} + \dots + b_1 \cdot s + b_0} \quad ; m < n$$

1. Find the roots of the denominator (poles) and represent $V(s)$ as:

$$\tilde{V}(s) = \text{Const.} \cdot \frac{s^m + a_{m-1} \cdot s^{m-1} + \dots + a_1 \cdot s + a_0}{(s-p_1)^{k_1} \dots (s-p_\ell)^{k_\ell}} \quad ; n = \sum_{i=1}^{\ell} k_i$$

2. Find the coefficients in the partial fraction expansion for each pole:

$$\tilde{V}(s) = \frac{A_{k_1}}{(s-p_1)^{k_1}} + \frac{A_{k_1-1}}{(s-p_1)^{k_1-1}} + \dots + \frac{A_1}{s-p_1} + \dots$$

$$A_{k_1} = \tilde{V}(s)(s-p_1)^{k_1} \Big|_{s=p_1}$$

$$A_{k_1-1} = ? \quad A_{k_1-1} = \frac{d}{ds} (\tilde{V}(s) \cdot (s-p_1)^{k_1}) \Big|_{s=p_1}, \text{ etc.}$$

3. Find the time-domain function corresponding to each term in partial fraction expansion:

$$\mathcal{L}[e^{-\alpha t} \cdot h(t)] = \frac{1}{s+\alpha} \quad \text{and} \quad \mathcal{L}\left[\frac{t^{n-1}}{(n-1)!} e^{-\alpha t}\right] = \frac{1}{(s+\alpha)^n}$$

Complex roots always come in conjugate pairs.

$$p_2 = p_1^* \quad ; \quad p_1 = \alpha + j\beta$$

$$\tilde{V}(s) = \frac{1}{(s-p_1)(s-p_2)} = \frac{A}{s-p_1} + \frac{B}{s-p_2}$$

$$A = \tilde{V}(s)(s-p_1) - B \cdot \frac{s-p_1}{s-p_2} = \frac{1}{s-p_2} - B \cdot \frac{s-p_1}{s-p_2} = \frac{1}{p_1-p_2}$$

$$\text{or} \quad \left. \begin{aligned} A &= \tilde{V}(s)(s-p_1) \Big|_{s=p_1} = \frac{1}{p_1-p_2} \\ B &= \tilde{V}(s)(s-p_2) \Big|_{s=p_2} = \frac{1}{p_2-p_1} = A^* \end{aligned} \right\} B = A^*$$


$$V(t) = A e^{p_1 t} + A^* e^{p_2 t} = A e^{\alpha t} e^{j\beta t} + A^* e^{\alpha t} e^{-j\beta t}$$

$$A = |A| e^{j\varphi} \quad ; \quad A^* = |A| e^{-j\varphi}$$

$$V(t) = |A| e^{\alpha t} \left[e^{j(\omega t + \varphi)} + e^{-j(\omega t + \varphi)} \right] = 2|A| e^{\alpha t} \cos(\omega t + \varphi)$$

Resistor in s-domain.


time-domain

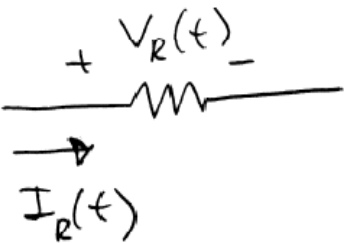

$$I_R(t) = \frac{V_R(t)}{R}$$

$$\mathcal{L} [I_R(t)] = \mathcal{L} \left[\frac{V_R(t)}{R} \right] = \frac{\mathcal{L} [V_R(t)]}{R}$$

s-domain

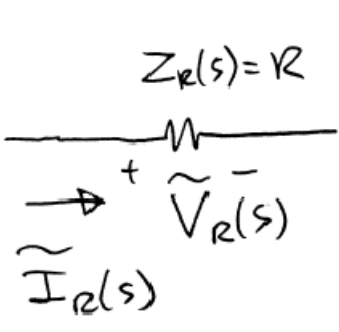


$$\tilde{I}_R(s) = \frac{\tilde{V}_R(s)}{R} = \frac{\tilde{V}_R(s)}{Z_R(s)}$$

$$Z_R(s) = R \quad - \text{ Impedance in s-domain}$$

Capacitor in s-domain.


time-domain

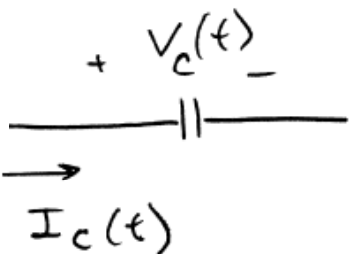

$$I_c(t) = C \frac{dV_c}{dt}$$

$$\mathcal{L}[I_c(t)] = C \mathcal{L}\left[\frac{d}{dt} V_c\right] = C \cdot (s \cdot \mathcal{L}[V_c(t)] - V_c(0-))$$
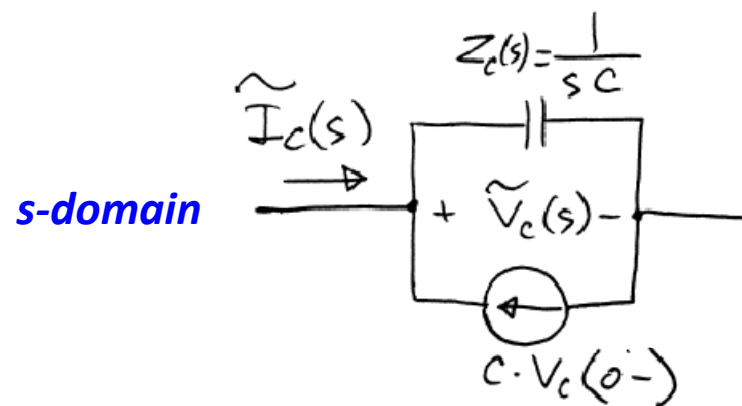
$$\tilde{I}_c(s) = (C \cdot s) \cdot \tilde{V}_c(s) - \underbrace{C \cdot V_c(0-)}_{\text{Initial condition}}$$




$$\tilde{I}_c(s) = \frac{\tilde{V}_c(s)}{Z_c(s)} - C \cdot V_c(0-)$$

$$Z_c(s) = \frac{1}{s \cdot C} - \text{Impedance in s-domain}$$

Inductor in s-domain.

time-domain

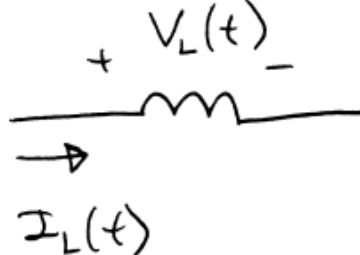


$$V_L(t) = L \cdot \frac{dI_L}{dt}$$

$$\mathcal{L}[V_L(t)] = \mathcal{L}\left[L \cdot \frac{dI_L}{dt}\right] = L \cdot \mathcal{L}\left[\frac{d}{dt} I_L(t)\right]$$

$$\tilde{V}_L(s) = L \cdot (s \cdot \tilde{I}_L(s) - I_L(0^-)) = (s \cdot L) \cdot \tilde{I}_L(s) - \underbrace{L \cdot I_L(0^-)}_{\text{Initial condition}}$$


s-domain

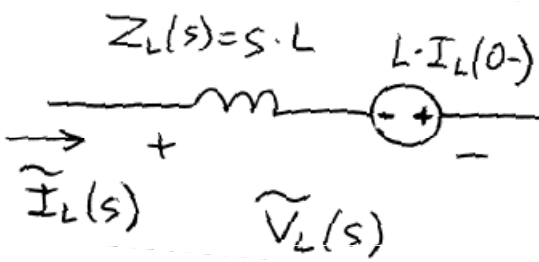

$$\tilde{V}_L(s) = Z_L(s) \cdot \tilde{I}_L(s) - L \cdot I_L(0^-)$$

$$Z_L(s) = s \cdot L - \text{Impedance in s-domain}$$


Example.

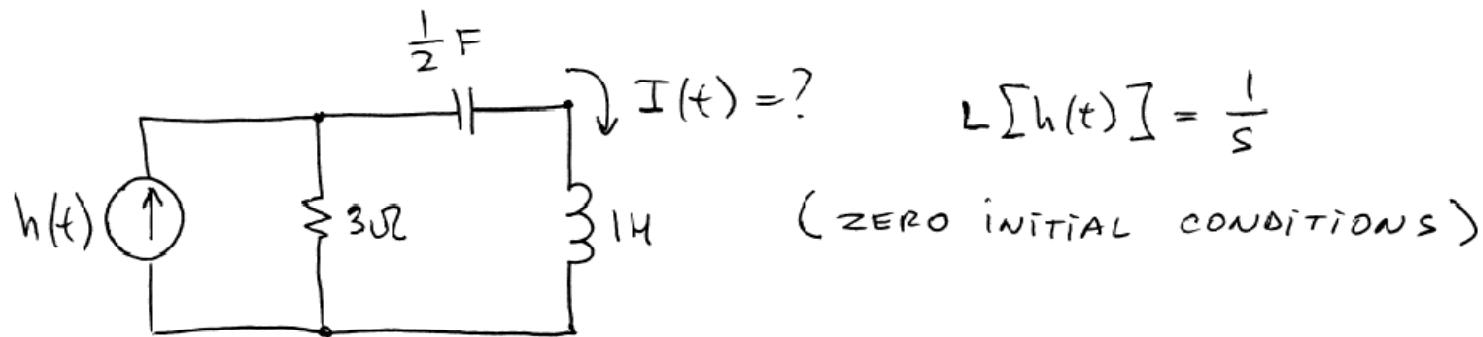

$$\mathcal{L}[h(t)] = \frac{1}{s}$$

(ZERO INITIAL CONDITIONS)

\downarrow to s-DOMAIN

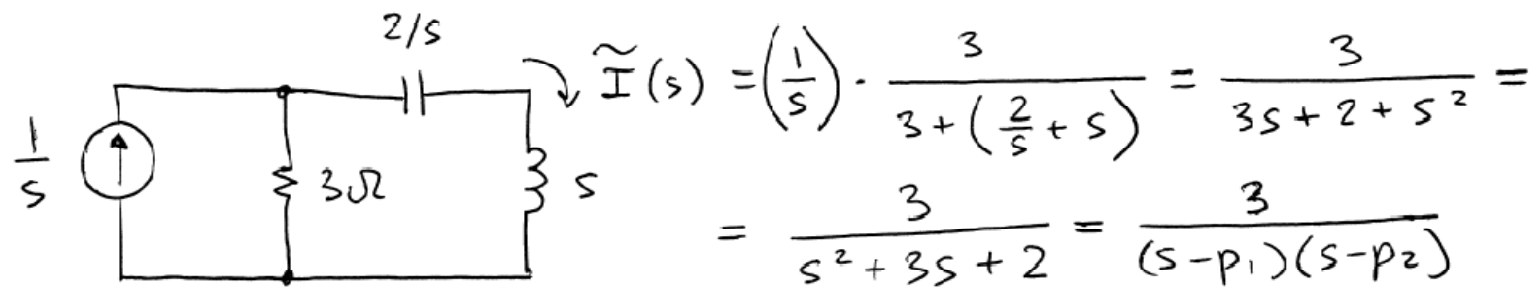

$$p_{1,2} = -\frac{3}{2} \pm \sqrt{\frac{9}{4} - 2} = -\frac{3}{2} \pm \sqrt{\frac{1}{4}} = -\frac{3}{2} \pm \frac{1}{2} = \{-1; -2\}$$

$$\tilde{I}(s) = 3 \left(\frac{A}{s+1} + \frac{B}{s+2} \right) = 3 \frac{As + 2A + Bs + B}{(s+1)(s+2)} \Rightarrow \begin{aligned} A &= -B \\ A &= 1 \end{aligned}$$

$$\tilde{I}(s) = 3 \left(\frac{1}{s+1} - \frac{1}{s+2} \right)$$

Example - cont.

$$\widetilde{I}(s) = 3 \left(\frac{1}{s+1} - \frac{1}{s+2} \right) \quad ; \quad \mathcal{L}[e^{-\alpha t}] = \frac{1}{s+\alpha}$$



$$I(t) = 3(e^{-t} - e^{-2t}), \text{ A}$$

$$\begin{aligned} V_c(t) &= \frac{1}{C} \int_0^t I(\tau) d\tau = 2 \cdot 3 \cdot \left(\int_0^t e^{-\tau} d\tau - \int_0^t e^{-2\tau} d\tau \right) = \\ &= 6 \cdot \left(e^{-\tau} \Big|_t^0 - \frac{1}{2} e^{-2\tau} \Big|_t^0 \right) = 6 \cdot \left(1 - e^{-t} - \frac{1}{2} (1 - e^{-2t}) \right) = \\ &= 6 \left(\frac{1}{2} - e^{-t} + \frac{1}{2} e^{-2t} \right) = 3 + 3 \cdot e^{-2t} - 6 \cdot e^{-t}, \text{ V} \end{aligned}$$

Example - cont.


$$\begin{aligned}
 \tilde{V}_c(s) &= \tilde{I}(s) \cdot Z_c(s) = \frac{3}{(s+1)(s+2)} \cdot \frac{2}{s} = \frac{6}{s(s+1)(s+2)} = \\
 &= 6 \left(\frac{A}{s} + \frac{B}{s+1} + \frac{C}{s+2} \right) \rightarrow \begin{cases} A = \frac{\tilde{V}_c(s)}{6} \cdot s \Big|_{s=0} = \frac{1}{2} \\ B = \frac{\tilde{V}_c(s)}{6} (s+1) \Big|_{s=-1} = -1 \\ C = \frac{\tilde{V}_c(s)}{6} (s+2) \Big|_{s=-2} = +\frac{1}{2} \end{cases} \\
 V_c(t) &= 6 \left(A + B e^{-t} + C e^{-2t} \right) \\
 V_c(t) &= 3 - 6 \cdot e^{-t} + 3 \cdot e^{-2t}, \text{ V}
 \end{aligned}$$

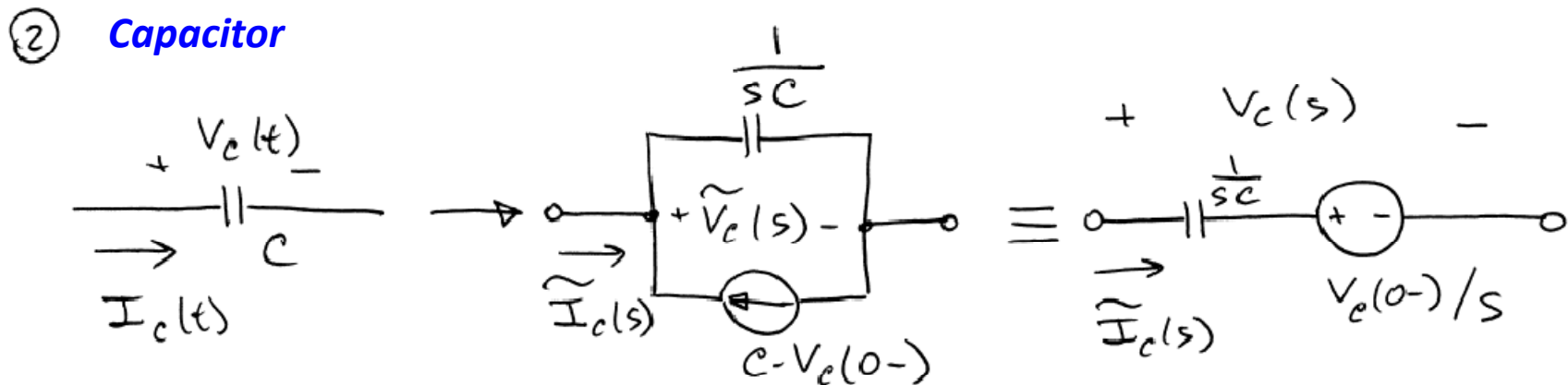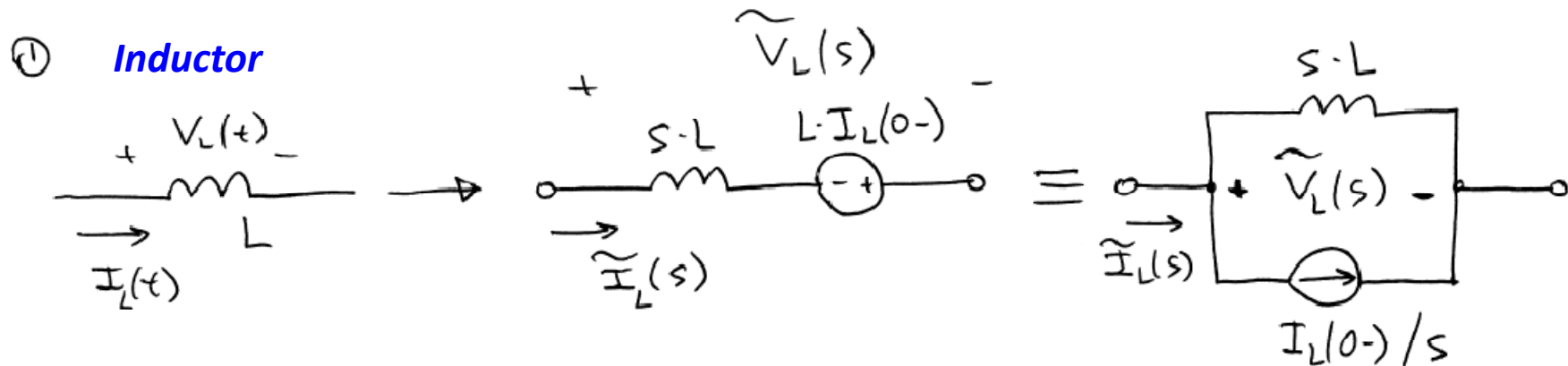Thevenin and Norton forms for inductor and capacitor.



Initial conditions are treated like independent sources in s-domain circuits



Example 1.

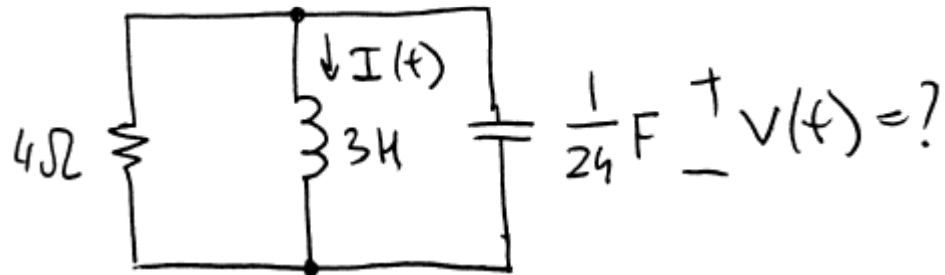

$$I(0^-) = 1 \text{ A}$$

$$V(0^-) = 4 \text{ V}$$

1. Construct s-domain circuit.

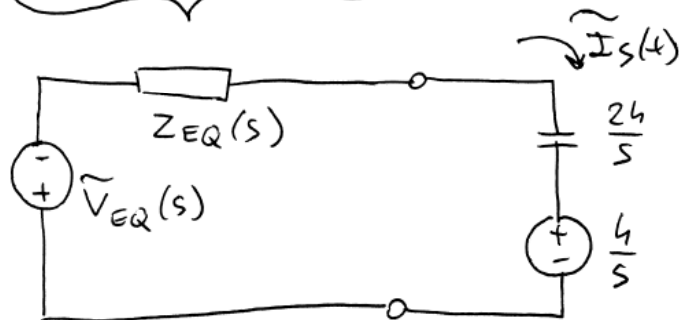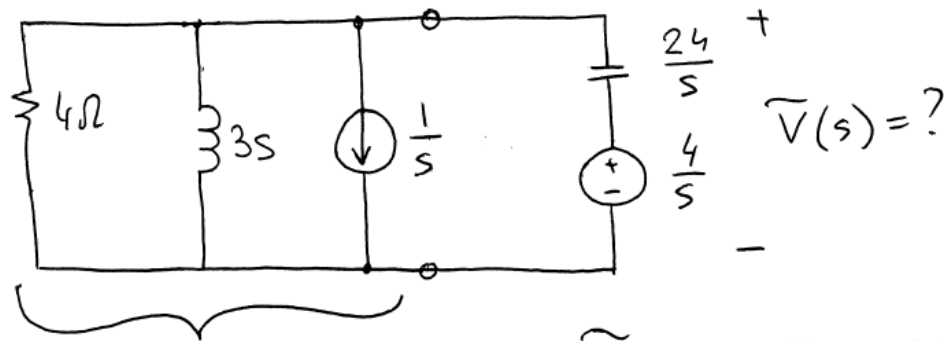


$$Z_{EQ}(s) = \frac{4 \cdot 3s}{4 + 3s} = \frac{12s}{3s + 4}$$

$$\tilde{V}_{EQ}(s) = \frac{1}{s} \cdot \frac{12s}{3s + 4} = \frac{12}{3s + 4}$$

Example 1 - cont.

2. Solve problem in s-domain.

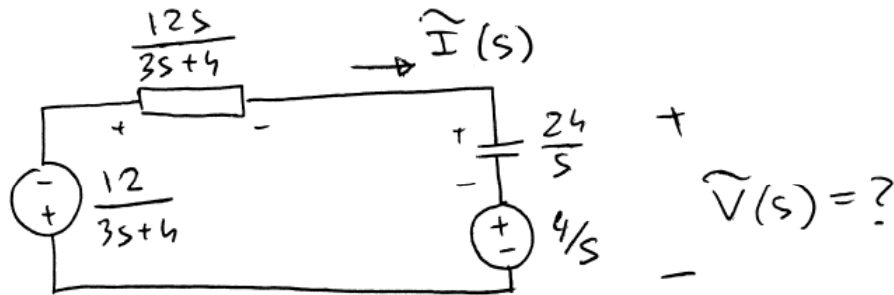

$$\tilde{I}(s) \cdot \frac{12s}{3s+4} + \tilde{I}(s) \cdot \frac{24}{s} + \frac{4}{s} + \frac{12}{3s+4} = 0 \quad \leftarrow \text{s-KVL}$$

$$\begin{aligned} \tilde{I}(s) &= - \frac{\frac{4}{s} + \frac{12}{3s+4}}{\frac{12s}{3s+4} + \frac{24}{s}} = - \frac{4}{12} \cdot \frac{\frac{1}{s} + \frac{3}{3s+4}}{\frac{s}{3s+4} + \frac{2}{s}} = \\ &= - \frac{1}{3} \cdot \frac{\frac{3s+4+3s}{s(3s+4)}}{\frac{s^2+6s+8}{s(3s+4)}} = - \frac{1}{3} \cdot \frac{6s+4}{s^2+6s+8} \end{aligned}$$

$$\begin{aligned} \tilde{V}(s) &= \tilde{I}_s(s) \cdot \frac{24}{s} + \frac{4}{s} = \frac{4}{s} (6 \cdot \tilde{I}(s) + 1) = \\ &= - \frac{4}{s} \left(2 \frac{6s+4}{s^2+6s+8} - 1 \right) = - \frac{4}{s} \left(\frac{12s+8-s^2-6s-8}{s^2+6s+8} \right) \end{aligned}$$

Example 1 - cont.**3. Partial fraction expansion.**

$$\widetilde{V}(s) = -\frac{4}{s} \cdot \frac{12s+8-s^2-6s-8}{s^2+6s+8} = \frac{4}{s} \cdot \frac{s^2-6s}{s^2+6s+8} = \frac{4(s-6)}{s^2+6s+8}$$

Find poles: $s^2+6s+8=0$

$$s = -3 \pm \sqrt{9-8} = -3 \pm 1 = \{-2, -4\}$$


$$\frac{4(s-6)}{(s+2)(s+4)} = \frac{A}{s+2} + \frac{B}{s+4} = \widetilde{V}(s)$$

$$A = \widetilde{V}(s)(s+2) \Big|_{s=-2} = \frac{4(-8)}{-2+4} = -16$$


$$B = \widetilde{V}(s)(s+4) \Big|_{s=-4} = \frac{4(-10)}{-4+2} = +20$$

$$\widetilde{V}(s) = \frac{-16}{s+2} + \frac{20}{s+4}$$

Example 1 - cont.

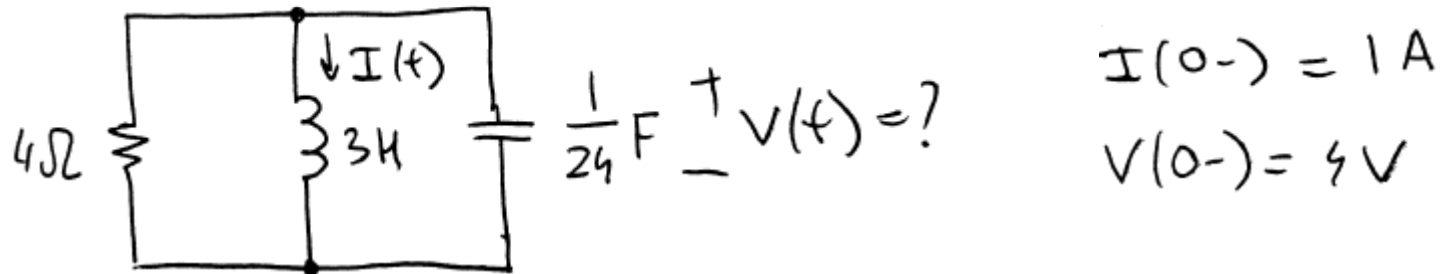

Solution in s-domain:

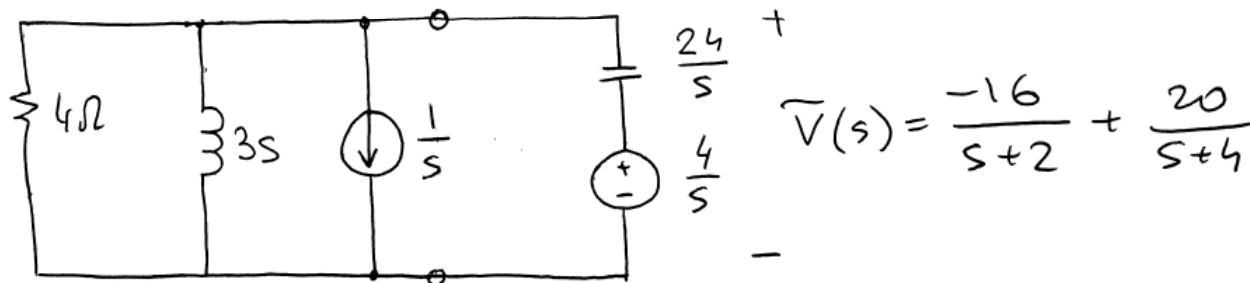


Solution in time-domain: $V(t) = -16e^{-2t} + 20e^{-4t}$


$$t=0 \Rightarrow V(0) = 4$$

$t \rightarrow \infty \Rightarrow V \rightarrow 0$ *Circuit contains resistive element and no independent sources.*


Example 2.

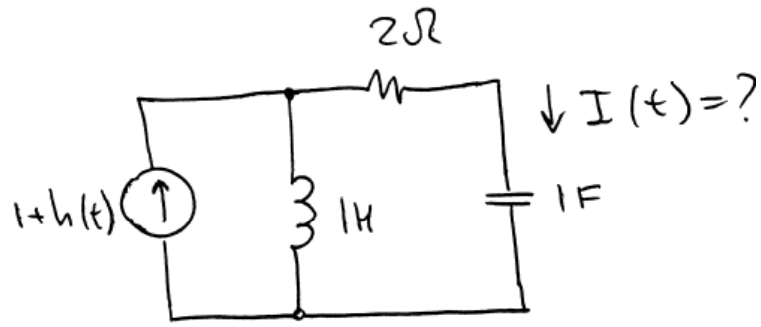

1. Find initial conditions: $t = 0^-$

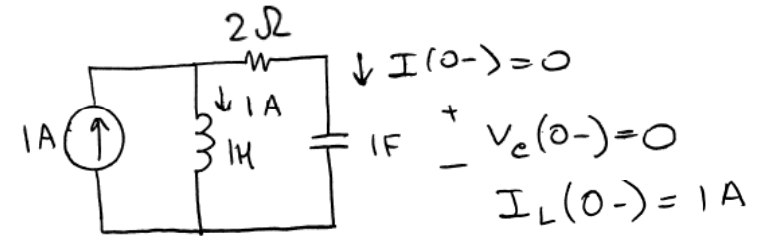


2. Construct s-domain circuit: $t > 0$

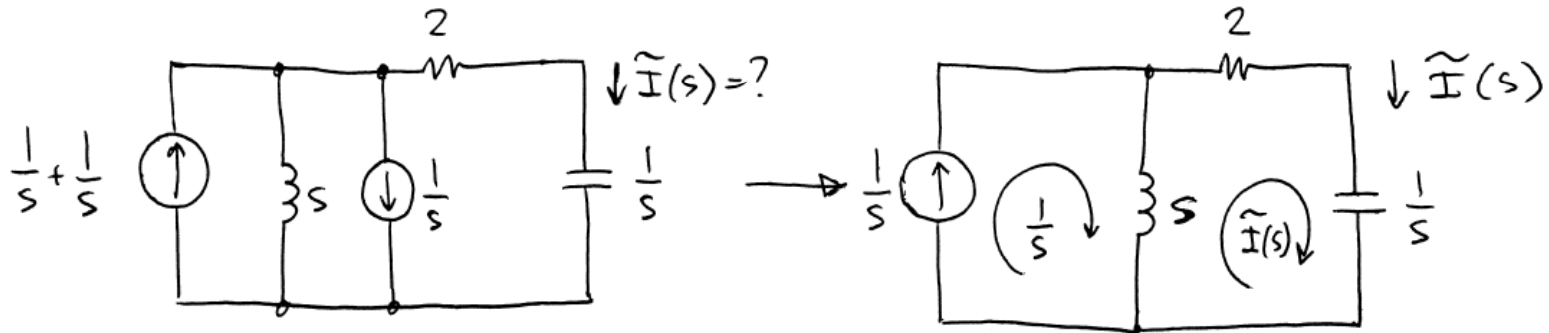


Use mesh analysis – KVL: $s \left(\tilde{I}(s) - \frac{1}{s} \right) + 2 \cdot \tilde{I}(s) + \tilde{I}(s) \frac{1}{s} = 0$


Example 2 - cont.

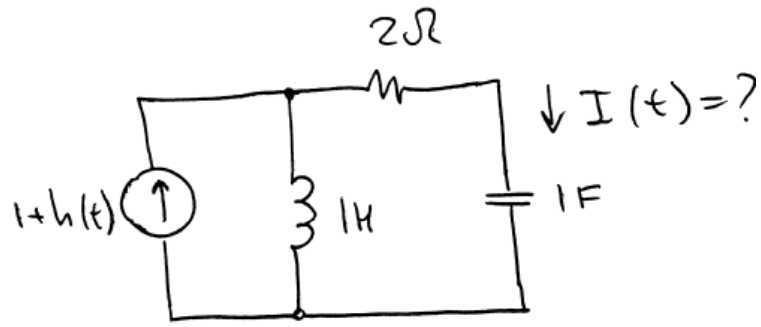

1. Find initial conditions: $t = 0^-$

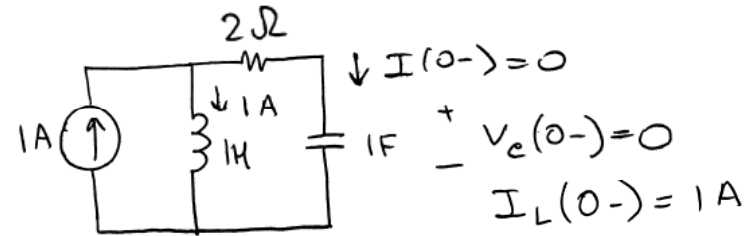

3. Solve in s-domain:

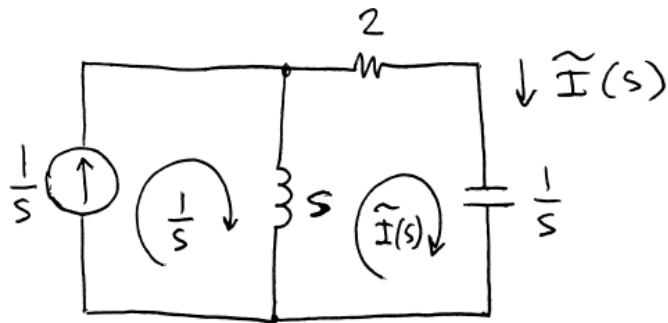


$$s\left(\tilde{I}(s) - \frac{1}{s}\right) + 2 \cdot \tilde{I}(s) + \frac{1}{s} \cdot \tilde{I}(s) = 0$$


$$\tilde{I}(s) \left(s + 2 + \frac{1}{s}\right) = 1 \Rightarrow \tilde{I}(s) = \frac{1}{s + 2 + \frac{1}{s}}$$

$$\tilde{I}(s) = \frac{s}{s^2 + 2s + 1} = \frac{s}{(s + 1)^2}$$

Example 2 - cont.

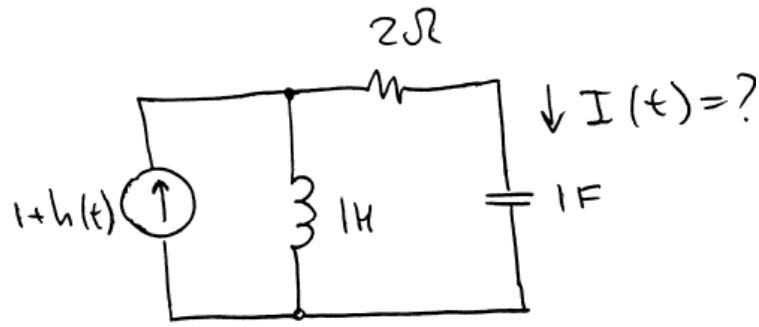

1. Find initial conditions: $t = 0^-$

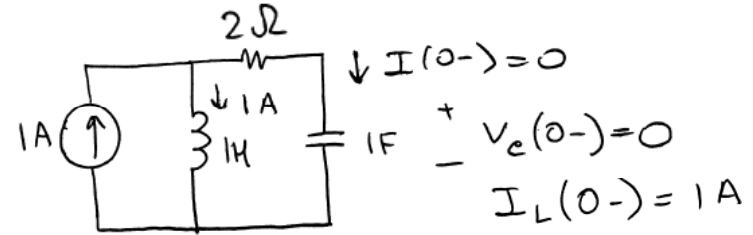

4. Convert to time-domain:

$$\tilde{I}(s) = \frac{s}{(s+1)^2} = \frac{A}{(s+1)^2} + \frac{B}{s+1}$$

$$\begin{cases} A = \left(\tilde{I}(s) \cdot (s+1)^2 \right) \Big|_{s=-1} = -1 \\ B = \frac{d}{ds} \left(\tilde{I}(s) (s+1)^2 \right) \Big|_{s=-1} = 1 \end{cases}$$


$$\tilde{I}(s) = -\frac{1}{(s+1)^2} + \frac{1}{s+1}$$

$$I(t) = -t \cdot e^{-t} + e^{-t} = (1-t)e^{-t}, A$$

$$I(0^+) = 1A \quad \& \quad I(\infty) = 0$$

Transfer function.

We already considered:

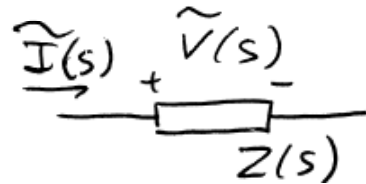


where

$$Z(s) = \left. \frac{\tilde{V}(s)}{\tilde{I}(s)} \right|_{\text{ZERO } I_C}$$

- impedance in s-domain.

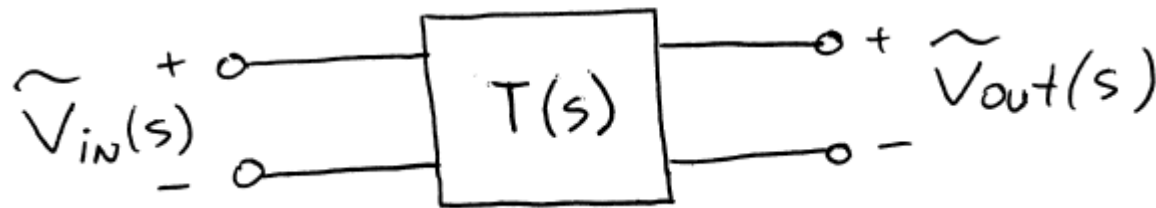
Now let's consider somewhat generalized case:




Transfer function:
$$T(s) = \left. \frac{\tilde{V}_{out}(s)}{\tilde{V}_{in}(s)} \right|_{\text{ZERO } I_C}$$

$$\tilde{V}_{out}(s) = T(s) \cdot \tilde{V}_{in}(s)$$

Transfer function of RC integrator.

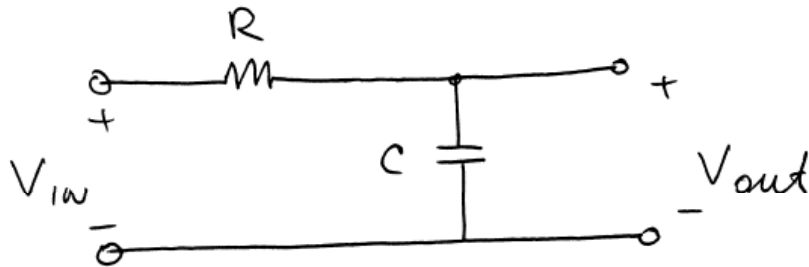


↓ S-DOMAIN + $[1C=0]$

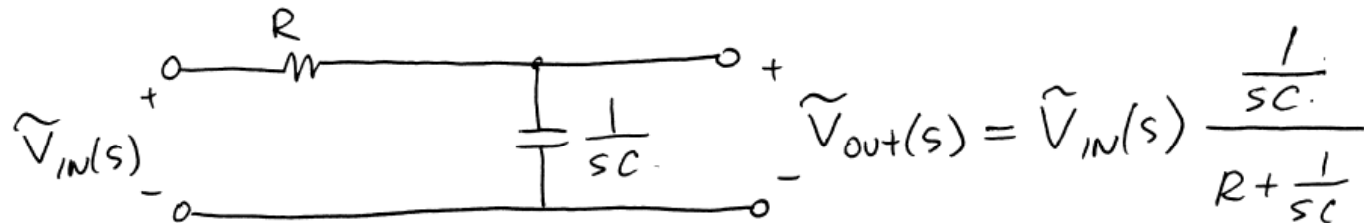

$$T(s) = \frac{\tilde{V}_{out}(s)}{\tilde{V}_{in}(s)} = \frac{1}{1 + s \cdot RC}$$


T-function has single negative real pole: $s = -\frac{1}{RC}$

Example.

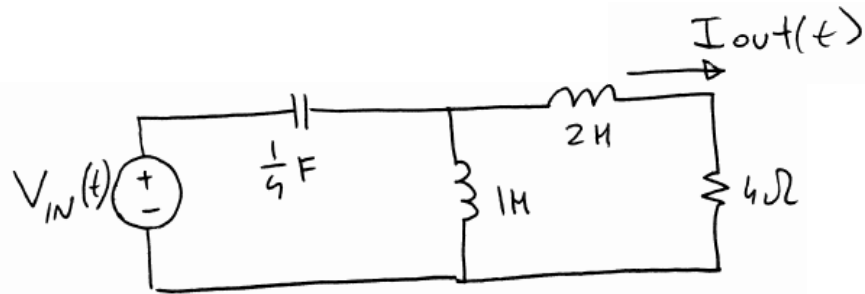

T-function does not necessarily means ratio of voltages.
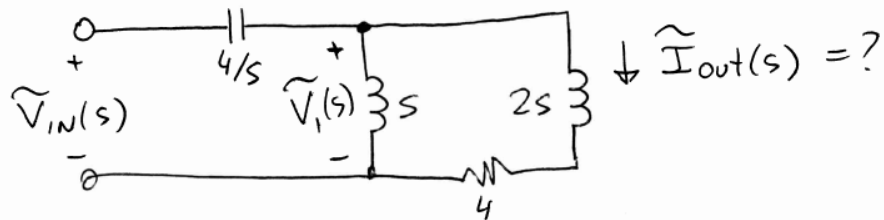
$$T(s) = \frac{\tilde{I}_{out}(s)}{\tilde{V}_{in}(s)} = ?$$



$$\begin{aligned}\tilde{V}_1(s) &= \tilde{V}_{in}(s) \frac{s \parallel (2s+4)}{\frac{4}{s} + s \parallel (2s+4)} = \\ &= \tilde{V}_{in}(s) \cdot \frac{s^2(s+2)}{s^2(s+2) + 2(3s+4)}\end{aligned}$$

$$\tilde{I}_{out}(s) = \tilde{V}_1(s) / (2s+4) = \tilde{V}_{in}(s) \frac{s^2/2}{s^3 + 2s^2 + 6s + 8}$$

$$T(s) = \frac{\tilde{I}_{out}(s)}{\tilde{V}_{in}(s)} = \frac{s^2}{2(s^3 + 2s^2 + 6s + 8)}$$

T-function has two “zeros” $s = 0$ and three “poles”.


Circuits with multiple inputs.

For single input circuit:

$$\widetilde{V}_{out}(s) = T(s) \cdot \widetilde{V}_{in}(s)$$

$$\widetilde{V}_{in}(s) = 0 \Rightarrow \widetilde{V}_{out}(s) = 0$$

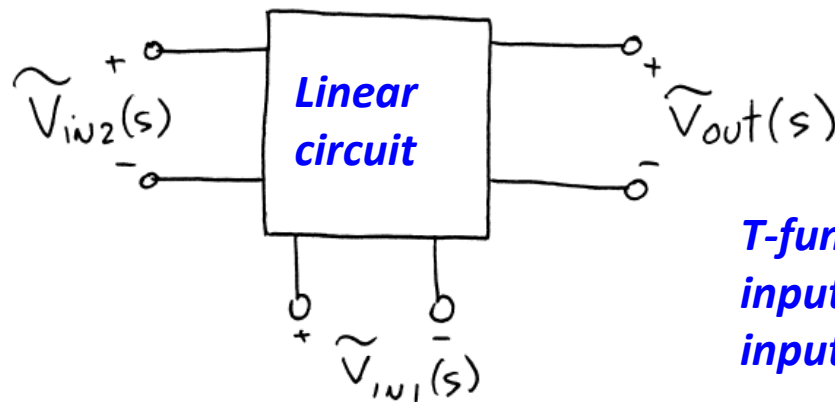But if circuit has independent sources inside then: $\widetilde{V}_{out}(s) \neq 0$




Each source is input.

T-function can be found for each input independently with other inputs "killed".

$$\widetilde{V}_{out}(s) = T_1(s) \Big|_{\widetilde{V}_{in2}=0} \cdot \widetilde{V}_{in1}(s) + T_2(s) \Big|_{\widetilde{V}_{in1}=0} \cdot \widetilde{V}_{in2}(s)$$


**Always use zero initial conditions to compute T-function.*

Example.

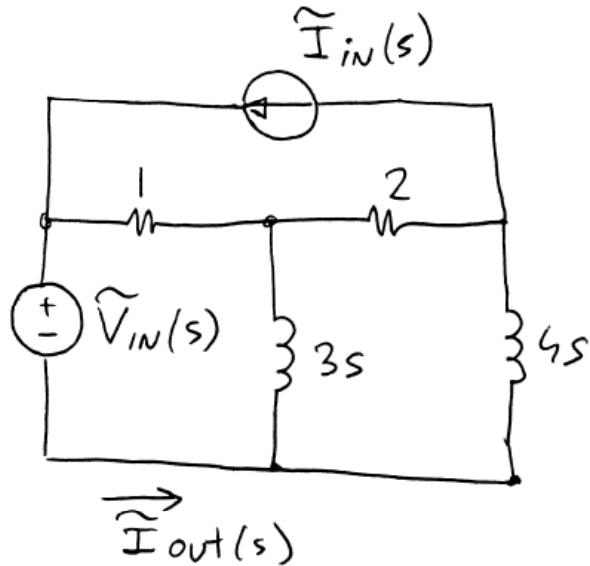

$$\tilde{I}_{out}(s) = T_1(s) \cdot \tilde{V}_{IN}(s) + T_2(s) \cdot \tilde{I}_{IN}(s)$$

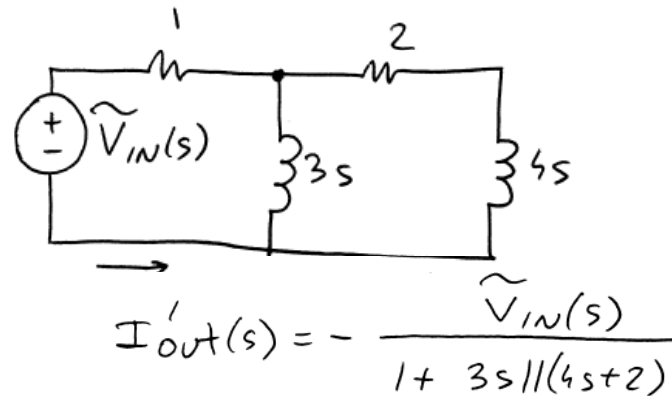
① $T_1(s) = ? \Rightarrow \tilde{I}_{IN}(s) \rightarrow 0$



$$T_1(s) = \frac{I'_{out}(s)}{\tilde{V}_{IN}(s)} = - \frac{1}{1 + \frac{3s(4s+2)}{7s+2}} = \frac{-(7s+2)}{7s+2+12s^2+6s}$$


$$T_1(s) = \frac{-(7s+2)}{12s^2+13s+2}$$

Example - cont.

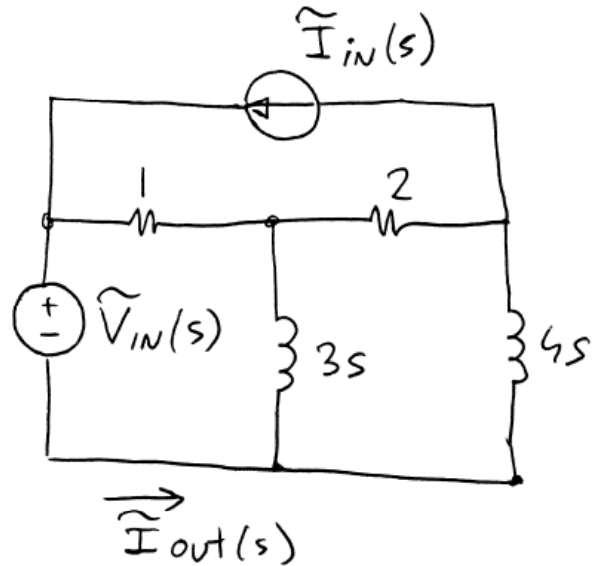

$$\tilde{I}_{out}(s) = T_1(s) \cdot \tilde{V}_{in}(s) + T_2(s) \cdot \tilde{I}_{in}(s)$$

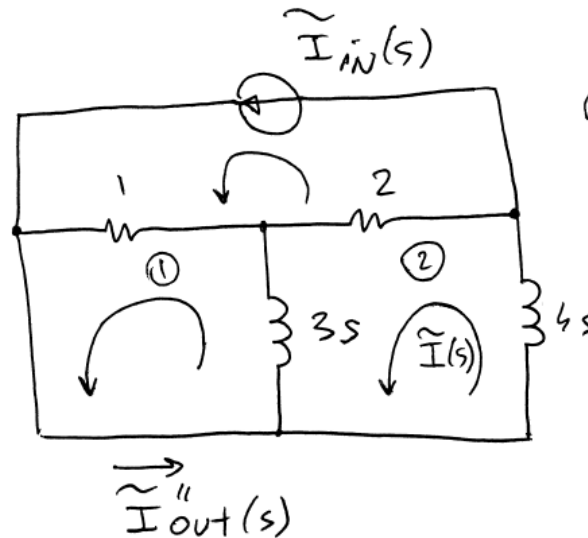② $T_2(s) = ? \Rightarrow \tilde{V}_{in}(s) \rightarrow 0$




① $(\tilde{I}_{out}''(s) - \tilde{I}_{in}(s)) \cdot 1 + (\tilde{I}_{out}''(s) - \tilde{I}(s)) \cdot 3s = 0$

② $\tilde{I}(s) \cdot 4s + (\tilde{I}(s) - \tilde{I}_{in}(s)) \cdot 2 + (\tilde{I}(s) - \tilde{I}_{out}''(s)) \cdot 3s = 0$

$$T_2(s) = \frac{13s + 2}{12s^2 + 13s + 2}$$

Example - cont.

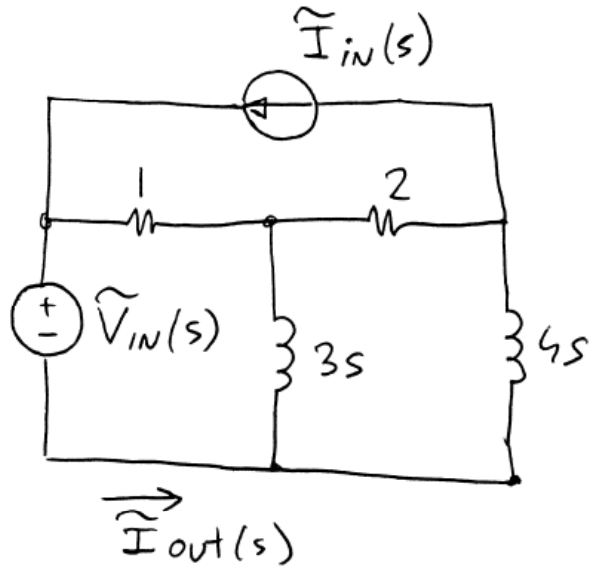


$$\tilde{I}_{out}(s) = T_1(s) \cdot \tilde{V}_{IN}(s) + T_2(s) \cdot \tilde{I}_{IN}(s)$$

$$\tilde{I}_{out}(s) = -\frac{7s+2}{12s^2+13s+2} \cdot \tilde{V}_{IN}(s) + \frac{13s+2}{12s^2+13s+2} \cdot \tilde{I}_{IN}(s)$$


$$\tilde{I}_{IN}(s) = \frac{1}{s} \quad \& \quad \tilde{V}_{IN}(s) = \frac{1}{s}$$

$$\tilde{I}_{out}(s) = \frac{6}{12s^2+13s+2} = \frac{1}{2} \cdot \frac{1}{s^2 + \frac{13}{12}s + \frac{1}{6}} \dots$$

Impulse response

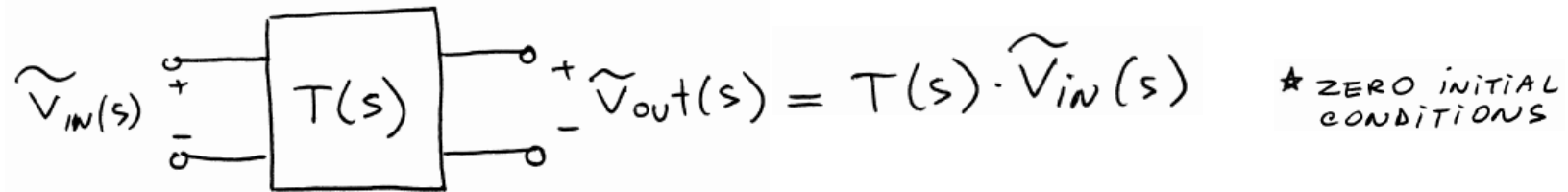

Now assume that

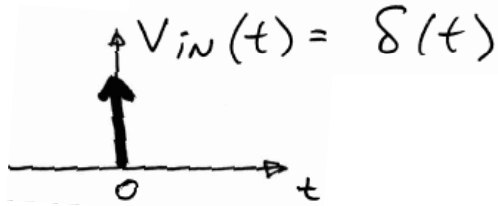

$$L[\delta(t)] = 1 = \widetilde{V}_{in}(s)$$

$$\Rightarrow \widetilde{V}_{out}(s) = T(s) \cdot 1 = T(s)$$


$$L^{-1}[\widetilde{V}_{out}(s)] = V_{out}(t) = L^{-1}[T(s)] = \text{imp}(t)$$

Impulse response

$$T(s) = L[\text{imp}(t)]$$

$$\star \text{imp}(t) = 0 \text{ FOR } t < 0$$

Impulse response of RC-integrator


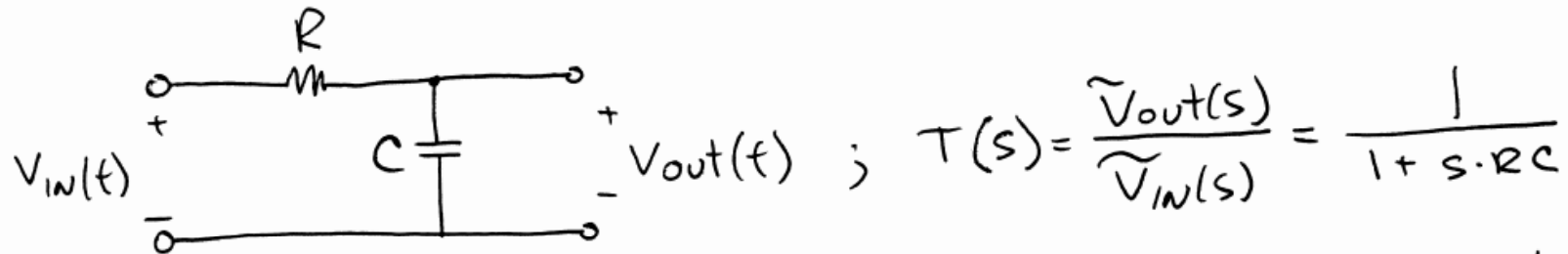


$$T(s) = \frac{\tilde{V}_{out}(s)}{\tilde{V}_{in}(s)} = \frac{1}{1 + s \cdot RC}$$


$$imp(t) = L^{-1} [T(s)] = L^{-1} \left[\frac{1}{1 + s \cdot RC} \right] = \frac{1}{RC} \cdot L^{-1} \left[\frac{1}{s + \frac{1}{RC}} \right]$$

$$\star L[e^{-\alpha t}] = \frac{1}{s + \alpha}$$
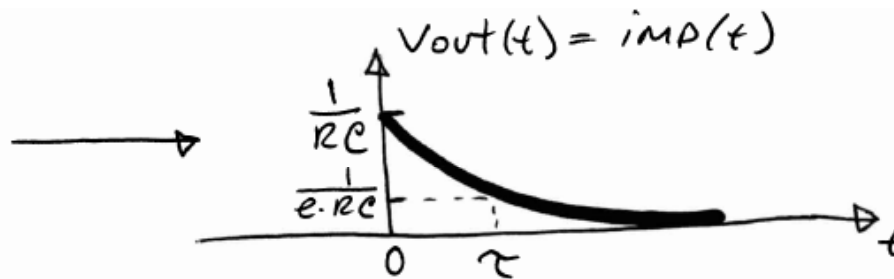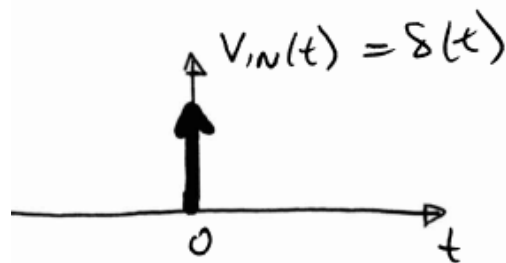
$$imp(t) = \frac{h(t)}{RC} \cdot \exp\left(-\frac{t}{RC}\right)$$



Impulse response of RC-differentiator

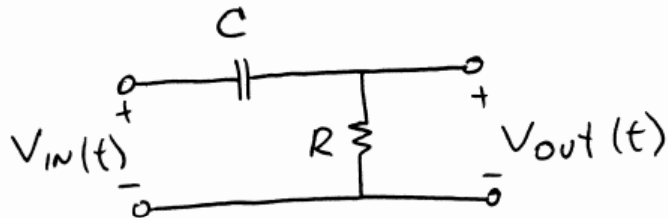



AGAIN $V_{in}(t) = \delta(t)$

$\Rightarrow V_{out}(t) = \text{imp}(t)$


$$\text{imp}(t) = \mathcal{L}^{-1}[T(s)] \quad ; \quad T(s) = \frac{R}{R + \frac{1}{sC}} = \frac{s \cdot RC}{1 + s \cdot RC}$$

$$T(s) = \frac{s \cdot RC}{1 + s \cdot RC} = \frac{s \cdot RC + 1 - 1}{1 + s \cdot RC} = 1 - \frac{1}{1 + s \cdot RC}$$
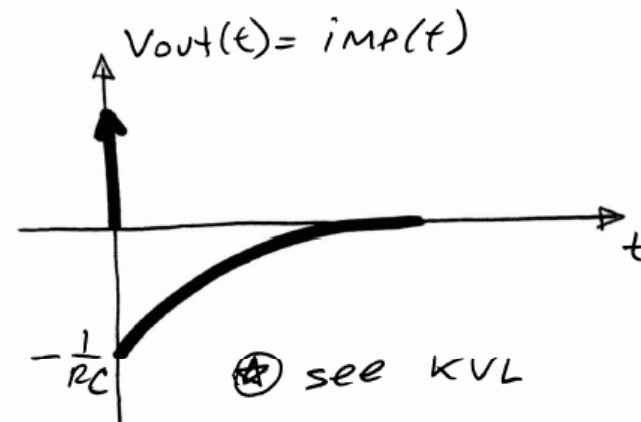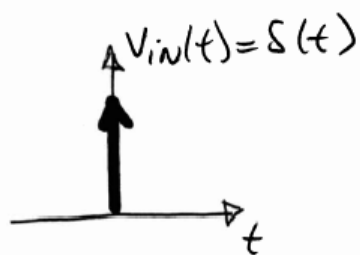
$$\text{imp}(t) = \delta(t) - \frac{1}{RC} \cdot \exp\left(-\frac{t}{RC}\right) \cdot h(t)$$



Example.

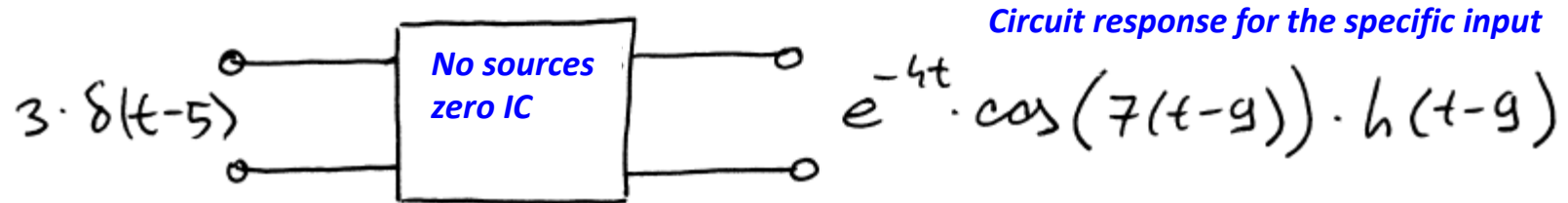

Find: $T(s) = ?$ & $i_{mp}(t) = ?$

$$\textcircled{1} \quad \mathcal{L}[3 \cdot \delta(t-5)] = 3 \cdot \mathcal{L}[\delta(t-5)] = 3 \cdot e^{-5s} \cdot 1 = 3e^{-5s}$$

$$\star \quad \mathcal{L}[v(t-t_0) \cdot h(t-t_0)] = e^{-s \cdot t_0} \cdot \tilde{v}(s)$$


$$\textcircled{2} \quad \mathcal{L}[e^{-4t} \cdot \cos(7(t-9)) \cdot h(t-9)] = \mathcal{L}[e^{-4(t-9+9)} \cdot \cos(7 \cdot (t-9)) \cdot h(t-9)] =$$

$$= e^{-4 \cdot 9} \cdot \mathcal{L}[e^{-4(t-9)} \cdot \cos(7 \cdot (t-9)) \cdot h(t-9)] =$$

$$= e^{-36} \cdot e^{-9s} \cdot \mathcal{L}[\underbrace{e^{-4t} \cdot \cos(7t)}] = e^{-36} \cdot e^{-9s} \cdot \frac{s+4}{(s+4)^2 + 7^2}$$

Damped cosine – use table

Example - cont.

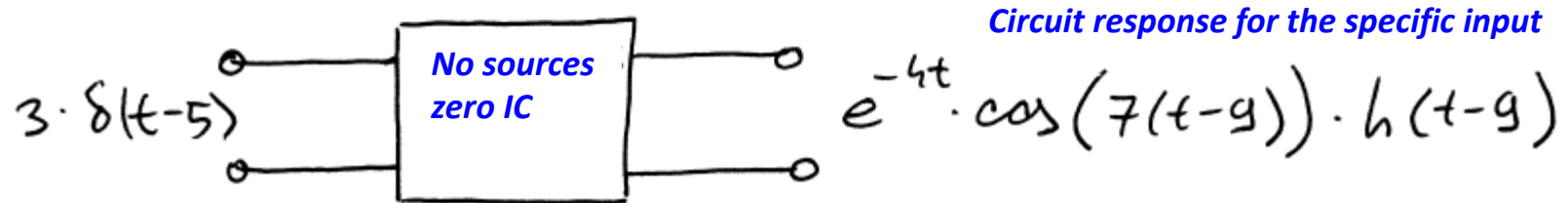

Find: $T(s) = ?$ & $\text{imp}(t) = ?$

$$T(s) = \frac{\widehat{V}_{out}(s)}{\widehat{V}_{in}(s)} = \frac{e^{-36} \cdot e^{-9s} \cdot (s+4)}{(s+4)^2 + 49} \bigg/ 3 \cdot e^{-5s}$$

$$T(s) = \frac{1}{3} \cdot e^{-36} \cdot e^{-4s} \cdot \frac{s+4}{(s+4)^2 + 49}$$

Damped cosine time shifted by 4 seconds

$$\begin{cases} \mathcal{L}[e^{-\alpha t} \cos \omega t] = \frac{s+\alpha}{(s+\alpha)^2 + \omega^2} \\ \mathcal{L}[v(t-t_0)h(t-t_0)] = e^{-st_0} \cdot \widetilde{V}(s) \end{cases}$$

$$\begin{aligned} \text{imp}(t) &= \mathcal{L}^{-1}[T(s)] = \frac{e^{-36}}{3} \cdot e^{-4(t-4)} \cdot \cos(7(t-4)) \cdot h(t-4) = \\ &= \frac{1}{3} \cdot e^{-4(t+5)} \cdot \cos(7(t-4)) \cdot h(t-4) \end{aligned}$$

Observe: $\text{imp}(t) = 0$ FOR $t < 4$