

# EE P 538

# Analog Circuits for Sensor Systems

Spring 2020

Instructor: Jason Silver, PhD

# Announcements

- Midterm due Sunday, May 17 at midnight
- Assignment 6 due Saturday, May 23 at midnight

# Week 7

- AoE Chapter 6 – Filters
  - Sections 6.1, 6.2
- James Karkin – Active Low-Pass Filter Design
  - [TI Application Note SLOA049B](#)
- James Karkin – Sallen–Key Filter Analysis
  - [TI Application Note SLOA024B](#)

# Overview


- Last time...
  - Thermal, flicker, and shot noise
  - Analyzing circuits with noise
  - Noise bandwidth
  - Opamp noise
- Today...
  - Noise filtering
  - Butterworth, Chebyshev, and Bessel filters
  - Sallen–Key filter architecture

# Lecture 7 – Filters 1

“An ideal electrical filter should not only completely reject the unwanted frequencies but should also have uniform sensitivity for the wanted frequencies.”


– *Stephen Butterworth*

# Front-End Gain

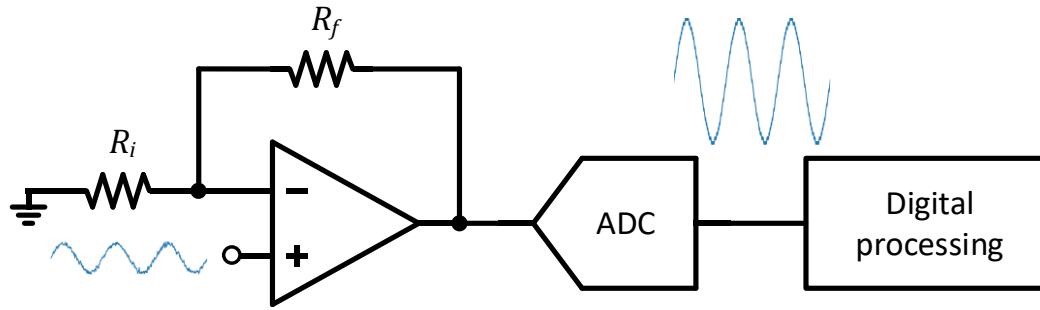

- The first circuit a sensor or transducer signal sees typically has a substantial amount of gain (20dB or higher)
- Gain is used to desensitize signals both to downstream noise and the finite resolution of ADCs
- An ideal amplifier merely increases the amplitude of a signal without adding noise

# Noise Bandwidth

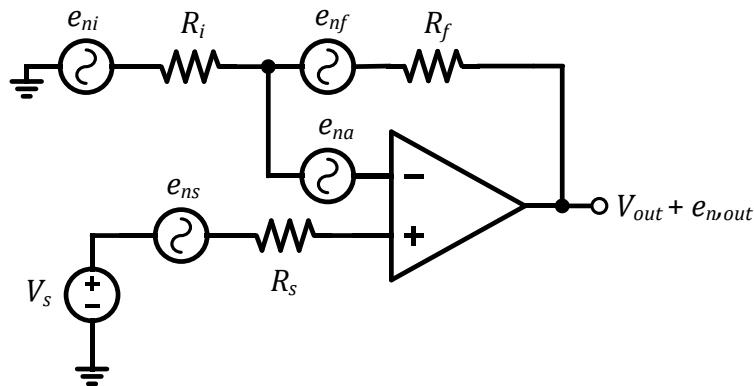

$$V_{out(rms)} = V_{out,pp}/\sqrt{2}$$

$$v_{n,out(rms)} \approx \sqrt{e_{n,out}^2 f_{ENB}}$$

$$SNR = V_{out(rms)} / v_{n,out(rms)}$$

- Unfortunately, all electronic components used to process signals contribute some amount of additional noise
- That is, a circuit can only *increase*, never reduce, the RMS noise in a given bandwidth
- In order to build precision circuits, we need to limit bandwidth to what is required for a given application



# Signal-to-Noise Ratio (SNR)


- Signal-to-noise ratio is the ratio of RMS signal amplitude the RMS noise
- For example, suppose we want to amplify and digitize a sensor signal with a peak-to-peak amplitude of 5mV and achieve an SNR of  $\geq 80\text{dB}$
- The signal-to-noise ratio is given by

$$SNR = 20 \log \frac{v_{s(rms)}}{v_{n(rms)}} = 20 \log \frac{1.77\text{mV}}{v_{n(rms)}} = 80\text{dB}$$

- To meet this specification, the noise should be

$$v_{n(rms)} \leq \frac{1.77\text{mV}}{10^{\frac{80\text{dB}}{20}}} = 177\text{nV}$$

# Gain Stage Noise

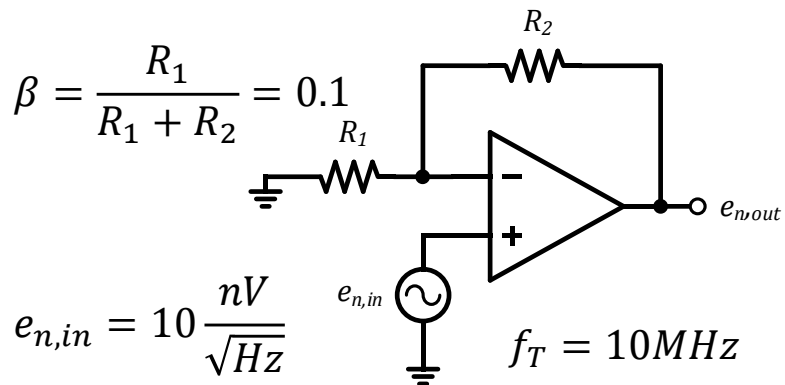


$$f_{3dB,CL} = \beta f_T = 1MHz$$

$$f_{ENB,amp} = \frac{\pi}{2} \beta f_T \approx 1.57MHz$$

$$v_{n,in(rms)} \approx \sqrt{e_{n,in}^2 f_{ENB}} \approx 12.5\mu V$$

- For high precision, opamp bandwidth may be much wider than that required for the signal
- This results in a wide noise bandwidth, and consequently a large amount of noise and degraded SNR
- In order to limit the RMS noise and improve the SNR, we need to add filtering

# RC Lowpass Filter

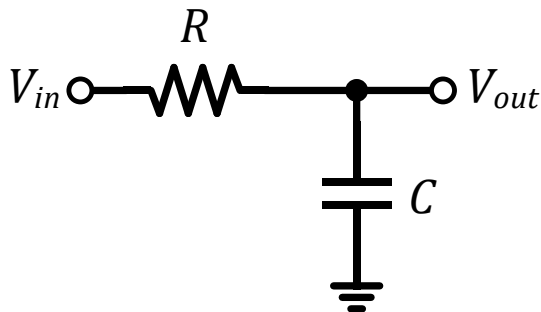

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (f/f_{3dB})^2}} \quad f_{3dB} = 1/RC$$

$$f_{ENB} = \frac{\pi}{2} f_{3dB} \approx 1.57 f_{3dB}$$

- What about adding a single-pole passive RC filter?
- The noise bandwidth is approximately  $\sim 1.57 f_{3dB}$ , which can be used to limit the total noise from the amplifier
- However, we need to ensure that the filter's “gain” doesn't vary significantly over the bandwidth of the signal

# Signal vs Noise Bandwidth

- Suppose we want to pass a given signal with less than 5% attenuation across its bandwidth
- To do this, we need a filter that satisfies

$$\frac{1}{\sqrt{1 + (f_{SBW}/f_{3dB})^2}} = 0.95 \quad \longrightarrow \quad f_{SBW} \approx 0.33f_{3dB}$$


- We know the equivalent noise bandwidth ( $f_{ENB}$ ) is  $\sim 1.57f_{3dB}$ , so the ratio between the noise and signal bandwidths is

$$f_{ENB}/f_{SBW} \approx 4.8$$

- This means that the SNR performance is  $4.8\times$  worse than that of a brick wall filter with a bandwidth of  $f_{SBW}$ ! ([Ltspice: RC filter](#))
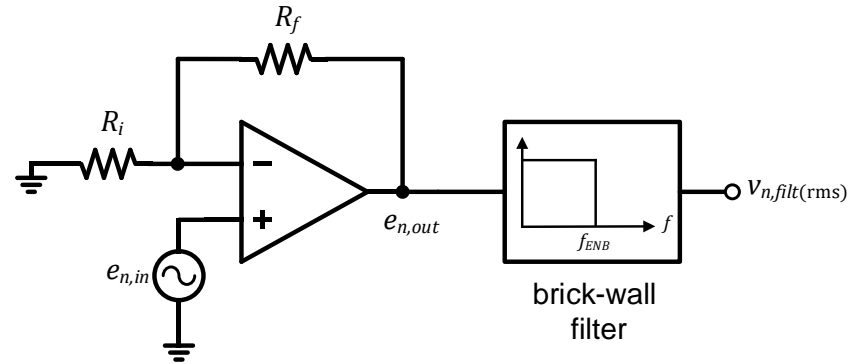
# Ideal Filter

- The bandwidth of the signal is fixed by the application, and sets the minimum limit on the circuit bandwidth
- For example for audio applications, the range of audible frequencies is from about 20Hz to 20kHz
- To maximize SNR, we should ensure that the noise bandwidth is as narrow as possible, ideally equal to the signal bandwidth




$$v_{n,filt(rms)} = \sqrt{e_{n,in}^2 A_{CL}^2 f_{ENB} V / \sqrt{Hz}}$$

$$f_{ENB,ideal} = f_{SBW}$$
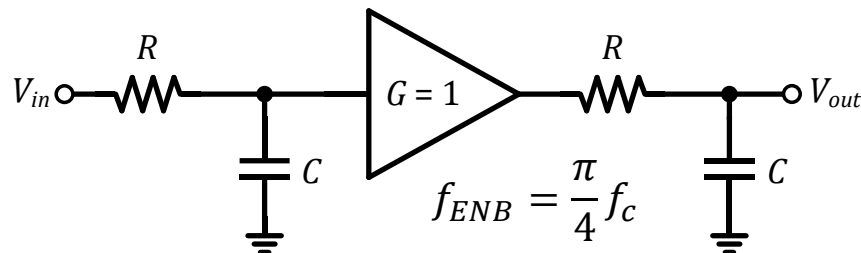
# Filter Cascading

- If we cascade multiple passive RC filters, can we do better?
- The equivalent noise bandwidth, which is determined by the total noise power across the frequency spectrum, is reduced by half
- However, the “passband” is also reduced, resulting in only a modest improvement
- To improve upon this, we need less attenuation in the pass band and steeper roll-off



**5% attenuation:** 
$$\frac{1}{1 + (f_{SBW}/f_0)^2} = 0.95$$

$$f_{SBW} = 0.23f_0$$

$$f_{ENB}/f_{SBW} \approx 3.4$$


# First-Order Filter

- The dynamic behavior of a 1<sup>st</sup> order filter is fully described by a single parameter,  $\omega_0$ :


$$H(s) = \frac{\omega_0}{s + \omega_0}$$

- To determine  $\omega_0$ , we solve for the pole frequency by setting the denominator of the transfer function equal to 0:

$$s_0 = -\omega_0 \quad \omega_0 = |s_0|$$

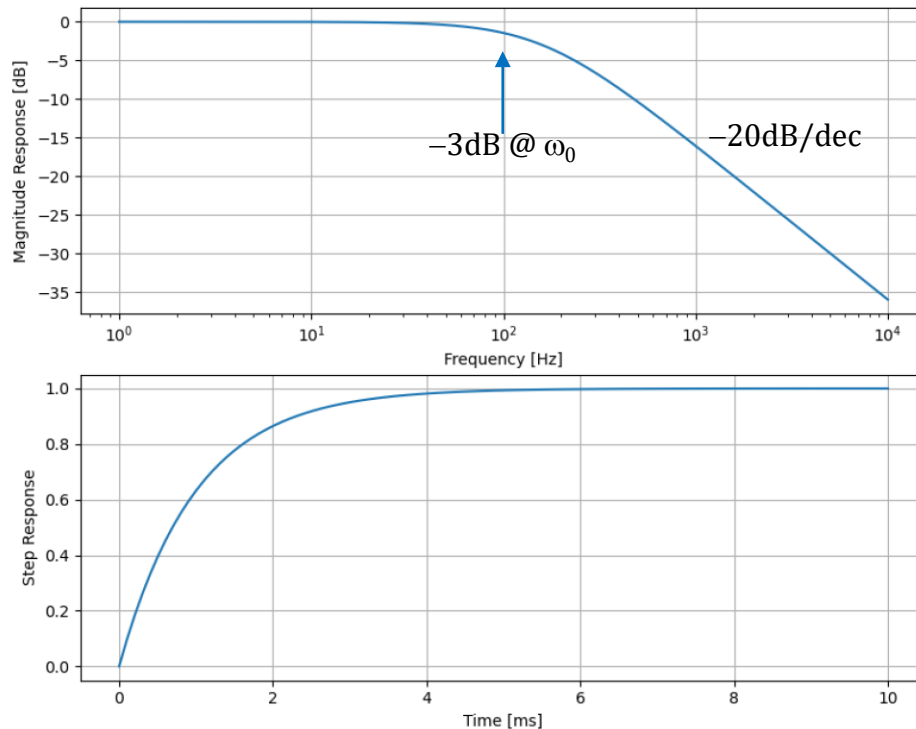


# 1<sup>st</sup> Order RC Filter

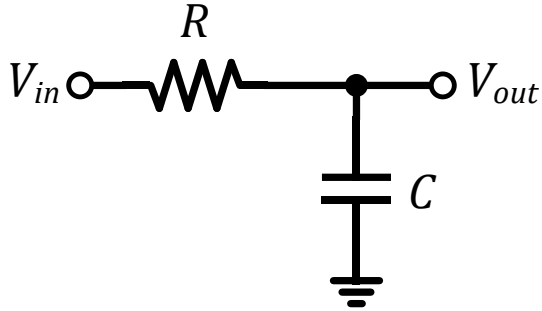

$$\frac{V_{out}}{V_{in}} = \frac{1/RC}{s + 1/RC} = \frac{\omega_0}{s + \omega_0}$$
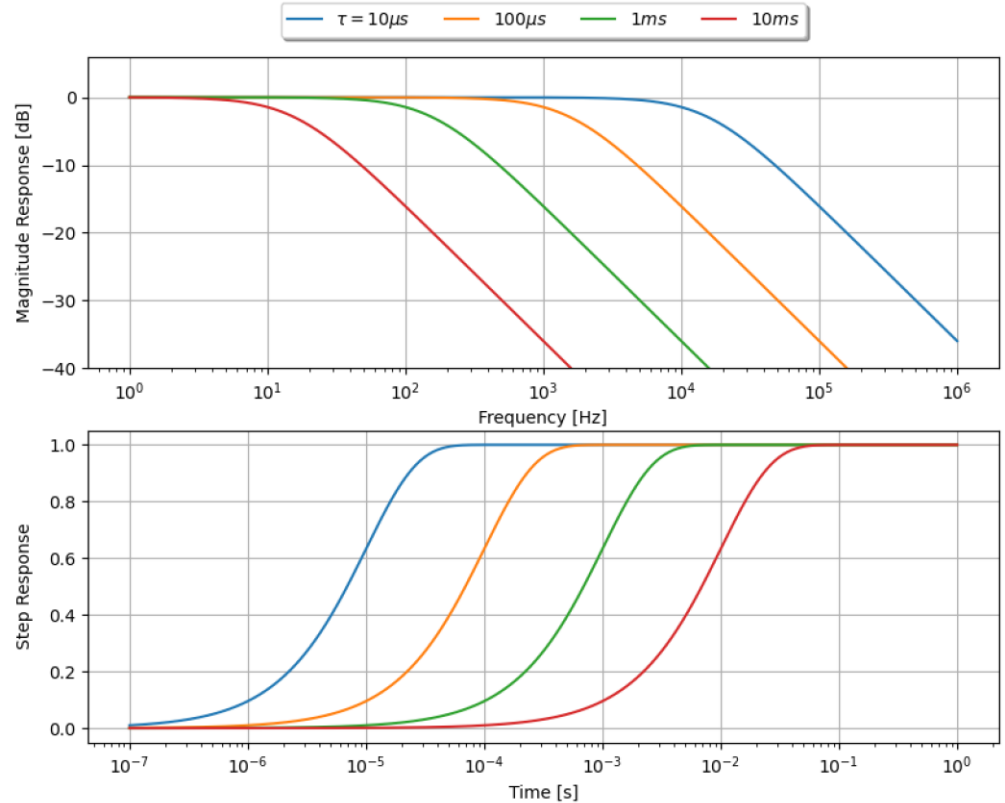
$$\omega_0 = \frac{1}{RC} = \frac{1}{\tau} \quad f_{3dB} = \frac{\omega_0}{2\pi}$$





# Second Order Filter

- The “order” of a filter is determined the number of poles in its transfer function, which for an analog filter depends on the number of reactive components (i.e. inductors and capacitors)
- For a second-order filter, rather than depending on only a single parameter  $\omega_0$ , the response is governed by two parameters,  $\omega_0$  and  $Q$
- The transfer function of a second order filter is given by


$$H(s) = \frac{\omega_0^2}{s^2 + 2\zeta\omega_0s + \omega_0^2}$$

where

$$Q = \frac{\omega_0}{2\zeta\omega_0}$$

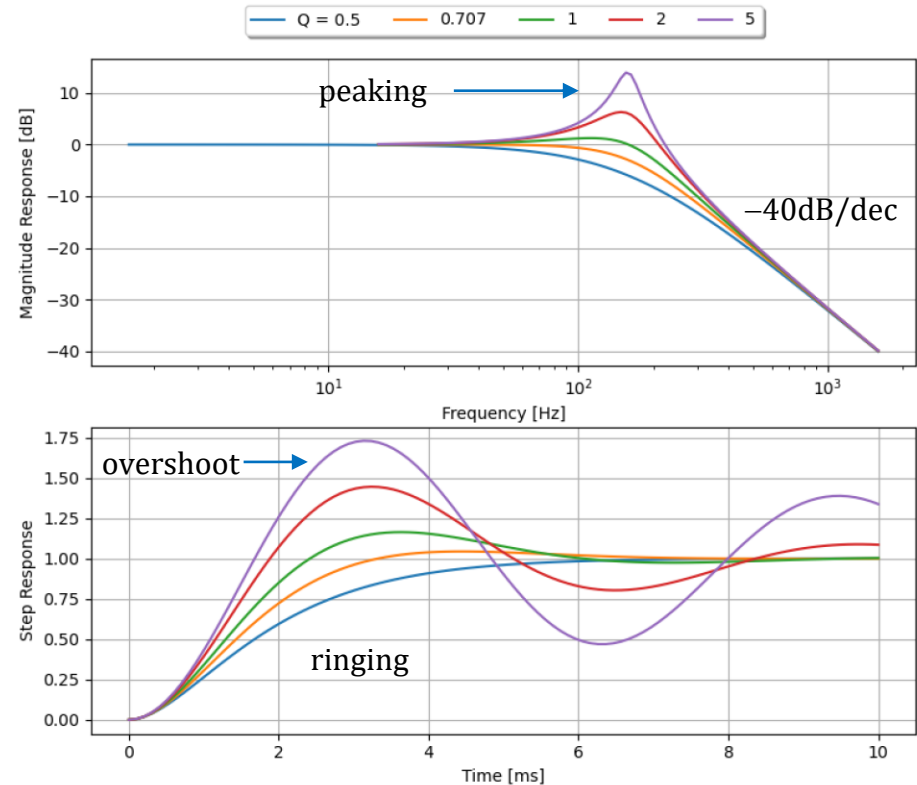
# Quality Factor (Q)

- While  $\omega_0$  still somewhat controls the settling of the transient response and the bandwidth of the frequency response, the *quality* of the response is determined by Q
- A higher value of Q results in more *peaking* in the frequency response and more *ringing* in the step response
- Depending on the application, both peaking and ringing (or neither) may be acceptable



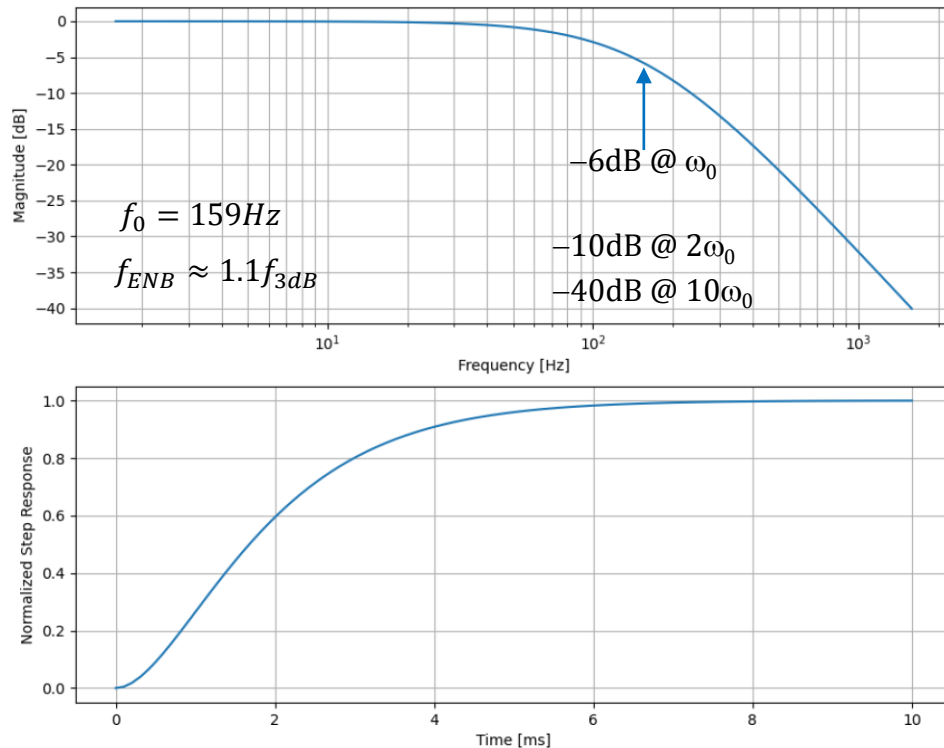
# 2<sup>nd</sup> Order RC Filter Response

- How does the RC filter cascade with a buffer in between stages perform?
- The Q factor is low (0.5), resulting in an *overdamped* response in the time domain
- The roll-off eventually reaches -40dB/dec, but it does so over a wide frequency range
- Attenuation at the “cutoff” frequency is severe at 6dB, so the useful signal bandwidth low



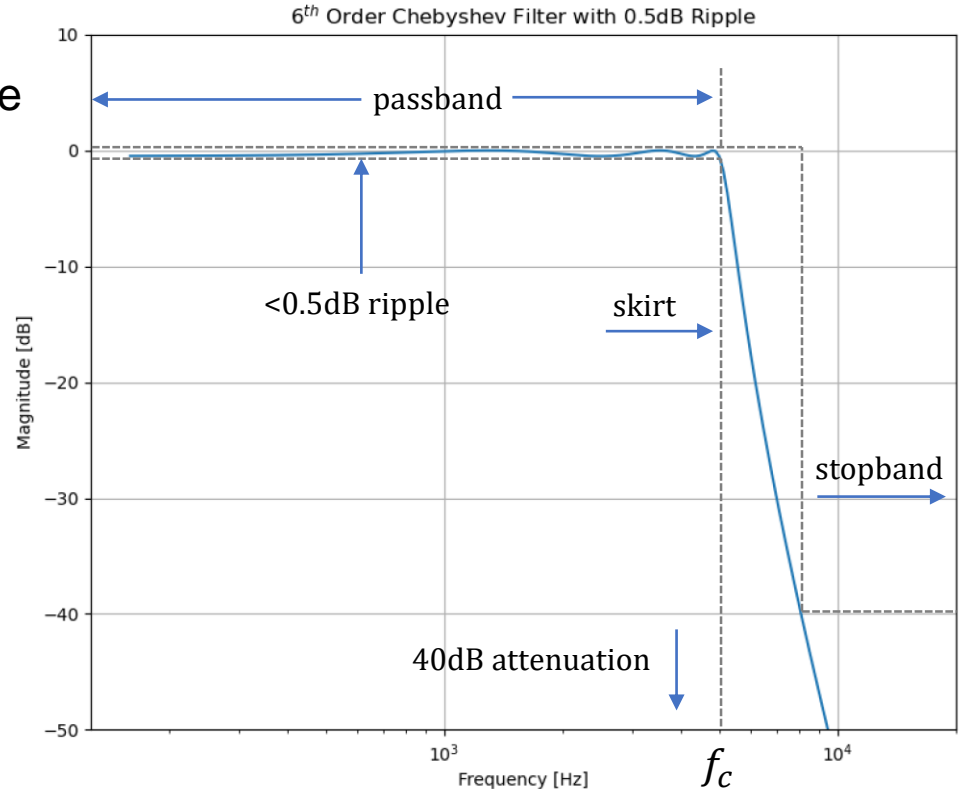
# Frequency Domain Specifications

- *Passband*
  - Region of frequencies with little attenuation
- *Cutoff frequency ( $f_c$ )*
  - End of the passband
- *Transition region*
  - Transition from passband to stopband
- *Stopband*
  - Defined by a minimum required attenuation above a given frequency


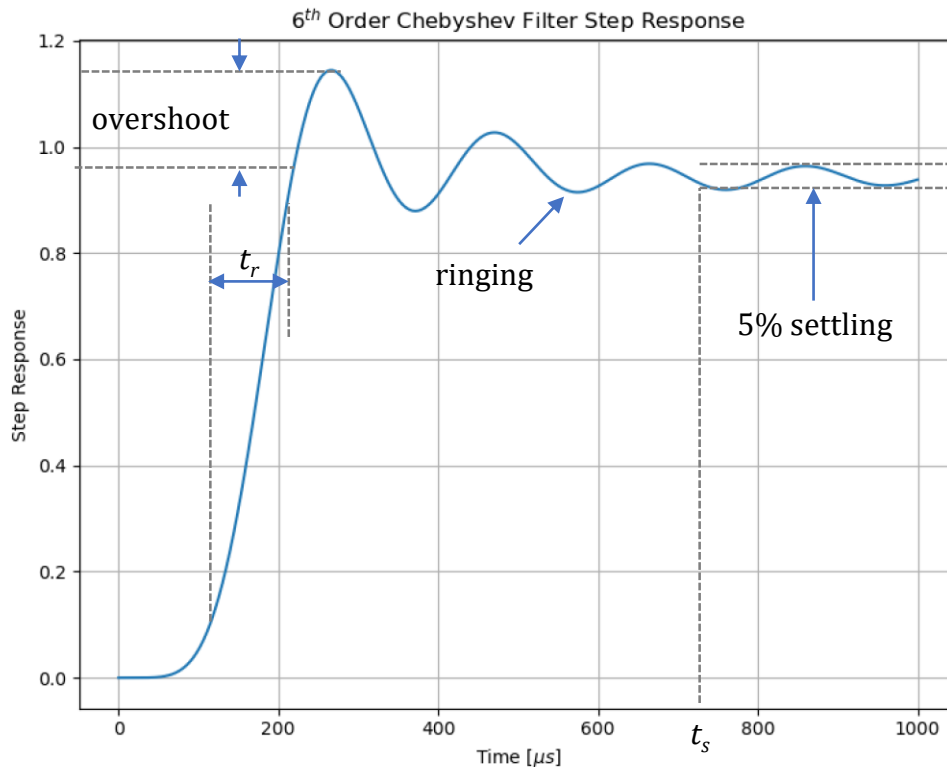
# Time-Domain Specifications

- *Rise time* is the time required to go from 10% to 90%
- *Settling time* is the time required to arrive within some specified range of the final value and remain there
- *Overshoot* and *ringing* describe (typically) undesirable characteristics that affect settling
- The step response of a filter may be of particular interest if the signal contains steps/pulses



# Butterworth Filter


- Designed to ensure minimal variation in the filter gain over the passband
- The magnitude response of a Butterworth filter is given by

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{(1 + (f/f_c)^{2n})^{\frac{1}{2}}}$$

- $n$  is the order of the filter and  $f_c$  is the cutoff frequency, the frequency at which the magnitude has decreased by 3dB
- The  $Q$  factor of a second order Butterworth filter is  $1/\sqrt{2}$ , giving an underdamped response with some peaking in the frequency domain and minor ringing in the time domain
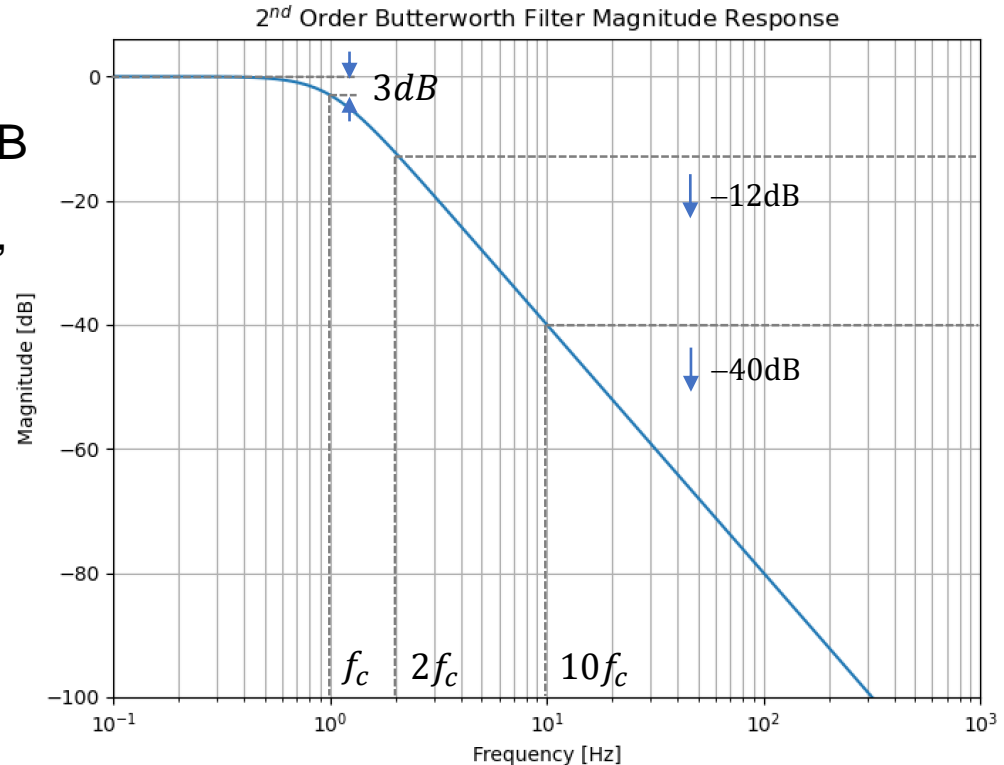
# Butterworth Magnitude Response

- No ripple in the passband, and minimal attenuation at low frequencies (approximately 0.1dB up to  $f_c/2$ )
- However, the passband “droops” early, resulting in  $-3dB$  attenuation at  $f_c$
- The stopband begins somewhat late, due to the slow transition from the passband



# Chebyshev Filters

- Maximum flatness in the passband may not be critical, as long as ripple is kept below some critical value (e.g. 0.1 or 0.5 dB)
- Chebyshev filters achieve much steeper roll-off in the transition band at the expense of increased ripple in the passband
- This tradeoff often proves beneficial, as design specifications can be achieved with fewer poles (relative to a Butterworth design)
- The magnitude response of a Chebyshev filter is given by


$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\left( 1 + \varepsilon^2 C_n^2(f/f_c) \right)^{\frac{1}{2}}}$$

where  $C_n$  is an  $n^{\text{th}}$  order Chebyshev polynomial and  $\varepsilon$  is a constant that sets the passband ripple ( $2^{\text{nd}}$  order  $Q$  factor depends on  $\varepsilon$ )



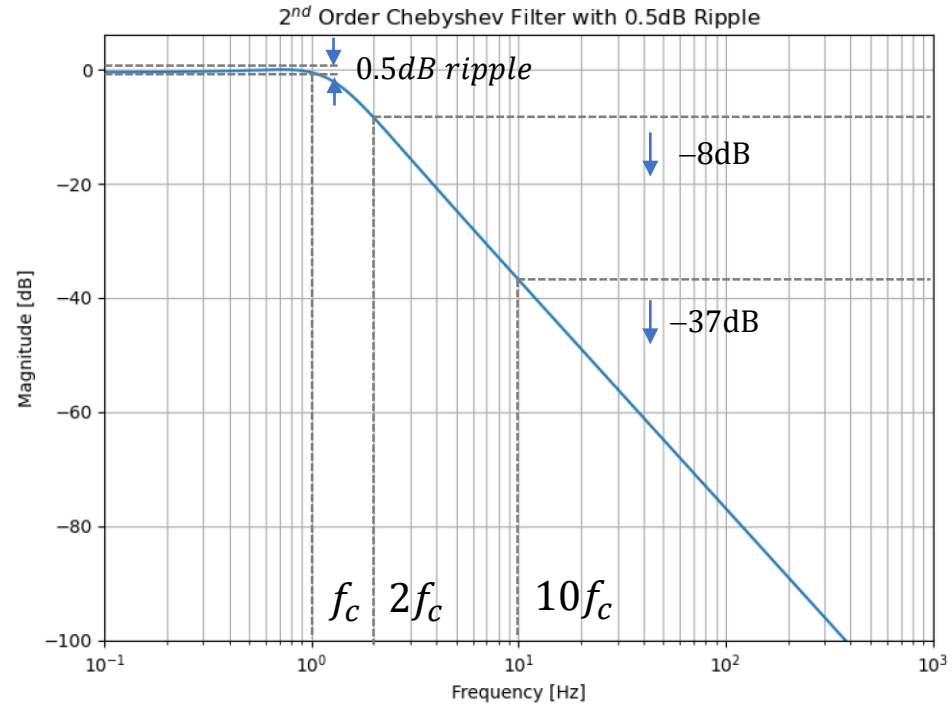
# Chebyshev Magnitude Response

- Designed for a sharp transition region, which is a trade-off for ripple in the passband
- For a Chebyshev design,  $f_c$  is defined as the frequency at which the response exits the ripple band
- The narrower filter bandwidth can reduce noise and improve SNR (depending on ripple spec and filter order)
- For the 2<sup>nd</sup> order Chebyshev, the stopband begins later than for the Butterworth design



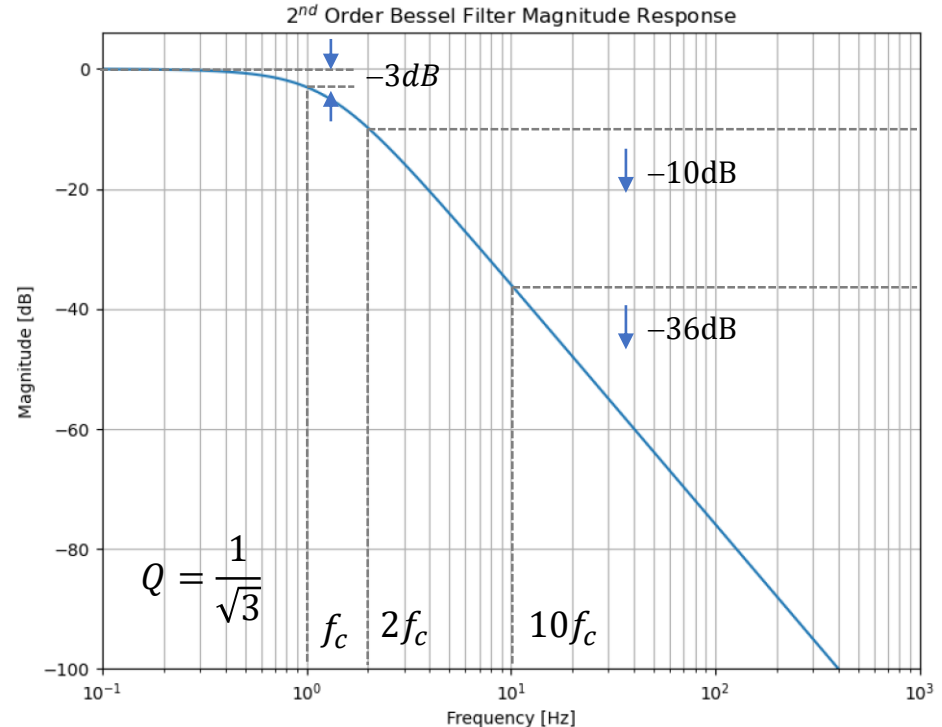
# Bessel Magnitude Response

- The magnitude response of the Bessel filter exhibits even more “passband droop” than the Butterworth filter
- $f_c$  for a 2<sup>nd</sup> order Bessel filter is 1.272 times lower than  $f_o$  for -3dB attenuation at  $f_c$
- The primary advantage of the Bessel filter lies in the phase domain, with a parameter called “group delay”, which ensures equal time delays for different frequencies



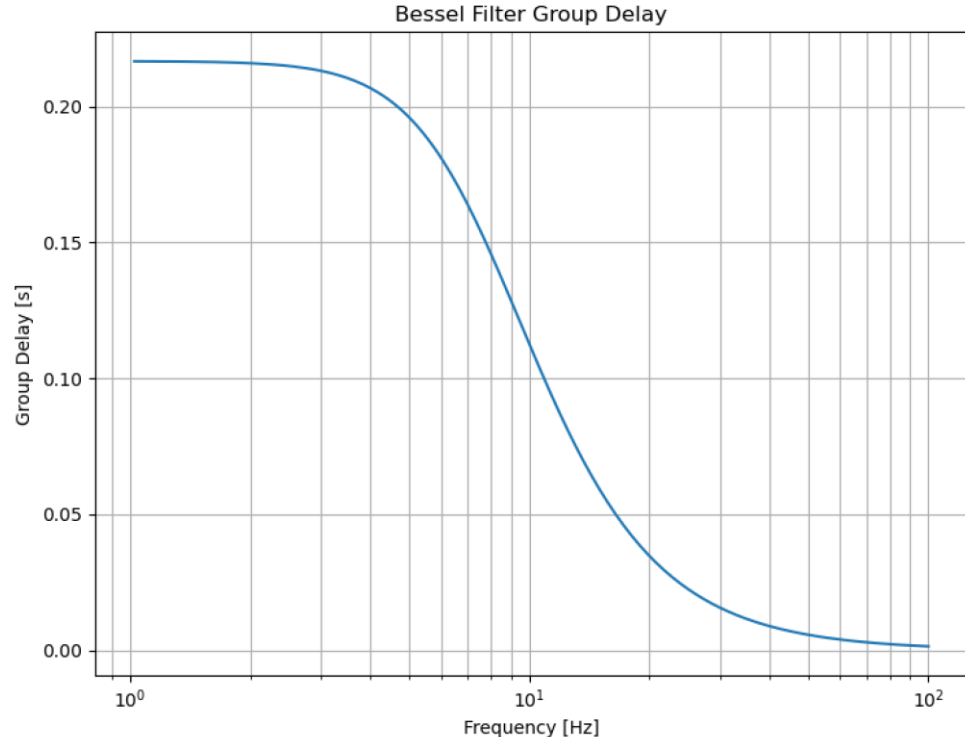
# Bessel Group Delay

- Group delay is the time delay for different frequencies through a filter or system
- It is defined as the derivative of phase with respect to frequency
- A constant group delay means that different frequency sinusoids pass through with identical time delays
- Bessel filters exhibit maximally flat group delay, similar to the magnitude of a Butterworth filter



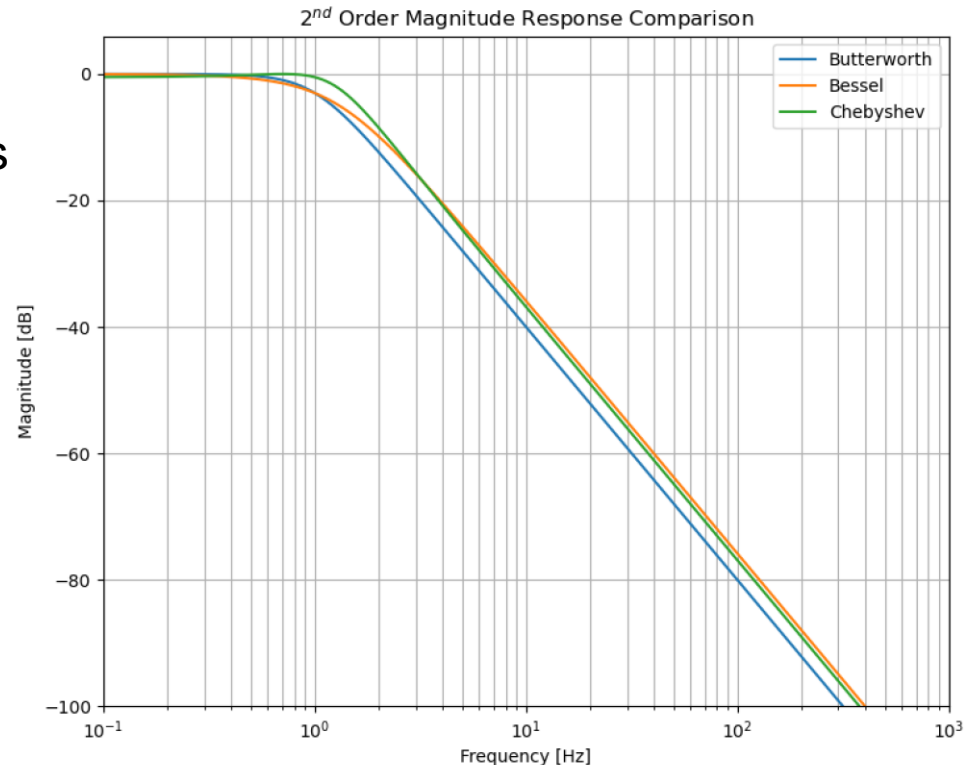
# Magnitude Response Comparison

- In the frequency domain, the salient characteristics of the three filters types can be summarized as follows:
  - *Butterworth*: maximally flat, minor peaking
  - *Chebyshev*: widest passband, with ripple as a design parameter
  - *Bessel*: Almost no peaking, slower transition to maximum roll-off


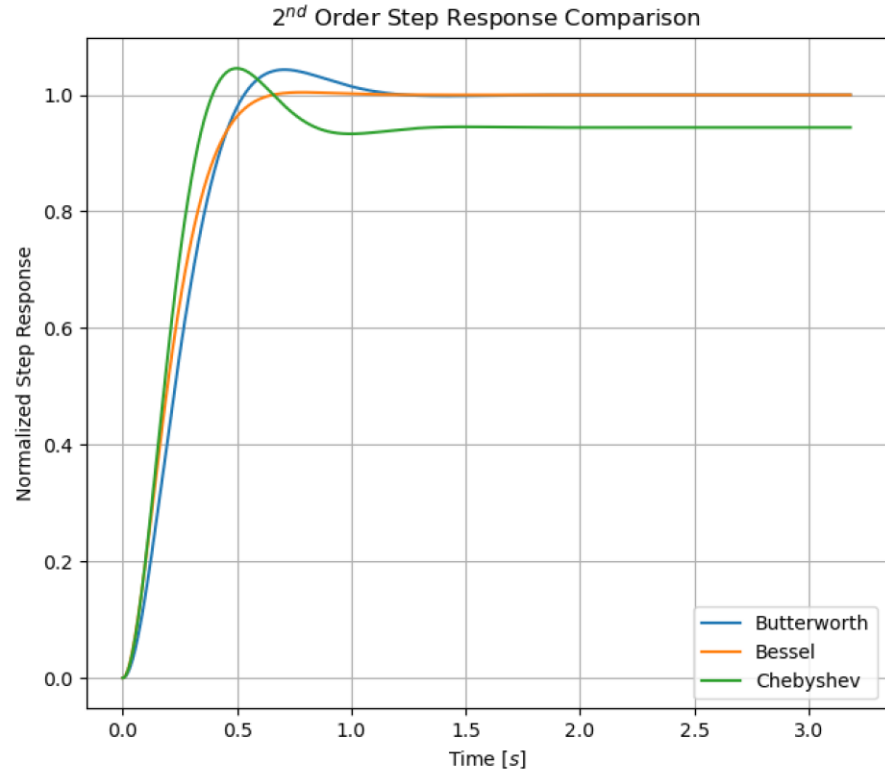
# Step Response Comparison

- The Chebyshev trades its sharp transition and wide passband in the frequency domain for significant ringing in the time domain
- The Bessel filter exhibits almost no overshoot or ringing, and has a slower rise time ( $t_r$ )
- The Butterworth filter constitutes the middle ground of the three in both the frequency and the time domain, with moderate peaking (frequency domain) and ringing (time domain)




# Filter Performance Comparison

Type	$f_{3dB}/f_c$	Poles	Rise Time (0 – 90%)	Overshoot (%)	0.1% Settling (s)	Stopband attenuation	
						2fc	10f <sub>c</sub>
<b>Bessel</b> (–3dB at f <sub>c</sub> )	1.0	2	0.4/f <sub>c</sub>	0.4	1.1/f <sub>c</sub>	10	36
	1.0	4	0.5/f <sub>c</sub>	0.8	1.2/f <sub>c</sub>	13	66
	1.0	6	0.6/f <sub>c</sub>	0.6	1.2/f <sub>c</sub>	14	92
<b>Butterworth</b> (–3dB at f <sub>c</sub> )	1.0	2	0.4/f <sub>c</sub>	4	1.7/f <sub>c</sub>	12	40
	1.0	4	0.6/f <sub>c</sub>	11	2.8/f <sub>c</sub>	24	80
	1.0	6	0.9/f <sub>c</sub>	14	3.9/f <sub>c</sub>	36	120
<b>Chebyshev</b> <b>0.5dB ripple</b> (–0.5dB at f <sub>c</sub> )	1.39	2	0.4/f <sub>c</sub>	1.1	1.6/f <sub>c</sub>	8	37
	1.09	4	0.7/f <sub>c</sub>	3.0	5.4/f <sub>c</sub>	31	89
	1.04	6	1.1/f <sub>c</sub>	5.9	10.4/f <sub>c</sub>	54	141
<b>Chebyshev 2dB</b> <b>ripple</b> (–2dB at f <sub>c</sub> )	1.07	2	0.4/f <sub>c</sub>	21	2.7/f <sub>c</sub>	15	44
	1.02	4	0.7/f <sub>c</sub>	28	8.4/f <sub>c</sub>	37	96
	1.01	6	1.1/f <sub>c</sub>	32	16.3/f <sub>c</sub>	60	148


# Passive LC Filters

## 2<sup>nd</sup> Order LC Lowpass

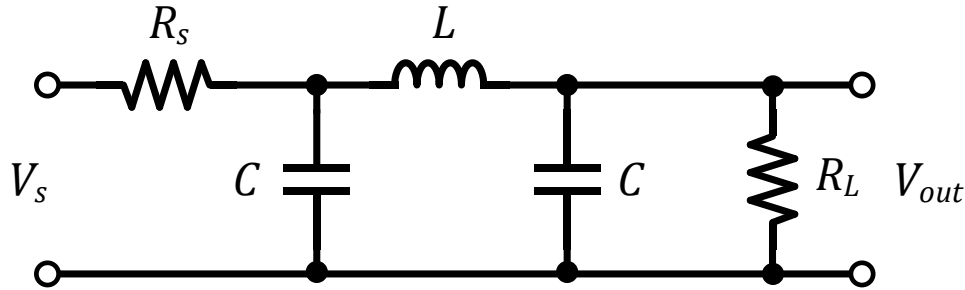

- LC filters are bulky and expensive, and aren't electrically tunable
- Further, they aren't able to achieve gain, but rather exhibit attenuation
- However, they tend to be the only viable option at high frequencies (i.e. above  $\sim 100\text{kHz}$ ), due to the limited bandwidth of opamps
- For low-frequency applications, active filters are the preferred approach


# Active Filters

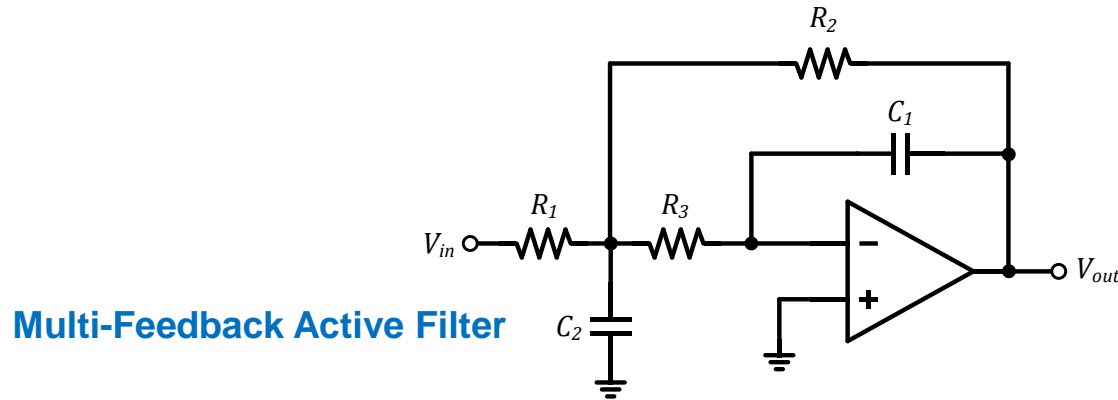

- We can synthesize RLC filter characteristics without inductors by using opamps
- Such filters are known as “active” filters, due to the presence of active devices (i.e. opamps)
- Active filters can be used to make lowpass, highpass, bandpass, and band-reject filters, with Butterworth, Bessel, and Chebyshev responses




# Sallen–Key Filter

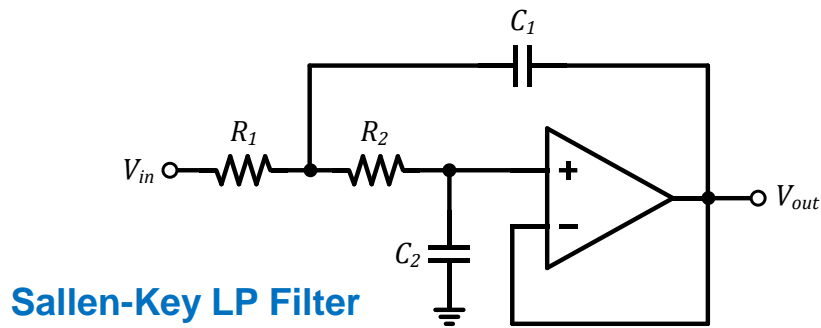

$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \frac{1}{C_1} \left( \frac{R_1 + R_2}{R_1 R_2} \right) + \frac{1}{R_1 R_2 C_1 C_2}}$$

- Similar to the cascade of two RC stages, with the bottom of  $C_1$  “bootstrapped” by the active follower
- The energy loss in the RC cascade is compensated by the opamp, raising the  $Q$  factor
- Similar configuration can be used to realize highpass and bandpass filters

# Sallen–Key Transfer Function

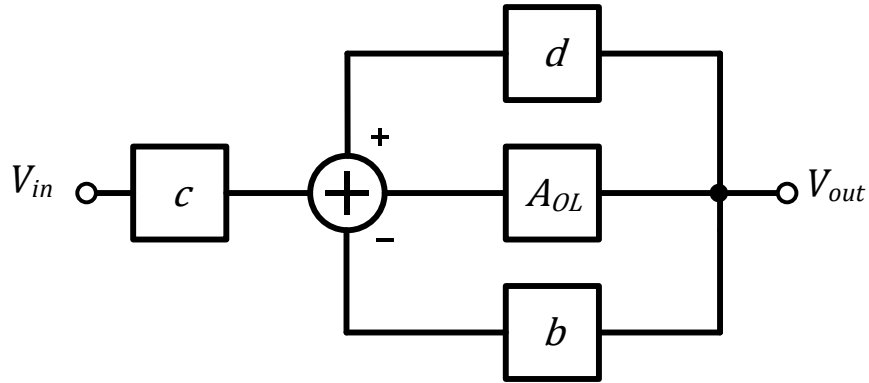


$$V_{out} = A_{OL}[cV_{in} + V_{out}(d - b)]$$

$$A_{OL} \rightarrow \infty$$

$$\frac{V_{out}}{V_{in}} = \frac{c}{b - d}$$

- Positive feedback allows the realization of higher  $Q$  factors than were possible with a passive filter, and since  $b > d$  the *net* feedback is still negative
- $c$  and  $d$  can be determined via circuit analysis, using the same techniques used for standard feedback structures (i.e. inverting, non-inverting, etc)

# Sallen–Key Transfer Function

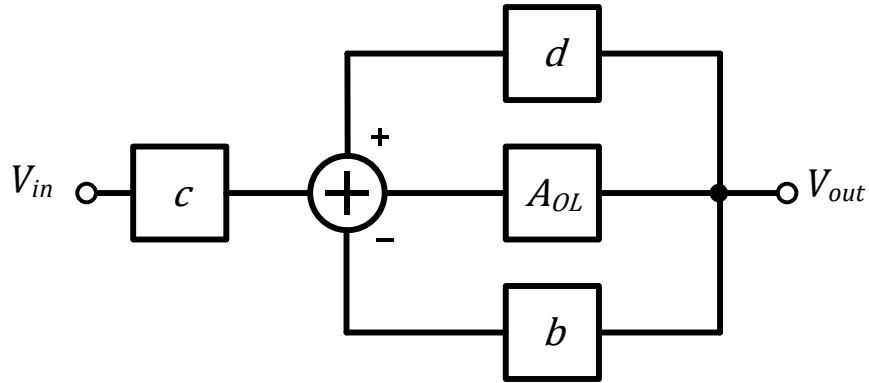

$$V_{out} = A_{OL}[cV_{in} + V_{out}(d - b)]$$

$$A_{OL} \rightarrow \infty$$

$$\frac{V_{out}}{V_{in}} = \frac{c}{b - d}$$

$$b = 1$$

$$c = \frac{1}{s^2 C_1 C_2 R_1 R_2 + s(R_1 C_2 + R_2 C_1 + R_1 C_1) + 1}$$

$$d = \frac{s C_1 R_1}{s^2 C_1 C_2 R_1 R_2 + s(R_1 C_2 + R_2 C_1 + R_1 C_1) + 1}$$



$$\frac{V_{out}}{V_{in}} = \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \frac{1}{C_1} \left( \frac{R_1 + R_2}{R_1 R_2} \right) + \frac{1}{R_1 R_2 C_1 C_2}}$$

# Sallen–Key Transfer Function (2)


- The transfer function as derived using circuit analysis can be cast in the standard form to determine  $\omega_0$  and  $Q$
- Component values  $R_1$ ,  $R_2$ ,  $C_1$ , and  $C_2$  are selected to achieve a desired response (e.g. Butterworth, Chebyshev, etc.)
- Analysis of Sallen–Key highpass and bandpass structures is the same, with the exception that the impedances are different

$$\begin{aligned}\frac{V_{out}}{V_{in}} &= \frac{\frac{1}{R_1 R_2 C_1 C_2}}{s^2 + s \frac{1}{C_1} \left( \frac{R_1 + R_2}{R_1 R_2} \right) + \frac{1}{R_1 R_2 C_1 C_2}} \\ &= \frac{\omega_0^2}{s^2 + 2\zeta \omega_0 s + \omega_0^2}\end{aligned}$$

$$\begin{aligned}\omega_0 &= \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \\ Q &= \frac{\omega_0}{2\zeta \omega_0} = \frac{1}{C_1} \frac{1}{\sqrt{R_1 R_2 C_1 C_2}} \left( \frac{R_1 + R_2}{R_1 R_2} \right)\end{aligned}$$
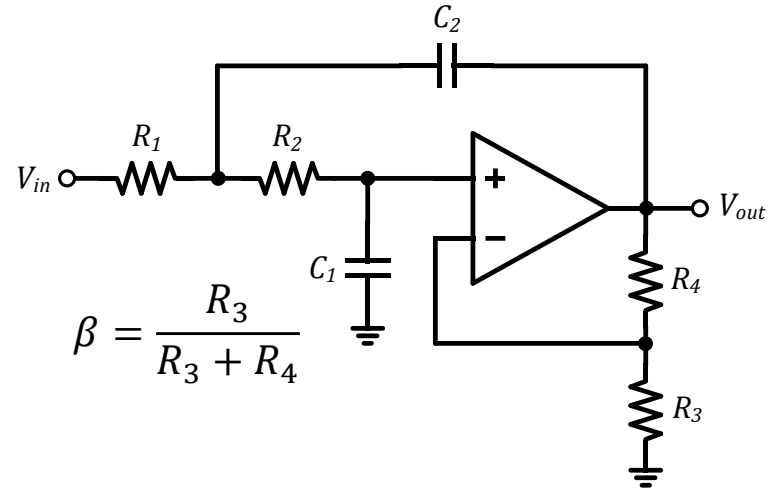
# Sallen–Key Filter Design

- The design process for active filters can be challenging to carry out manually, but second-order structures can be constructed easily if we make certain assumptions
- Component values are determined based on the desired response
- *Caveat:* Here the DC gain is coupled to its response type, which may be unacceptable if a particular DC gain is needed (e.g. unity)



$$\beta = \frac{R_3}{R_3 + R_4}$$

$$C_1 = C_2 = C_{nom}$$

$$R_1 = R_2$$

# Sallen–Key Design Process

- To simplify the design procedure, let  $C_1 = C_2$  and  $R_1 = R_2$
- Solving for the transfer function gives


$$\frac{V_{out}}{V_{in}} = \frac{1}{\beta} \frac{1/R_1^2 C_1^2}{s^2 + \frac{s}{R_1 C_1} \left(3 - \frac{1}{\beta}\right) + \frac{1}{R_1^2 C_1^2}} = K \frac{\omega_0^2}{s^2 + 2\zeta\omega_0 s + \omega_0^2}$$

- Which results in expressions for  $\omega_0$  and  $Q$ :

$$\omega_0 = \frac{1}{R_1 C_1} \qquad Q = 1/(3 - 1/\beta)$$

- To achieve a certain response (i.e. Butterworth, Chebyshev, etc.), we can select values for  $\omega_0$  and  $Q$  and solve for the component values
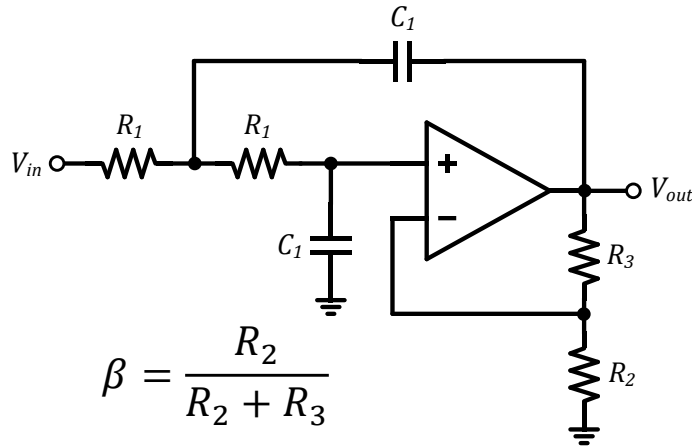
# 2<sup>nd</sup> Order Butterworth Design



$$\beta = \frac{R_2}{R_2 + R_3}$$

$$\omega_0 = 2\pi \cdot 5kHz$$

$$\omega_0 = \frac{1}{R_1 C_1} \quad Q = 1/(3 - 1/\beta)$$

- Choose  $C_1 = 10nF$  and solve for  $R_1$ :

$$R_1 = \frac{1}{\omega_0 C_1} \approx 15.9k\Omega$$

- For a Butterworth response, we need  $Q = 1/\sqrt{2}$ , which leads to

$$\beta = \frac{1}{3 - \sqrt{2}} \approx 0.63$$

- Setting  $R_2 = 10k\Omega$  results in  $R_3 \approx 5.86k\Omega$ , which gives us a gain of  $\sim 4dB$

# Frequency Scaling Factor


- To achieve other types of responses (i.e. Bessel or Chebyshev), we need to scale  $\omega_0$  so the filter provides a given attenuation at  $\omega_c$
- A Butterworth filter exhibits 3dB attenuation at  $\omega_0$ , so  $\omega_0 = \omega_c$
- For a Bessel Filter, the 3dB frequency occurs at a frequency *lower than*  $\omega_0$ , so we need to scale  $\omega_0$  in our design equation(s)
- Similarly, for a Chebyshev filter, a *frequency scaling factor* needs to be applied to  $\omega_0$  to obtain the appropriate attenuation (e.g. 0.5dB) at  $\omega_c$
- To do this, we merely replace  $\omega_0$  in our design equations with the relation

$$\omega_0 = c_n \omega_c$$

- The frequency scaling factor  $c_n$  is always greater than 1 and depends on the filter order



# 2<sup>nd</sup> Order Bessel Design

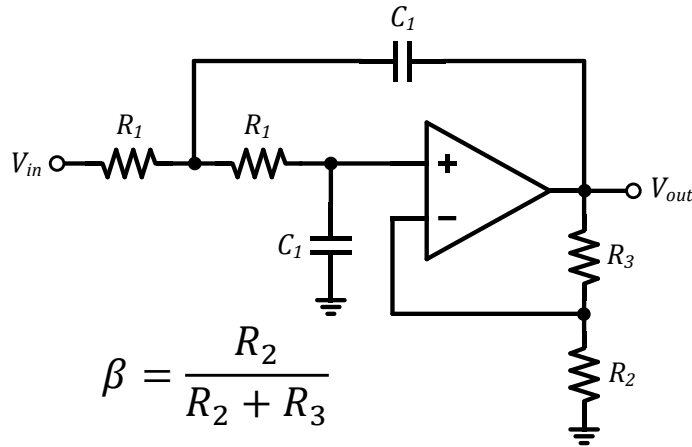

$$\omega_c = 2\pi \cdot 5kHz = \omega_0/c_n$$

$$\omega_c = \frac{1}{c_n R_1 C_1} \quad Q = 1/(3 - 1/\beta)$$

- For a second order Bessel,  $\omega_c \approx 1.272$
- Choose  $C_1 = 10\text{nF}$  and solve for  $R_1$ :

$$R_1 = \frac{1}{\omega_c C_1} \approx 20.2k\Omega$$

- For a Bessel response, we need  $Q = 1/\sqrt{3}$ , which leads to

$$\beta = \frac{1}{3 - \sqrt{3}} \approx 0.789$$

- Setting  $R_2 = 10k\Omega$  results in  $R_3 \approx 2.68k\Omega$ , giving a gain of  $\sim 2.06\text{dB}$

# Generalized Design Approach

- Depending on the application, the dependence of the filter response on closed-loop gain may be unacceptable
- So, although the previous design procedure is intuitive and simple, it may not be ideal
- A generalized design approach for low-pass filters is presented by James Karki of Texas Instruments here: [Active Low-Pass Filter Design](http://www.ti.com/lit/an/sloa049b/sloa049b.pdf?ts=1589465107385)
- This approach utilizes ratios of component values to achieve a desired response with arbitrary gain, including a gain of 1
- The basic approach is
  1. Choose ratios  $m$  and  $n$  to achieve the desired value of  $Q$ , and
  2. Select component values to achieve the target value of  $f_c$

Source: SLOA049B: Active Low-Pass Filter Design. Texas Instruments, September 2002. <http://www.ti.com/lit/an/sloa049b/sloa049b.pdf?ts=1589465107385>. Accessed 14 May 2020.

# 2<sup>nd</sup> Order Butterworth

- Defining parameters  $m$ ,  $n$ , and  $\tau$  as


$$m = \frac{R_1}{R_2} \quad n = \frac{C_1}{C_2} \quad \tau = R_2 C_2$$

- The 2-pole filter section has a cutoff frequency

$$f_c = \frac{1}{2\pi\tau\sqrt{mn}}$$

- And a  $Q$  given by
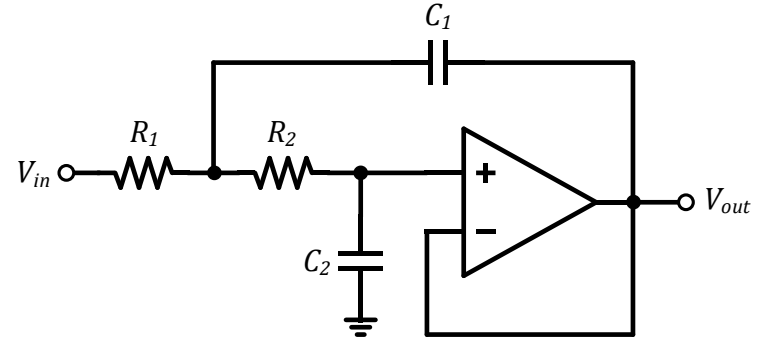
$$Q = \frac{\sqrt{mn}}{1 + m + mn(1 - K)}$$




$$Q = \frac{1}{\sqrt{2}}$$

$$f_c = 1\text{kHz}$$

$n$	$m$	$C_2$	$C_1$	$R_1$	$R_2$
3.3	0.229	0.01uF	0.033uF	4.22k	18.2k

# Higher Order Filters

## 4<sup>th</sup> Order Sallen-Key

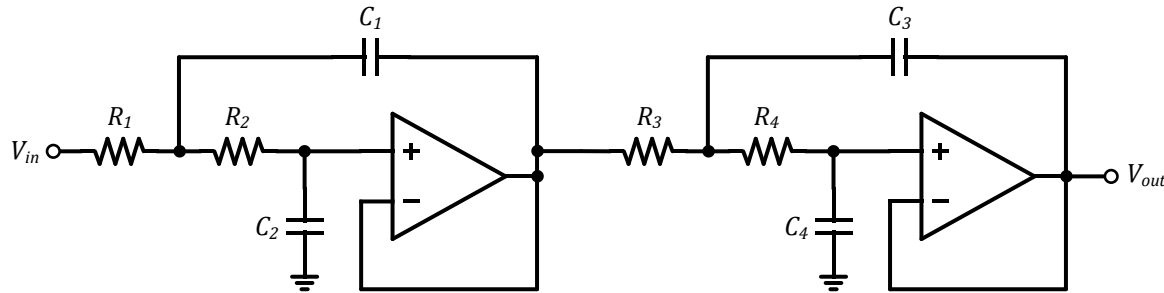

- Higher order and bandpass filters are typically constructed as cascades of 1<sup>st</sup> and 2<sup>nd</sup> order stages
- To realize the desired response,  $\omega_c$  and  $Q$  for each stage need to be modified from the values used in a second-order design
- For higher order filters, it is generally *much* easier to use a table-based approach or a filter design tool ([TI Filter Design Tool](#))