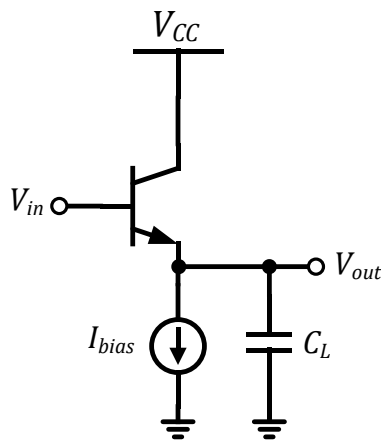


EE 538 Spring 2020
Analog Circuits for Sensor Systems
University of Washington Electrical & Computer Engineering

Instructor: Jason Silver
Practice Midterm

Please show your work.

Problem 1: Emitter-follower analysis




For the following, $V_{CC} = 5V$, $V_{IN} = 1V$, $I_{bias} = 1mA$, $C_L = 30pF$, and $I_S = 10^{-16}A$.

- Calculate the DC value of V_{out} . For this step, assume $V_A = \infty$.
- Calculate the small-signal DC gain (v_{out}/v_{in}) if $V_A = 100V$.
- Calculate the small-signal output resistance of the emitter follower if $V_A = 100V$.
- Calculate the transit frequency (f_T) of the emitter follower.
- Suppose we replace the BJT with a MOSFET with $V_{GS} - V_{TH} = 0.25V$ to construct a source follower. Ignoring r_o of the MOSFET, what is the new transit frequency?

a.
$$V_{BE} = V_T \ln(I_C / I_S)$$

$$\begin{aligned} V_{out,DC} &= V_{in,DC} - V_{BE} \\ &= 1V - V_T \ln(I_C / I_S) \approx \boxed{225mV} \end{aligned}$$

b. Small-signal model :

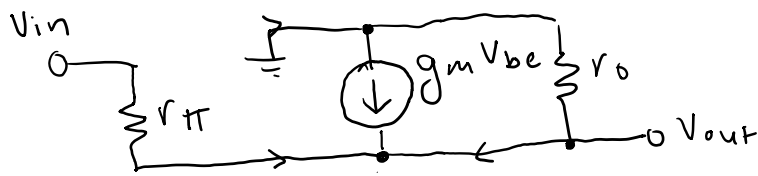

$$\begin{aligned} r_{\pi} &= \beta / g_m \\ r_o &= V_A / I_c \\ g_m &= I_c / V_T \end{aligned}$$

$$\frac{v_{in} - v_{out}}{r_{\pi}} + g_m (v_{in} - v_{out}) - v_{out} / r_o = 0$$

$$v_{in} \left(\frac{1}{r_{\pi}} + g_m \right) = v_{out} \left(\frac{1}{r_{\pi}} + g_m + \frac{1}{r_o} \right)$$

$$r_{\pi} = \beta / g_m \Rightarrow g_m v_{in} \left(1 + \frac{1}{\beta} \right) = v_{out} \left(g_m \left(1 + \frac{1}{\beta} \right) + \frac{1}{r_o} \right)$$


$$\frac{v_{out}}{v_{in}} = \frac{g_m \left(1 + \frac{1}{\beta} \right)}{g_m \left(1 + \frac{1}{\beta} \right) + 1/r_o}$$

$$= \frac{g_m \left(1 + \frac{1}{\beta} \right) r_o}{g_m \left(1 + \frac{1}{\beta} \right) r_o + 1}$$

assuming β is "large",

$$A_{v,DC} = \frac{g_m r_o}{g_m r_o + 1} = 0.997 \text{ V/V}$$

c.

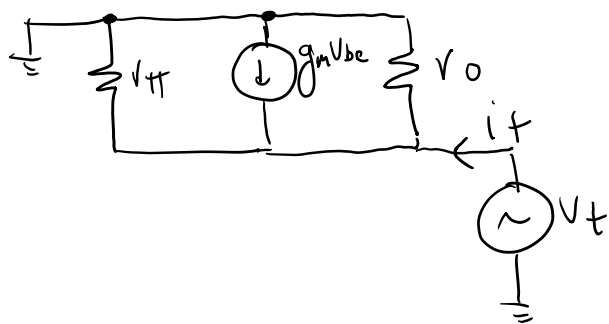

$$i_t = \frac{V_t}{r_o} + g_m V_t + \frac{V_t}{r_{\pi}}$$

$$Z_{out} = \frac{V_t}{i_t} = \frac{1}{\frac{1}{r_o} + g_m + \frac{1}{r_{\pi}}} \approx \frac{1}{g_m}$$

$$d. A_v(s) = \frac{g_m r_o \parallel C_L}{g_m r_o \parallel C_L + 1} = \frac{g_m r_o}{g_m r_o + s C_L r_o + 1}$$

$$f_T : g_m r_o + s_0 C_L r_o + 1 = 0$$


$$s_0 C_L r_o = -1 - g_m r_o$$

$$s_0 = \frac{-1 - g_m r_o}{C_L r_o} \approx -\frac{g_m}{C_L}$$

$$f_T = \frac{|s_0|}{2\pi} = \frac{g_m}{2\pi C_L} \approx 205 \text{ MHz}$$

$$e. g_m = \frac{2I_D}{V_{ov}} = 8 \text{ mS}, \quad f_T = \frac{g_m}{2\pi C_L} \approx \boxed{42 \text{ MHz}}$$

Problem 2: Filter analysis and design

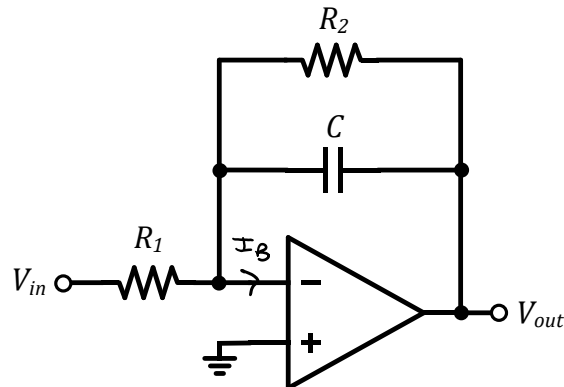

Assume the opamp has infinite gain and bandwidth, with input bias current $I_B = 1\text{nA}$.

- Ignoring bias current, derive an expression for the closed-loop transfer function of the filter.
- Design the filter (choose R_1 , R_2 , and C) to have a DC gain of 20dB and a 0.1% settling time of $10\mu\text{s}$.
- Still ignoring bias current, derive an expression for the closed-loop step response. Sketch the response for an input step of 0 to 1V and label all relevant times/voltages.
- Re-sketch the closed-loop step response, accounting for the effect of input bias current.
- Modify the design to reduce/eliminate the effect of the input bias current.

$$a. \quad \frac{V_{out}}{V_{in}} = \frac{-R_2 \parallel \frac{1}{sC}}{R_1} = \boxed{-\frac{R_2}{R_1} \cdot \frac{1}{s(R_2 + 1)}}$$

$$b. \quad \tau_{CL} = CR_2; \quad \ln(0.001) \times \tau_{CL} = 10\mu\text{s}$$

$$\tau_{CL} = 10\mu\text{s} / 6.9$$

$$\approx 1.45\mu\text{s} = CR_2$$


$$\text{let } \boxed{C = 10\text{pF}} \Rightarrow \boxed{R_2 = 145\text{k}\Omega}$$

$$R_1 = R_2 / 10 = \boxed{14.5\text{k}\Omega}$$

Many combinations possible

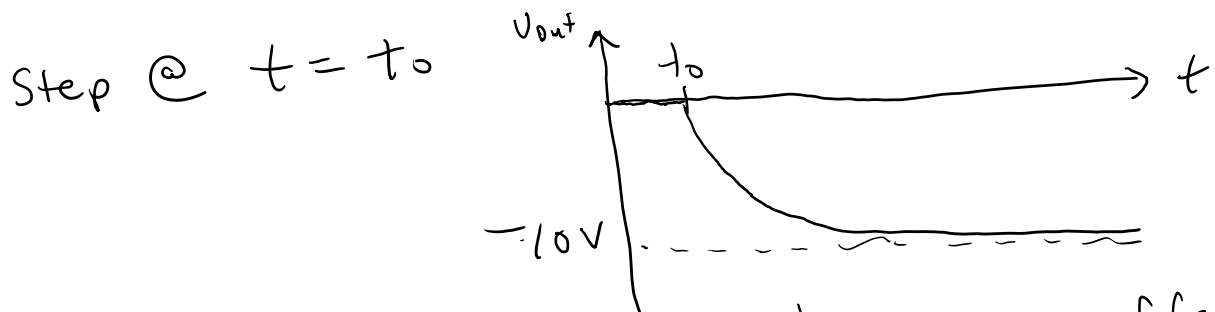c. $V_{in} = V_1 u(t)$


$$V_{out} = -V_1 u(t) \left(1 - e^{-t/\tau_{cc}}\right) \cdot \frac{R_2}{R_1}$$



d. With bias current, we have an offset

$$V_{out,os} = 0V + I_B \cdot R_2$$

for $R_2 = 1nA$, $V_{out,os} = 145\mu V$

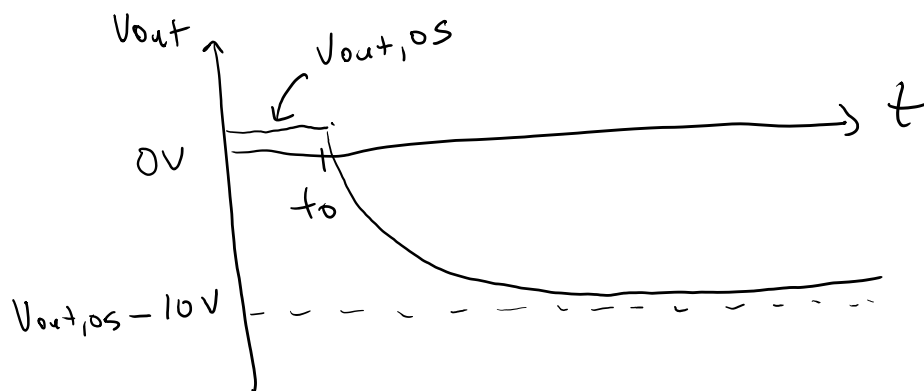

e. We could decrease R_1, R_2 to reduce the offset. E.g. $R_2 = 14.5k\Omega$, $R_1 = 1.45k\Omega$
 $C = 100pF$

This would reduce the offset to $14.5\mu V$

Problem 3. Opamp circuit design

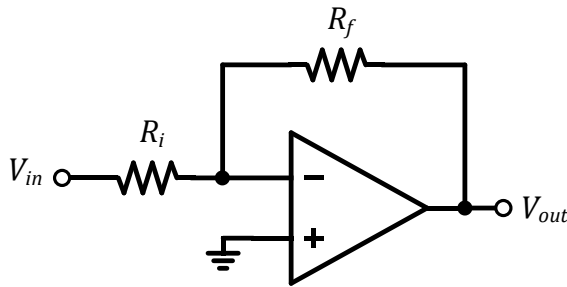


Figure 3a. Inverting amplifier

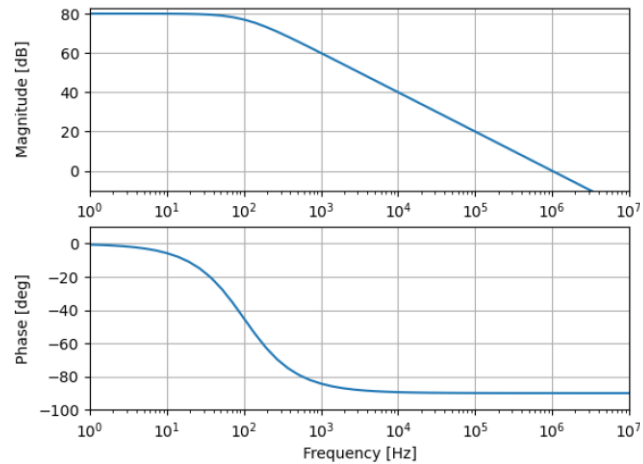


Figure 3b. Opamp open-loop frequency response

Assume ideal input/output resistances (R_{in} and R_o) for the opamp. Let $R_f = 10R_{in}$.

- Determine the gain and the 3dB frequency of the closed loop transfer function.
- Calculate the closed-loop gain error at DC and 100Hz.
- Suppose you want to use this amplifier to amplify the voltage of a sensor with an equivalent source resistance of 1k Ω . Determine the values of R_i and R_f to achieve a DC gain of 10V/V and less than 0.1% input attenuation due to loading (*you can ignore finite gain for this step*).
- Based on your answer to part c), is this a good choice of circuit for the application? How could it be improved?

a. $80 \text{ dB} \Rightarrow 10^4 \text{ V/V} = A_o$; $\beta = R_i / (R_i + R_f) = \frac{1}{11}$

$$\frac{V_{out}}{V_{in}} = \frac{-(1-\beta) A_o}{1 + \beta A_o} = \frac{-10}{11} \cdot \frac{A_o}{1 + A_o/11} = \frac{-10 A_o}{11 + A_o}$$

$$= \boxed{-9.989 \text{ V/V}}$$


$$f_{3dB} \approx \beta f_T \approx \boxed{91 \text{ kHz}}$$

$$b. A_{OL}(f=0) = 10^4 V/V$$

$$A_{OL}(f=100\text{Hz}) = 10^4 V/V / \sqrt{2} \approx 7071 V/V$$

$$\text{DC: } \frac{10 - 9.989}{10} = \boxed{0.11\%}; \quad 100\text{Hz: } \frac{10 \cdot A_{OL}(100)}{1 + A_{OL}(100)} \approx \boxed{0.16\%}$$
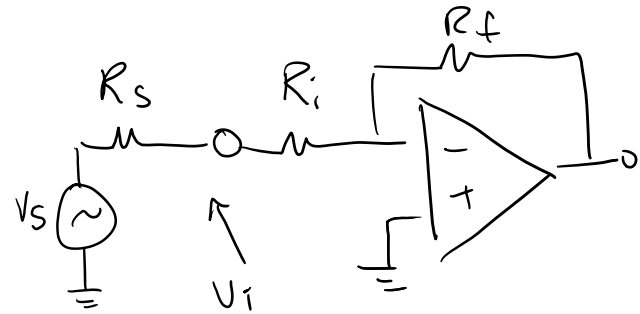
$$c. R_{in} = R_i; \quad R_f = 10 \cdot R_i$$



$$V_i = \frac{R_i}{R_s + R_i} V_s = 0.999 V_s$$

$$\frac{R_i}{R_s + R_i} = 0.999$$

$$0.001 R_i = 0.999 R_s$$

$$\boxed{R_i = 999 k\Omega}$$

$$\boxed{R_f = 9.99 M\Omega}$$

d. $R_i \approx 1 M\Omega$ is quite large. The input bias current of the opamp flowing through R_i will result in a large offset voltage. R_i will also generate a substantial amount of noise.

\Rightarrow Use a non-inverting stage instead.