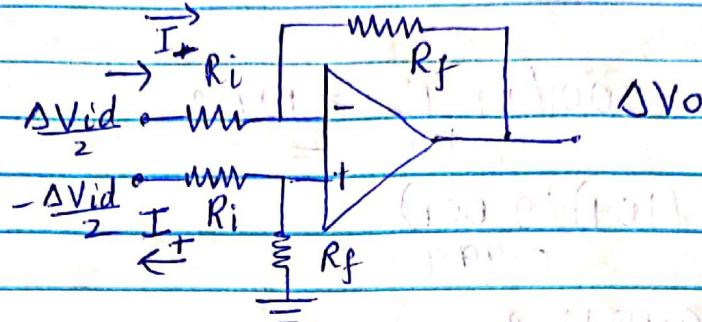


# HW 5

①

$$R_f = 10k\Omega, R_i = 100\Omega$$

a)



$$Z_{in} = \frac{\Delta V_{id}}{I_o - I_i} \quad \text{--- (1)}$$

$$V_- = V_+ = -\frac{\Delta V_{id}}{2} \left( \frac{R_f}{R_i + R_f} \right)$$

$$\frac{I_o - \Delta V_{id}}{2} = V_- = \frac{\Delta V_{id}}{2} \left[ 1 + \frac{R_f}{R_i + R_f} \right] \quad \text{--- (2)}$$

$$\frac{I_i + \frac{\Delta V_{id}}{2}}{R_i} + V_+ = \frac{\Delta V_{id}}{2} \left[ 1 - \frac{R_f}{R_i + R_f} \right] \quad \text{--- (3)}$$

from (1)


$$Z_{in} = \Delta V_{id} \cdot R_i$$

$$\Delta V_{id} = \frac{R_f}{2} \left( \frac{R_f}{R_i + R_f} \right)$$

$$Z_{in} = R_i \left( 1 + \frac{R_f}{R_i} \right)$$

$$\Rightarrow Z_{in} = R_i \left( 1 + \frac{1}{A_{cl}} \right)$$

$$A_{cl} = \frac{R_f}{R_i}$$

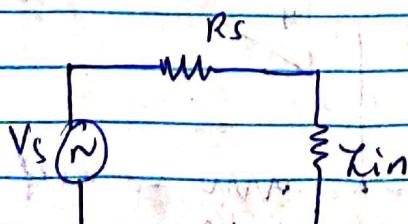

For 0.1% Attenuation

$$\frac{Z_{in}}{R_s + Z_{in}} = 0.999$$

$$R_s (0.999) = Z_{in} (0.001)$$

$$A_{CL} = \frac{R_f}{R_i} = 10$$

$$R_s =$$

$$Z_{in} = 100 \left(1 + \frac{1}{100}\right) = 101 \Omega$$

$$\Rightarrow R_s = \frac{(101)(0.001)}{0.999}$$

$$R_s = \underline{0.1011 \Omega}$$

Problem

(2)

$$A_{DC} = 120 \text{ dB}$$

$$R_G = 100 \Omega$$

$$f_T = 1 \text{ MHz}$$

$$R_1 = R_2 = 10 \text{ k}\Omega$$

$$R_{fp} = R_{fm} = 4.95 \text{ k}\Omega$$

$$t_{OL} = 0.1 \text{ s}$$

a)


$$V_{id} = V_{ip} - V_{im}$$

$$\Rightarrow V_{od} = V_{op} - V_{om}$$

$$A_{OL} = \frac{A_O}{1 + ST}$$

$$A_O = 10^6 \text{ V/V}$$
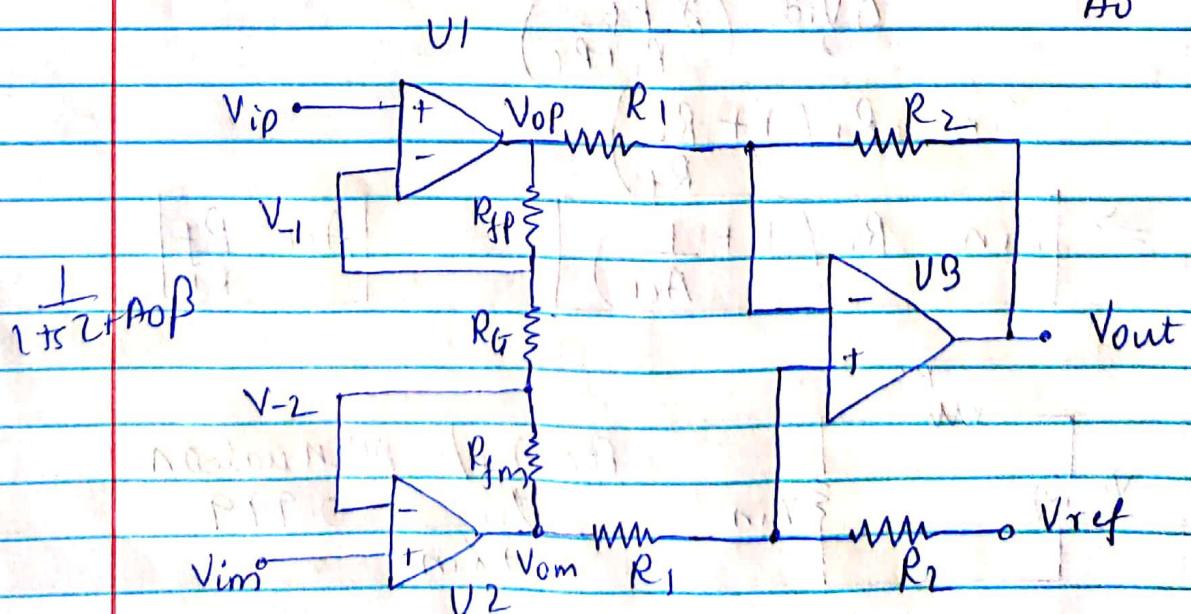
$$f_{3dB} = \frac{f_T}{A_O} = 1 \text{ Hz}$$



$$V_{-1} = V_{ip} - \frac{V_{op}}{AOL} \quad | \quad V_{-2} = V_{im} - \frac{V_{om}}{AOL}$$

$$I_G = \frac{V_{-1} - V_{-2}}{R_G} \quad \text{--- } ①$$

$$I_G = \frac{\left( V_{ip} - \frac{V_{op}}{AOL} \right) - \left( V_{im} - \frac{V_{om}}{AOL} \right)}{R_G}$$

$$I_G R_G = \left( V_{ip} - V_{im} \right) - \left( V_{op} - V_{om} \right) AOL \quad \text{--- } ②$$

$$\text{Also, } V_{op} - V_{om} = I_G (R_{fp} + R_G + R_{fm}) \quad \text{--- } ③$$

$$(V_{op} - V_{om}) = \frac{(R_{fp} + R_G + R_{fm})}{R_G} [V_{ip} - V_{im} - (V_{op} - V_{om}) AOL]$$

$$(V_{op} - V_{om}) \left[ 1 + AOL \left( 1 + \frac{R_{fp} + R_{fm}}{R_G} \right) \right] = (V_{ip} - V_{im}) \left( 1 + \frac{R_{fp} + R_{fm}}{R_G} \right)$$

$$\frac{V_{op} - V_{om}}{V_{ip} - V_{im}} = \frac{\left( 1 + R_{fp} + R_{fm} \right)}{1 + \left( 1 + \frac{R_{fp} + R_{fm}}{R_G} \right)}$$

$$= \frac{AO (R_G + R_{fp} + R_{fm})}{R_G AOL + \left( 1 + \frac{R_{fp} + R_{fm}}{R_G} \right) (R_G + R_{fp} + R_{fm})}$$

$$= \frac{(R_G + R_{fp} + R_{fm})}{R_G}$$

$$\frac{R_G + (R_G + R_{fp} + R_{fm})}{R_G AOL}$$

$\frac{V_{op} - V_{om}}{V_{ip} - V_{im}}$	$= \frac{AOL}{1 + \frac{R_G}{R_G + R_{fp} + R_{fm}} \cdot AOL}$	$\text{--- } ④$
---	---	-----------------

$$\frac{V_{out}}{V_{op} - V_{om}} = -\frac{R_2}{R_1} \cdot \frac{10K}{10K} = -1$$

$$\Rightarrow \boxed{\frac{V_{out}}{V_{in} - V_m} = \frac{A_{OL}}{1 + \frac{R_U}{R_G + R_{fp} + R_{gm}} \cdot A_{OL}}}$$

where  $\beta = \frac{R_U}{R_G + R_{fp} + R_{gm}}$

$$E) A_{OL} = \frac{A_0}{1 + \beta Z} \quad A_0 = 10^6 \text{ V/V}$$

$$\Rightarrow A_{OL} = \frac{-A_0}{1 + \beta A_0} = \frac{10^6}{1 + 10^2 \cdot 10^6} \quad \beta = 0.01$$

$$A_{DC, CL} = 99.99 \text{ V/V}$$

$$f_{3dB, CL} = (1 + \beta A_0) f_{3dB, OL} \\ = (1 + 10^2 \cdot 10^6) \frac{f_T}{A_0}$$

$$f_{3dB, CL} = (1 + 10^4) \frac{10^6}{10^6}$$

$$\boxed{f_{3dB, CL} = 10.001 \text{ kHz}}$$

b)

$$\text{Gain error} = \frac{G_{ideal} - G_{actual}}{G_{ideal}}$$

$$G_{ideal} = \left(1 + \frac{R_{fp} + R_{gm}}{R_U}\right) (-1)$$

$$G_{ideal} = -100 \text{ V/V}$$

$$\text{At } 100 \text{ Hz, } G_{actual} = \boxed{\frac{10^6}{1 + j(2\pi \times 100) + 10^4}}$$

$$= -99.79325 \text{ V/V}$$

$$\text{Gain error} = \frac{-100 + 99.79325}{-100}$$

$$= 0.20674\%$$

c) CMRR = ? Worst-case DC gain error = ?

$$\begin{aligned} \text{CMRR} &= \text{CMRR}_1 \cdot \text{CMRR}_2 \\ &= \frac{1 + (R_{fp} + R_{fm})}{R_G} \times \frac{A_{vd2} + 1}{M \times E} \\ &= \left(1 + \frac{9900}{100}\right) \times \frac{2}{4 \times 0.001} \end{aligned}$$

$$[\text{CMRR} = 93.9 \text{ dB}]$$

$$\Rightarrow A_{DC} = -\left(1 + \frac{R_{fp} + R_{fm}}{R_G}\right) \left(\frac{R_2}{R_1}\right)$$

$$A_{\text{ideal}} = -100 \text{ V/V}$$

w.c Resistor values:

$$R_{fp} = R_{fm} = 1.95K \times 0.999 = 1945.05\Omega$$

$$R_G = 100 / (1 + 0.001) = 100.1\Omega$$

$$R_2 = 10K / (1 - 0.001) = 9990\Omega$$

$$R_1 = 10K / (1 + 0.001) = 10010\Omega$$

$$A_{\text{worst-case}} = -\left(1 + \frac{R_{fp} + R_{fm}}{R_G}\right) \left(\frac{R_2}{R_1}\right)$$

$$= -\left(1 + \frac{9890.1}{100.1}\right) \left(\frac{9990K}{10010K}\right)$$

$$= -99.6 \text{ V/V}$$

$$[\text{w.c Gain error} = 0.4\%]$$

(d)

$$V_{OS, U1} = +100 \mu V$$

$$V_{OS, U2} = -100 \mu V$$

$$V_{out1} = \left(1 + \frac{R_f p + R_f m}{R_G}\right) (V_{OS, U1} - V_{OS, U2})$$

$$= 20 mV$$


$$V_{out} = -\frac{R_2}{R_1} (V_{OS, U3} + V_{out1}) + \left(1 + \frac{R_2}{R_1}\right) V_{OS, U3}$$

$$-250 \mu V \times 100 = -1 (V_{OS, U3} + 20 mV) + \left(1 + \frac{R_2}{R_1}\right) V_{OS, U3}$$

$$V_{OS, U3} = -5 mV$$

$$\Rightarrow V_{OS, U3} = -2.5 mV$$

Problem 1) Part B)

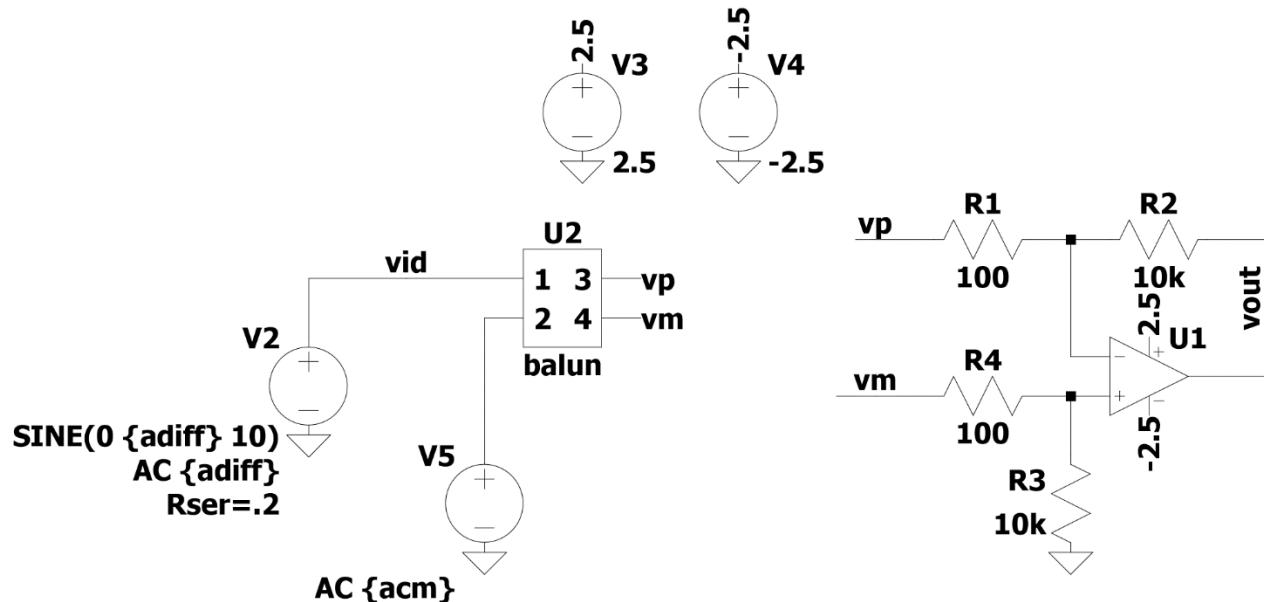

```
.param adiff = 1  
.param acm = 0  
.ac dec 100 1 100Meg
```

--- D:\OneDrive - UW\School\UDub\2020 Q3\EE 538\HW\HW 5\lspice\HW5\_1.asc ---

Fig 1) Schematic

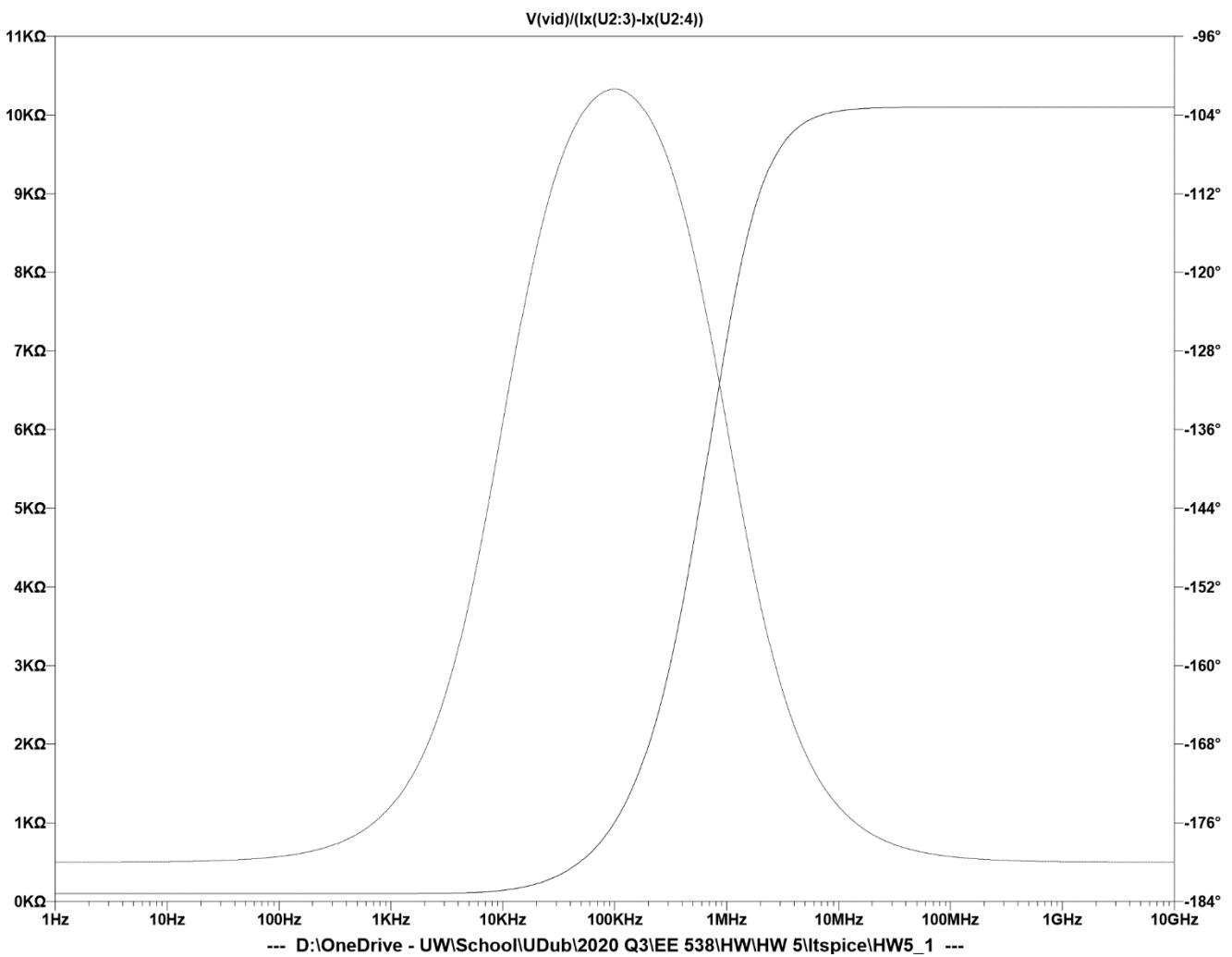


Fig 2) Zin vs Freq


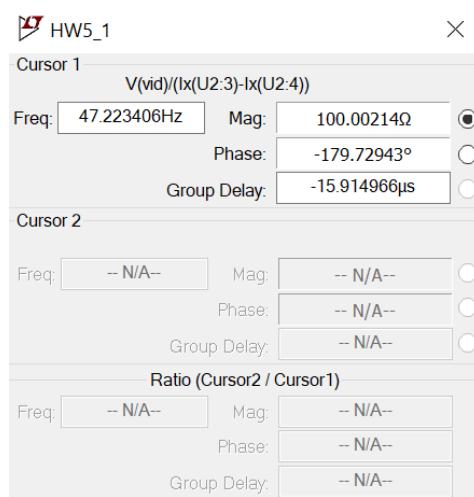


Fig 3) Zin value at low frequency


Problem 2) Part E)

1) DC Operating point

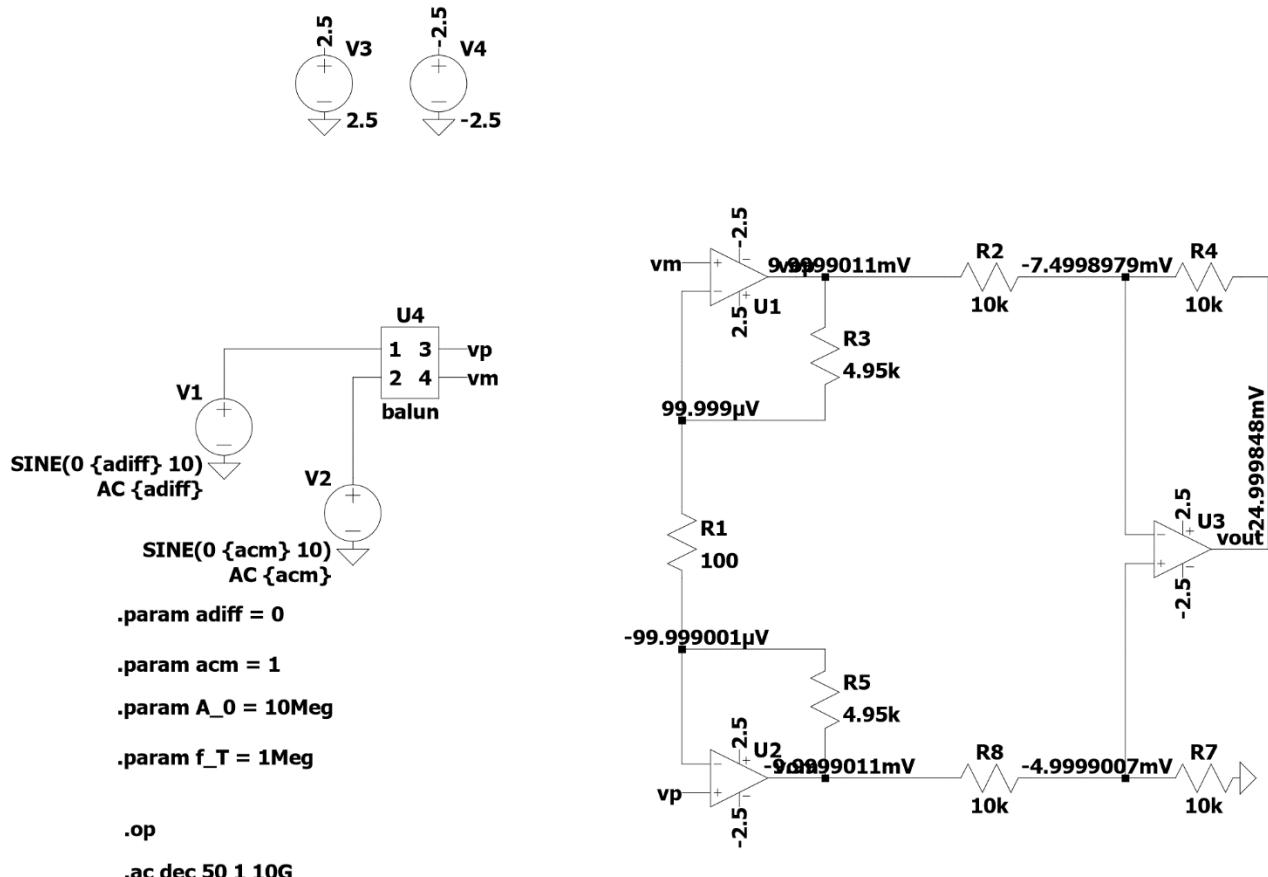

--- D:\OneDrive - UW\School\UDub\2020 Q3\EE 538\HW\HW 5\itspice\HW5\_2.asc ---

Fig 4) Schematic without resistor mismatch

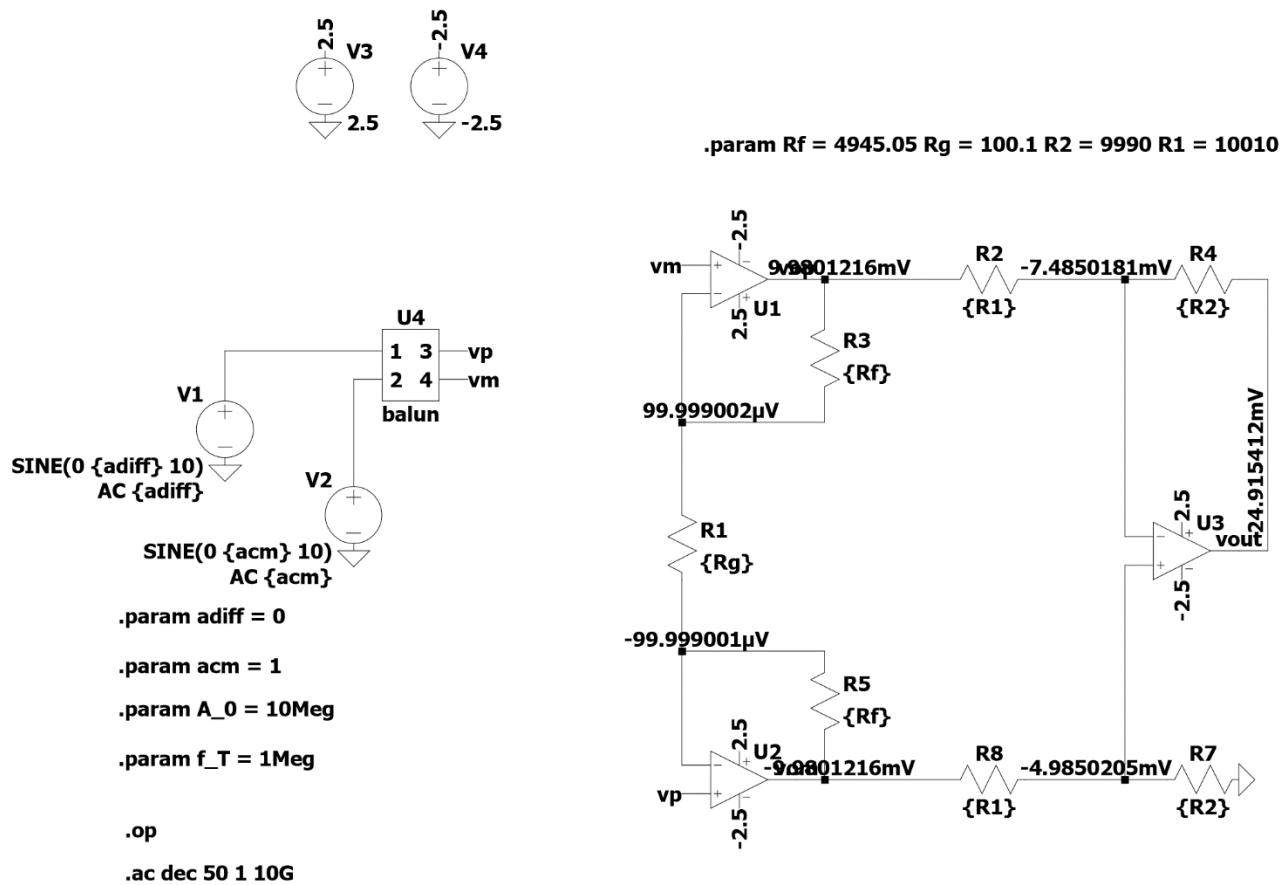

--- D:\OneDrive - UW\School\UDub\2020 Q3\EE 538\HW\HW 5\lspice\HW5\_2.asc ---

Fig 5) Schematic with resistor mismatch

Resistor mismatch causes an offset of about 85uV on  $V_{OUT}$

2) Gain error

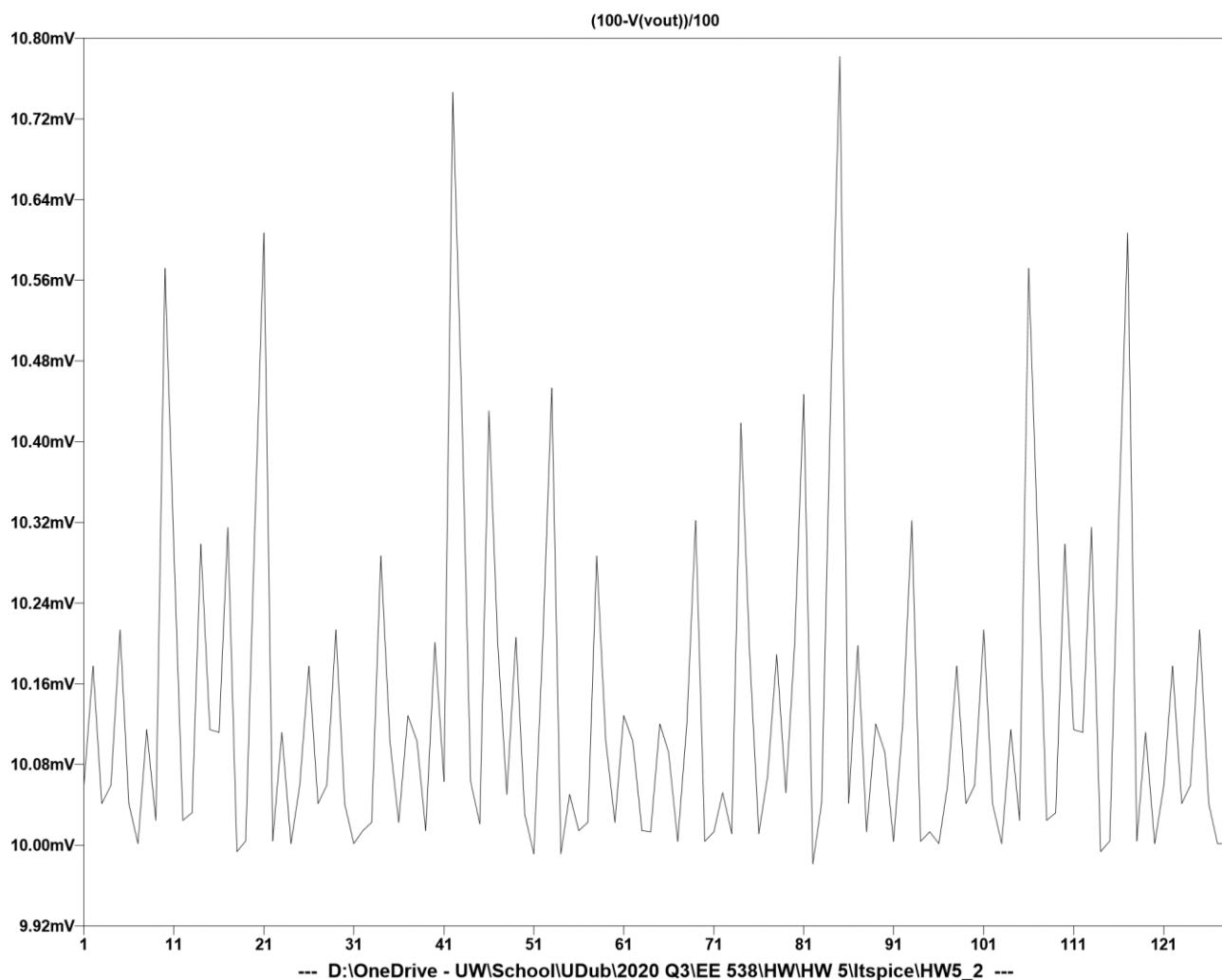


Fig 6) Gain error due to resistor mismatch

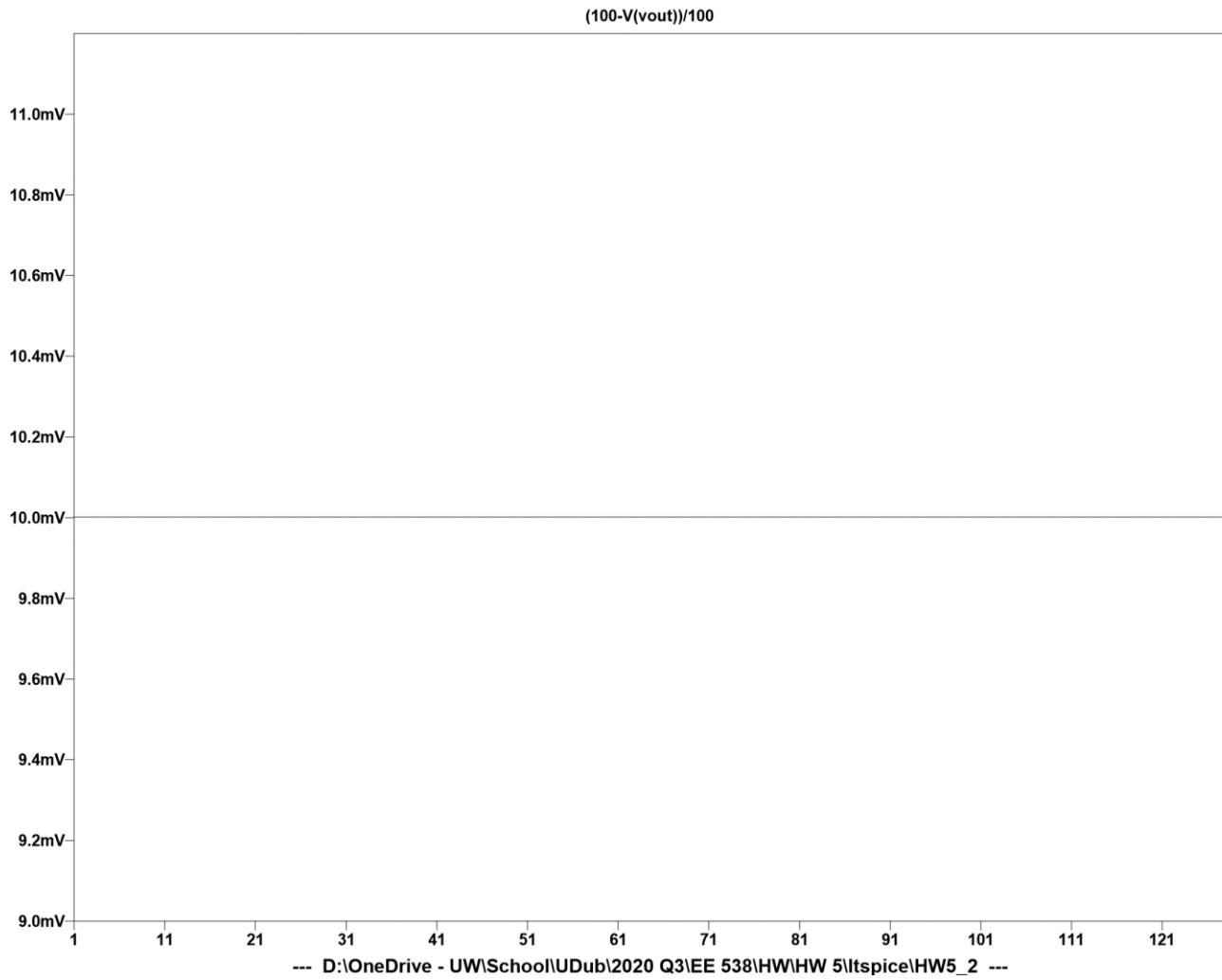


Fig 7) Gain error due to finite open loop gain of the Op-amp

From the plots, we can infer that gain error due to resistor mismatch is worse than the gain error due to finite open loop gain of the op-amp

### 3) Bode plots

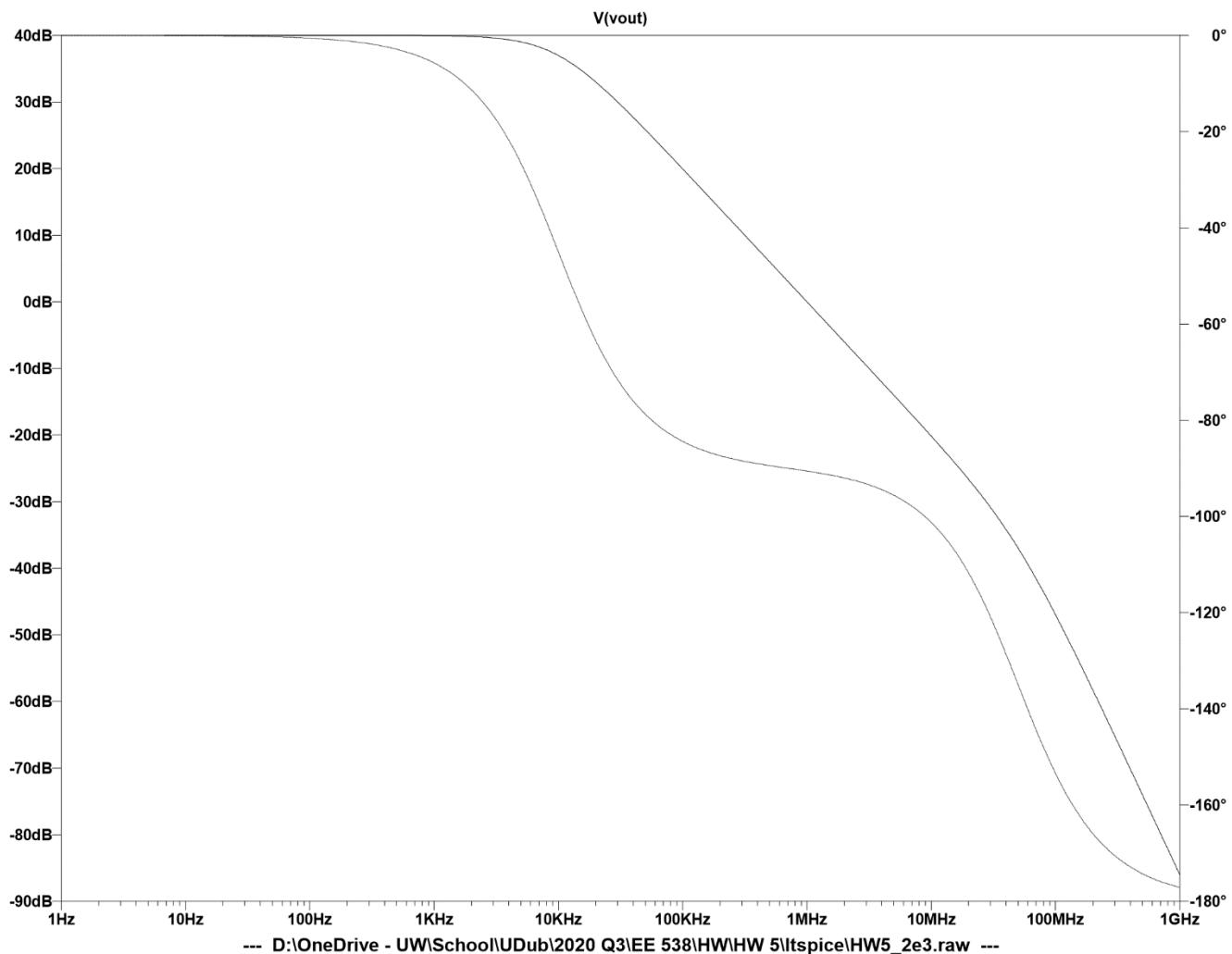


Fig 8) Closed loop differential gain (no resistor mismatch)

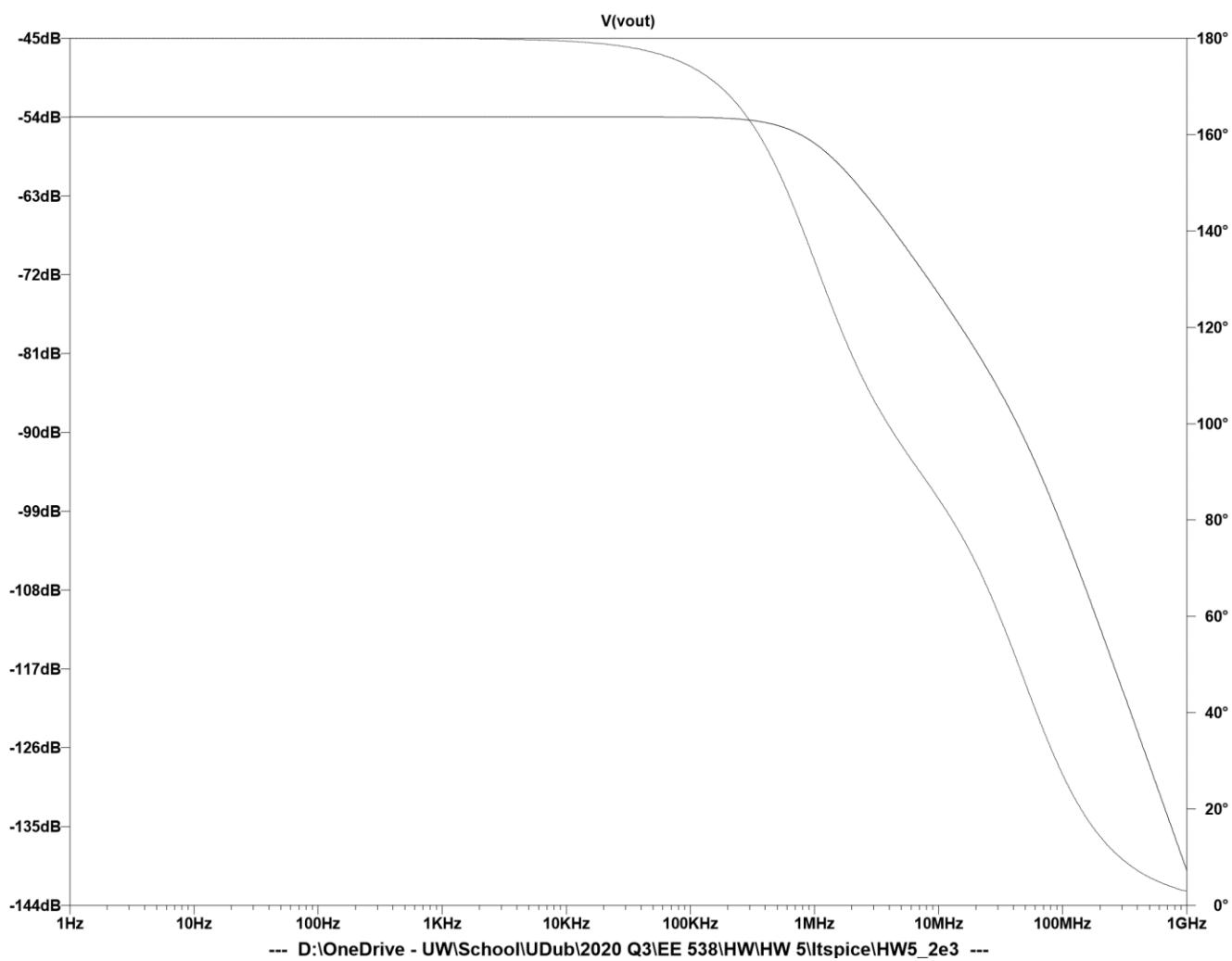


Fig 9s) Closed loop common mode gain (with resistor mismatch)