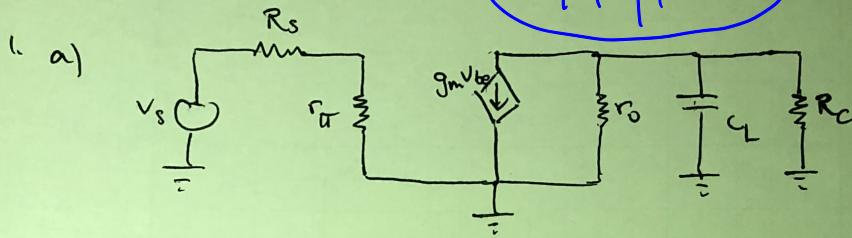


Problem 1

91 | 100

$\beta = 100$



$$V_T = 25 \text{ mV}$$

$$V_A \gg V_{CE} \rightarrow I_C \approx I_{CO}$$

$$R_{in} = R_B = \frac{\beta}{g_m} = \frac{\beta V_T}{I_{CO}} \approx \frac{\beta V_T}{I_C}$$

$$I_C = I_{SE} e^{\frac{V_{BE}}{V_T}}$$

$$I_c = I_{bias}$$

$$R_{in} = \frac{100 \cdot 25 \times 10^{-3}}{100 \cdot 10^{-6}} = 25 \cdot 10^3 = \boxed{25 \text{ k}\Omega} \quad I_C \approx I_E = 100 \mu\text{A}$$

$$I_C = \beta I_B = 100 \mu\text{A}$$

$$b.) \frac{V_{out}}{V_s} = \frac{V_{out}}{V_b} \cdot \frac{V_b}{V_s}$$

$$V_{out} = V_{out,DC} + \underbrace{Av V_{in}}_{V_{out}}$$

$$\frac{V_b}{V_s} = \frac{Z_{in}}{R_s + Z_{in}}$$

$$V_{be} = V_b - 0.6 \text{ V} \xrightarrow{\text{large signal}} V_{be} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.69 \text{ V}$$

$$\text{Find } \frac{V_{out}}{V_{in}} \text{ (small signal)}$$

$$O = g_m V_{be} + \frac{V_{out}}{r_o} + \frac{V_{out}}{Z_C} + \frac{V_{out}}{R_C}$$

$$O = g_m V_{be} + V_{out} \left(r_o \parallel Z_C \parallel R_C \right)^{-1} \rightarrow g_m V_{be} + V_{out} \left[\underbrace{\frac{r_o R_C}{r_o + R_C}}_{\alpha} \parallel Z_C \right]^{-1}$$

$$-g_m V_{be} = V_{out} \left[\frac{\alpha}{1 + s\alpha C} \right]^{-1}$$

$$\frac{V_{out}}{V_b} = -g_m \left[\frac{\alpha}{1 + s\alpha C} \right], \quad \alpha = \frac{r_o R_C}{r_o + R_C} \quad r_o \approx \frac{V_A}{I_C} = \frac{100 \text{ V}}{100 \mu\text{A}} = 10^8 \text{ }\Omega$$

$$\rightarrow \frac{V_{out}}{V_s} = -g_m \left[\frac{Z_{in}}{R_s + Z_{in}} \right] \left[\frac{\alpha}{1 + s\alpha C} \right]$$

$$V_{out,DC} =$$

$$\frac{V_{out,DC}}{V_{in}} = -g_m (R_C \parallel r_o) \approx -g_m R_C$$

$$c.) g_m = \frac{I_C}{V_T} = 0.004$$

$$DC \frac{V_{out}}{V_{in}}, \quad -g_m R_C = (0.004)(10,000) = -40 \text{ V/V}$$

c)

continued...

$$f_T = |s_0| = \frac{1}{\alpha C} = \frac{1}{\left(\frac{10^3 \cdot 10^8}{10^3 + 10^8}\right) 10 \text{ pF}} = 1 \times 10^8 \text{ Hz} = \boxed{100 \text{ MHz}}$$

this is f_{3dB} ,

but looking
for f_T

-5

Problem 2

a.) non-inverting

$$V_{out, \text{err}} = V_{os} \left(1 + \frac{R_f}{R_i} \right) + I_B R_f - \left(1 + \frac{R_f}{R_i} \right) I_B R_s$$

$$V_{out, \text{err}} = V_{os}(11) + 10R_i I_B - 11I_B R_s$$

$$V_{out, \text{err}} = (10^{-3})(11) + 10(-1nA)R_i - 11(-1nA)R_s$$

$$V_{out, \text{err}} = 11 \cdot 10^{-3} - 10 \cdot 10^{-9} R_i + 11 \cdot 10^{-9} R_s$$

b.) Given $R_s = 0$,

$$V_{out, \text{err}} = 11 \cdot 10^{-3} - 10 \cdot 10^{-9} R_i$$

$$R_i = 1.1 \cdot 10^6 \Omega = 1.1 M\Omega$$

$$R_f = 11 M\Omega$$

c.) Given $R_s = 1k$, $V_{os} = 0$

$$V_{out, \text{err}} = -10 \cdot 10^{-9} R_i + 11 \cdot 10^{-9} R_s \quad |_{R_s = 1k}$$

$$+ 10 \cdot 10^{-9} R_i = 11 \cdot 10^{-6}$$

$$R_i = \cancel{0.0009 \Omega} = \underline{0.9 m\Omega} \quad 1100 \Omega$$

$$R_f = \cancel{1 M\Omega} + \cancel{10,000 \Omega} \quad 11,000 \Omega$$

Problem 3

a.) non-inverting

$$\frac{V_{out}}{V_{in}} = \left[1 + \frac{R_2}{R_1} \right] \left[\frac{A\beta}{1 + A\beta} \right]$$

$$A_0 = 120 \text{ dB} = 10^6 \frac{V}{V}$$

$$\frac{1}{\beta} = 1 + \frac{R_f}{R_i} = 11$$

$$\beta = \frac{1}{11}$$

$$\frac{V_{out}}{V_{in}} = 11 \left[\frac{10^6 / 11}{1 + 10^6 / 11} \right]$$

$$= 10.9999 \quad \checkmark$$

$$f_T = \omega$$

$$f_{3dB} = \beta f_T = \frac{10}{11} = 909 \text{ kHz} \quad \checkmark$$

b.) $V_{out} = 100 \times 10^{-3} [u(t_{\frac{nT}{2}}) - u(t_{nT})]_{n=0,1,2,\dots,\infty} \left[1 + \frac{R_f}{R_i} \right] X$

~~$A_{CL} = \frac{A_0}{1 + s\tau + \beta A_0}$~~

$f_{3dB} = \frac{1 + \beta A_0}{2} \approx \frac{\beta A_0}{2}$


$\tau = \frac{A_0}{f_T} = 0.1$

$A_{CL} = \frac{A_0}{1 + 0.1s + \frac{A_0}{11}}$

$\tau_{CL} = \frac{\tau}{\beta A_0} = 9.09 \times 10^{-9}$

$= \frac{A_0}{1 + \frac{s}{10} + \frac{A_0}{11}}$

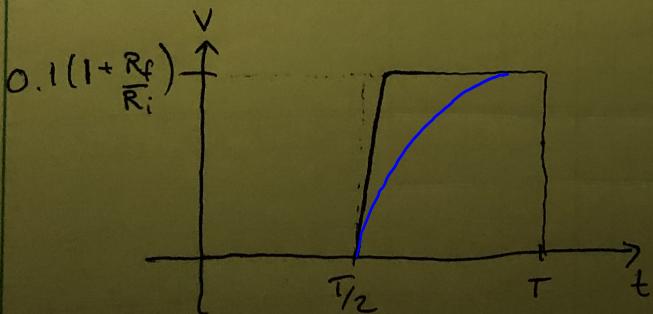$V_{out} = 0.1 \left[u(t_{\frac{nT}{2}}) - u(t_{nT}) \right]_{n=0,1,2,\dots,\infty} (1 - e^{-t/\tau_{CL}}) \left(1 + \frac{R_f}{R_i} \right)$



$\leftarrow \cancel{0.1(1 + R_f/R_i)} 0.1 \left(1 + \frac{10 R_i}{R_i} \right) = \boxed{1.1 V}$

Problem 3

c) $0.1\% \text{ settling} \rightarrow 6.9T = 6.9 \cdot 9.09 \times 10^{-9} = 6.27 \times 10^{-8}$

$$t_{\text{settle}} = \frac{1}{2f_{\text{clk}}}$$

$$T = \frac{1}{f}$$

$$f_{\text{clk}} = \frac{1}{2 \cdot 6.27 \times 10^{-8}} = 7.97 \times 10^6 \text{ Hz}$$

$$T = \frac{1}{7.97 \times 10^6 \text{ Hz}} = 1.254 \times 10^{-7} \text{ s} \times 2$$

- |

d) ideal gain = $0.1(11)$ $\frac{\text{V}}{\text{V}}$

$$\text{act. gain} = 0.1 \left(1 + \frac{R_f(0.999)}{R_i(1.001)} \right) \quad R_f = 10 R_i$$

$$= 1.098 \frac{\text{V}}{\text{V}}$$

$$\frac{\text{ideal} - \text{actual}}{\text{ideal}} = \frac{1.1 - 1.098}{1.1} = 0.18\% \text{ error}$$

Settling error? -3