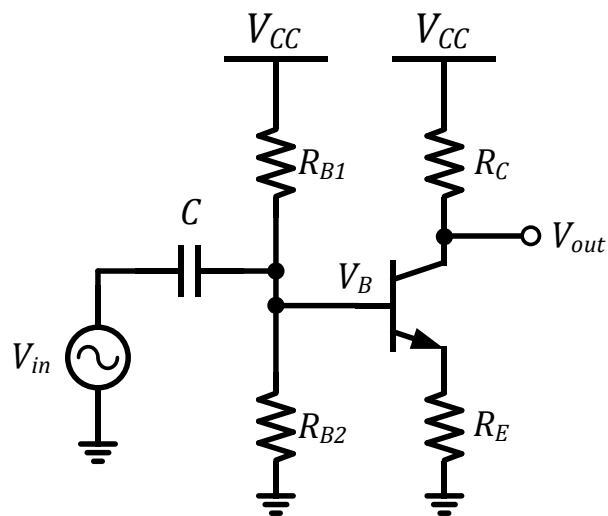


EE 538 Spring 2020
Analog Circuits for Sensor Systems
University of Washington Electrical & Computer Engineering

Instructor: Jason Silver
Homework #2 (40 points)
Due Saturday, April 18, Submit on Canvas

Please show your work.

Problem 1: Common-emitter amplifier



For the following, use the figure and the simplified NPN model from Section 2.1.1 in AoE. $V_{CC} = 5\text{V}$, $C = 1\mu\text{F}$, and $\beta = 100$. Use the *npn* Ltspice component for your simulations.

- Select values for R_{B1} and R_{B2} to achieve $V_B = 1\text{V}$ and a high-pass corner frequency (f_{3dB}) of 10Hz. You may ignore base current for this step.
- Choose R_C and R_E for a gain of -10V/V (at 10kHz) and a collector current of 1mA. What is the DC value of V_{CE} ?
- Derive the transfer function for V_{out}/V_{in} and plot the frequency response (magnitude and phase) in MATLAB/Python.
- Perform an AC simulation of the circuit in Ltspice. Export the frequency response data for comparison to the ideal response from Part c (plot them together). Provide reasons for any discrepancies between the two.

Problem 2: Emitter follower

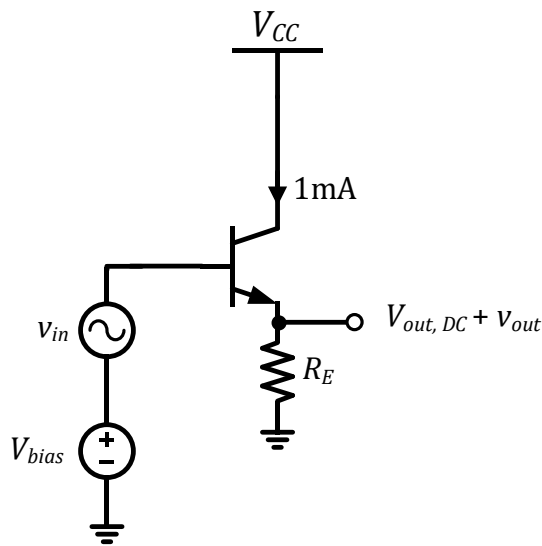


Figure 2a. Emitter follower

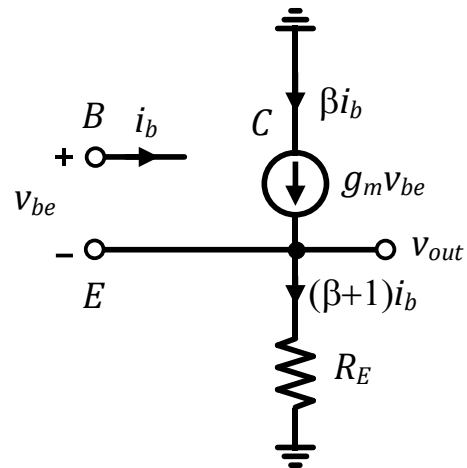


Figure 2b. Small-signal equivalent circuit

Use the Ebers-Moll model of the BJT and the figures to answer the following questions. $V_{CC} = 5\text{V}$, $I_S = 10^{-16}$, and $\beta = 100$. When determining input/output resistances, connect a test voltage to the small-signal circuit and determine the resistance as $r = v_{test}/i_{test}$. Use the *nnp* Ltspice component for your simulations.

- Design the biasing of the emitter follower (i.e. determine V_B and R_E) such that the collector current is 1mA and the DC level of V_{out} is 1V. You can do this by hand or use a MATLAB/Python script.
- Use the small-signal model (Fig. 2b) to determine the input resistance of the circuit.
- Use the small-signal model (Fig. 2b) to determine the output resistance of the circuit.
- Verify your design in Ltspice and include all relevant SPICE schematics and results in your submission.