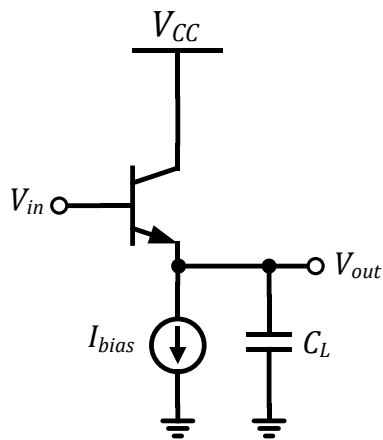


EE 538 Spring 2020
Analog Circuits for Sensor Systems
University of Washington Electrical & Computer Engineering

Instructor: Jason Silver
Practice Midterm

Please show your work.


Problem 1: Emitter-follower analysis



For the following, $V_{CC} = 5\text{V}$, $V_{IN} = 1\text{V}$, $I_{bias} = 1\text{mA}$, $C_L = 30\text{pF}$, and $I_S = 10^{-16}\text{A}$.

- Calculate the DC value of V_{out} . For this step, assume $V_A = \infty$.
- Calculate the small-signal DC gain (v_{out}/v_{in}) if $V_A = 100\text{V}$.
- Calculate the small-signal output resistance of the emitter follower if $V_A = 100\text{V}$.
- Calculate the transit frequency (f_T) of the emitter follower.
- Suppose we replace the BJT with a MOSFET with $V_{GS} - V_{TH} = 0.25\text{V}$ to construct a source follower. Ignoring r_o of the MOSFET, what is the new transit frequency?

Problem 2: Filter analysis and design

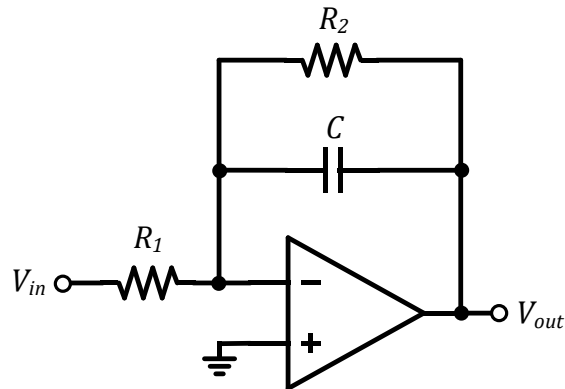

Assume the opamp has infinite gain and bandwidth, with input bias current $I_B = 1\text{nA}$.

- Ignoring bias current, derive an expression for the closed-loop transfer function of the filter.
- Design the filter (choose R_1 , R_2 , and C) to have a DC gain of 20dB and a 0.1% settling time of $10\mu\text{s}$.
- Still ignoring bias current, derive an expression for the closed-loop step response. Sketch the response for an input step of 0 to 1V and label all relevant times/voltages.
- Re-sketch the closed-loop step response, accounting for the effect of input bias current.
- Modify the design to reduce/eliminate the effect of the input bias current.

Problem 3. Opamp circuit design

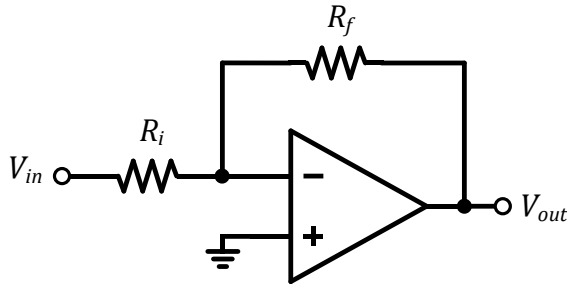


Figure 3a. Inverting amplifier

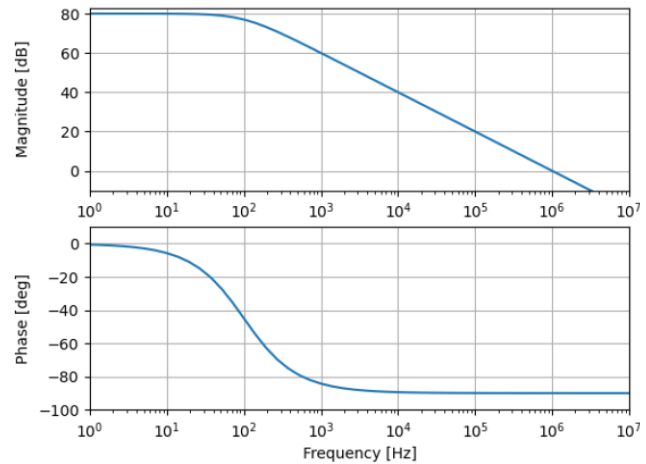


Figure 3b. Opamp open-loop frequency response

Assume ideal input/output resistances (R_{in} and R_o) for the opamp. Let $R_f = 10R_{in}$.

- Determine the gain and the 3dB frequency of the closed loop transfer function.
- Calculate the closed-loop gain error at DC and 100Hz.
- Suppose you want to use this amplifier to amplify the voltage of a sensor with an equivalent source resistance of $1\text{k}\Omega$. Determine the values of R_i and R_f to achieve a DC gain of 10V/V and less than 0.1% input attenuation due to loading (*you can ignore finite gain for this step*).
- Based on your answer to part c), is this a good choice of circuit for the application? How could it be improved?