

$$\begin{aligned} \text{- HPF} &\Rightarrow f_{3dB, HP} = 0.1 \text{ Hz} \\ \text{- LPF} &\Rightarrow f_{3dB, LP} = 100.5 \text{ KHz} \end{aligned}$$

a) Let's choose  $f_{3dB, HP}$  to be equal to 0.1 Hz  $\Rightarrow T_{HP} = \frac{1}{2\pi \times 0.1} = 1.59155$   
At  $f = 1 \text{ Hz}$

$$\left| \frac{V_o}{V_s} \right|_{dB} = 20 \log \sqrt{\frac{1}{1 + (\omega Z)^2}} = 20 \log \frac{(1/0.1)}{\sqrt{1 + (1/0.1)^2}} = -0.043 \text{ dB} < 0.1 \text{ dB (Meets spec)}$$

LPF needs to meet 20dB attenuation at 1MHz

$$\left| \frac{V_o}{V_s} \right|_{dB} = -20 \text{ dB} = 20 \log \frac{1}{\sqrt{1 + (\omega Z)^2}}$$

$$-1 = \log \frac{1}{\sqrt{1 + (2\pi \times 10^6 \times T_{LP})^2}} \Rightarrow \frac{\log \sqrt{1 + (2\pi \times 10^6 \times T_{LP})^2}}{1 + (2\pi \times 10^6 \times T_{LP})^2} = 1 \\ T_{LP} = \sqrt{10^2 - 1} \cdot \frac{1}{2\pi \times 10^6}$$

$$T_{LP} = 1.58357 \mu$$

$$f_{3dB, LP} = 100.5037815 \text{ KHz}$$

At  $f = 10 \text{ KHz}$ ,

$$\left| \frac{V_o}{V_s} \right|_{dB} = 20 \log \frac{1}{\sqrt{1 + (\omega Z)^2}} - 20 \log \frac{1}{\sqrt{1 + (2\pi \times 10^4 \times 1.58357 \mu)^2}} = -0.04 \text{ dB} < 0.1 \text{ dB (Meets spec)}$$

$$\text{Choose } f_{3dB, LP} = 100.5 \text{ KHz}$$

$$\& f_{3dB, HP} = 0.1 \text{ Hz}$$

b)  $R_S = 100 \Omega$ ,  $R_L = 10 \text{ M}\Omega$ ,  $R_1 = ?$ ,  $R_2 = ?$ ,  $C_1 = ?$  &  $C_2 = ?$

$$f_{3dB, HP} = \frac{1}{2\pi R_1 C_1} = 0.1$$

To minimize loading  $\Rightarrow R_1$  must be large compared to  $R_S$

$$\text{Choose } R_1 = 1000 R_S$$

$$R_1 = 100 \text{ k}\Omega$$

$$C_1 = 15.9155 \mu\text{F}$$

[ $0.1 \text{ dB} \Rightarrow 1\%$ . Lets target 0.1%]

$$f_{3dB, LP} = \frac{1}{2\pi R_2 C_2} = 100.5 \text{ KHz}$$

To minimize loading  $\Rightarrow R_L \gg 1000 R_2$

$$\text{Let } R_2 = R_L / 1000$$



$$R_2 = 10 \text{ k}\Omega$$

$$C_2 = 0.15836 \text{ nF}$$

$$R_2 = 10\text{ k}\Omega$$


$$C_2 = 0.15836\text{ nF}$$

c) LTspice Simulation & python

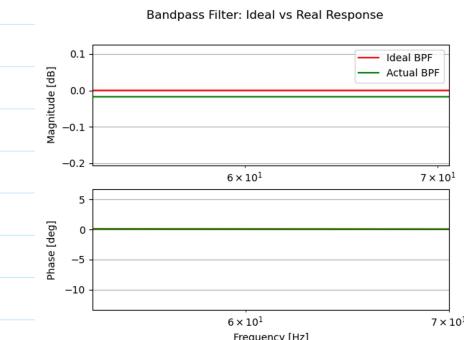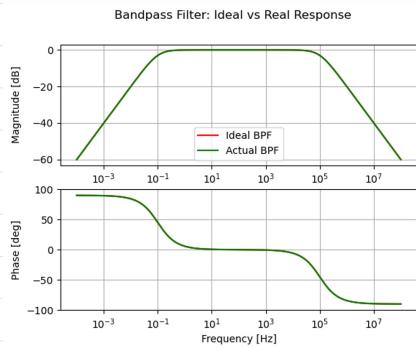

Zoomed in at  $f = 60\text{ Hz}$ .

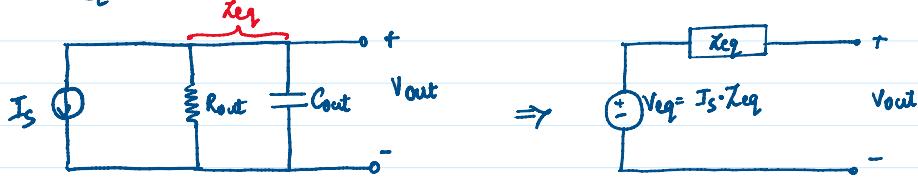② a)  $\frac{V_{out}}{I_s} = ? \quad X_L \rightarrow \infty \quad I_L \rightarrow 0$





$$\Rightarrow \frac{V_{eq}}{I_s} = Z_{eq} \quad V_{out}$$

$$Z_{eq} = Z_{out} = R_{out} \parallel C_{out} = \frac{R_{out} \frac{1}{sC_{out}}}{R_{out} + \frac{1}{sC_{out}}} = \frac{R_{out}}{sR_{out}C_{out} + 1}$$

$$\frac{V_{out}}{I_s} = \frac{I_s \cdot Z_{eq}}{I_s} = Z_{eq} = \frac{R_{out}}{sR_{out}C_{out} + 1} \quad \text{--- (1)}$$

$$\omega_p = \frac{1}{R_{out}C_{out}} \quad \text{--- (2)}$$

$$|Z_{eq}| \text{ at DC} = R_{out} \quad \text{--- (3)}$$

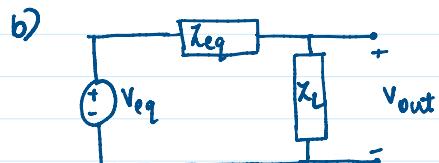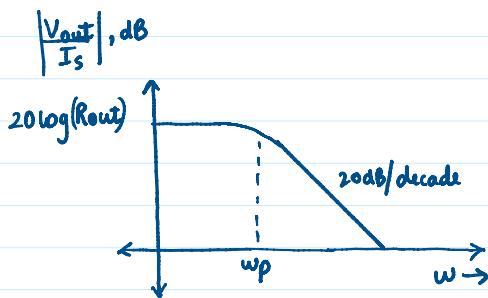

$$V_{eq} = -I_s Z_{eq} \quad \text{--- (4)}$$



$$V_{out} = \frac{X_L}{X_L + Z_{eq}} V_{eq} \Rightarrow \frac{V_{out}}{I_s} = -\frac{X_L \cdot Z_{eq}}{X_L + Z_{eq}}$$

$$= -X_L \parallel Z_{eq} \quad \text{--- (5)}$$

$$1) X_L = C_L \Rightarrow C_{eff} = C_{out} \parallel C_L = C_{out} + C_L$$

$$1) \chi_L = C_L \Rightarrow C_{\text{eff}} = C_{\text{out}} \parallel C_L = C_{\text{out}} + C_L$$

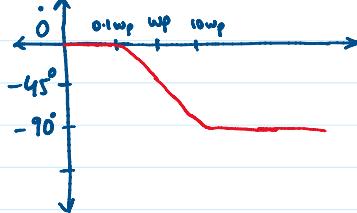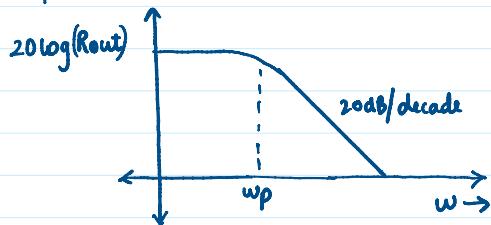
Pole frequency,  $w_p = \frac{1}{R_{\text{out}} C_{\text{eff}}} = \frac{1}{R_{\text{out}} (C_{\text{out}} + C_L)}$  — (6)



$$2) \chi_L = R_L \Rightarrow R_{\text{eff}} = R_{\text{out}} \parallel R_L = \frac{R_{\text{out}} R_L}{R_{\text{out}} + R_L}$$

Pole frequency,  $w_p = \frac{1}{C_{\text{out}} R_{\text{eff}}} = \frac{1}{C_{\text{out}} (R_{\text{out}} \parallel R_L)}$  — (7)


Also  $\left|\frac{V_{\text{out}}}{I_s}\right|$  at DC =  $R_{\text{out}} \parallel R_L$

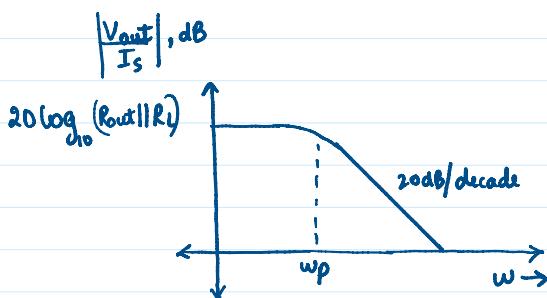

c) Transient response of  $V_{\text{out}}$   $I_s \rightarrow 0$  to  $I_{\text{max}}$  &  $\chi_L \rightarrow \infty$   
 for  $\chi_L \rightarrow \infty$ ,  $V_{\text{out}} = V_{\text{eq}}$   
 $V_{\text{out}} = -I_s R_{\text{eq}}$   
 $V_{\text{out}}(s) = -I_s \frac{R_{\text{out}}}{s R_{\text{out}} C_{\text{out}} + 1}$

Time domain,

$$V_{\text{out}}(t) = -I_s R_{\text{out}} \left( 1 - e^{-t/\tau} \right) \quad (8) \quad \left| \tau = R_{\text{out}} C_{\text{out}} \right.$$

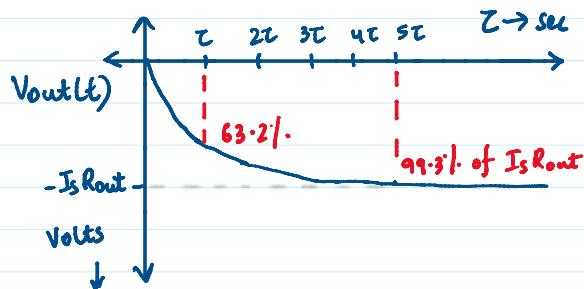

③

$$R = 100\Omega, C = 10\text{pF}$$

$$T = RC = \underline{\underline{1\text{ns}}}$$

a) for 0.1% settling precision.

$$T_{ON} \geq 6.9T$$

$$T_{CLK} = T_{ON} + T_{OFF} \geq 13.8T$$

$$f_{CLK} \leq \frac{1}{13.8T}$$


$$f_{CLK(max)} = \frac{1}{13.8 \times 10^{-9}} = \underline{\underline{72.4637 \text{MHz}}}$$

b)  $I_{avg} = \frac{\Delta q}{\Delta t}$


Charge delivered to capacitor  $Q = CV_{in}$

$$I_{avg} = \frac{CV_{in}}{\text{Simulation time}} = \frac{10\text{pF} \times 1V}{1.5\mu\text{s}} = 6.67\mu\text{s}. \quad (\text{Ideally the steady state average current is zero})$$

c)

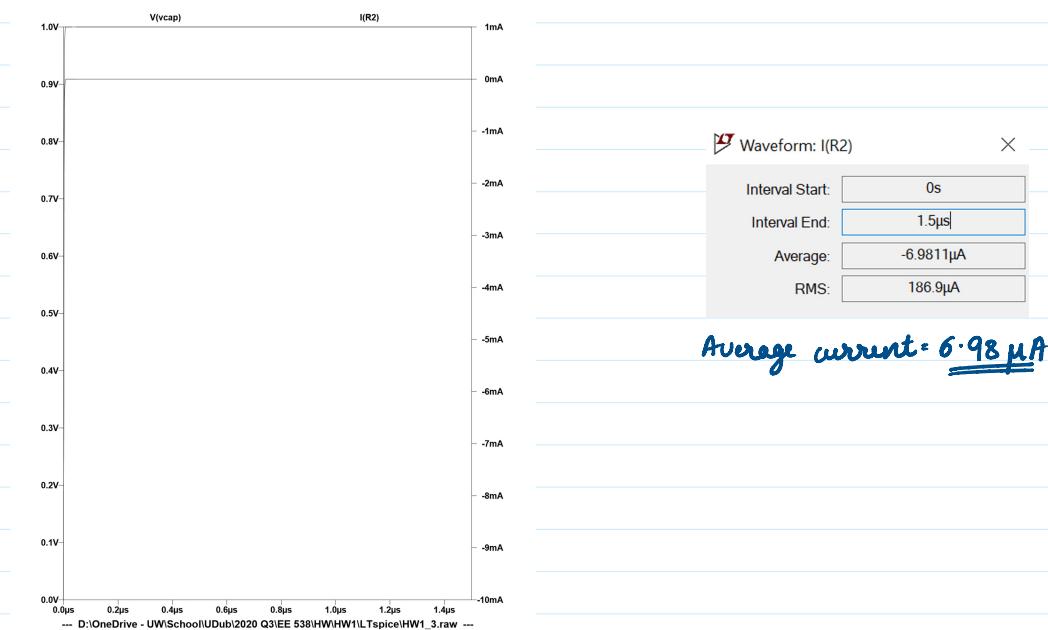


d)

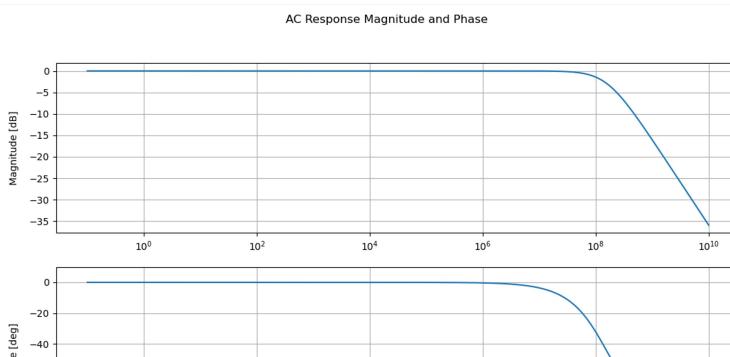

d)

AC Response Magnitude and Phase

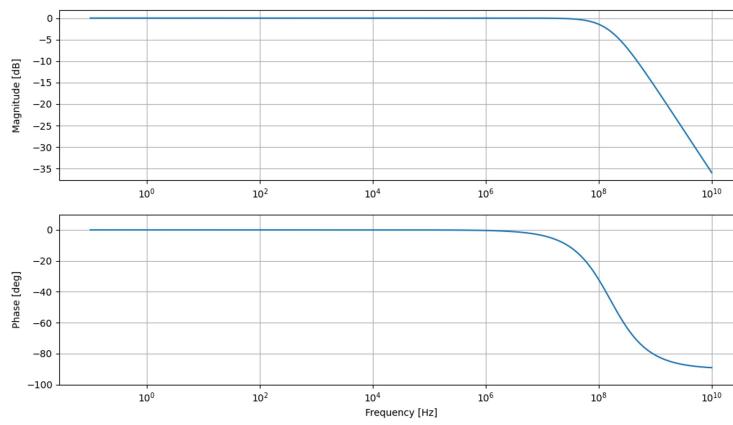

$$f_{3\text{dB}} = 159 \text{ MHz}$$

$$\tau = \frac{1}{2\pi f_{3\text{dB}}} = 1 \text{ ns}$$

$$\text{Settling time} = 6.9\tau = 6.9 \text{ ns}$$