

HW-6

① $R_f = 10 \text{ k}\Omega$, $R_i = 1 \text{ k}\Omega$, $f_T = 10 \text{ MHz}$, $e_n = 10 \text{ nV}/\sqrt{\text{Hz}}$, $i_n = 1 \text{ pA}/\sqrt{\text{Hz}}$

a) $e_{nR_i, \text{out}} = -\frac{R_f}{R_i} e_{nR_i} = -\frac{R_f}{R_i} \sqrt{4KT R_i} \frac{V}{\sqrt{\text{Hz}}}$

$e_{nR_f, \text{out}} = e_{nR_f} = \sqrt{4KT R_f} \frac{V}{\sqrt{\text{Hz}}}$

$e_{na, \text{out}} = \left(1 + \frac{R_f}{R_i}\right) e_n \frac{V}{\sqrt{\text{Hz}}}$

$e_{n, \text{out}} = \sqrt{e_{nR_i, \text{out}}^2 + e_{nR_f, \text{out}}^2 + e_{na, \text{out}}^2 + (R_f \cdot i_n)^2}$

$e_{n, \text{out}} = \sqrt{\frac{R_f^2}{R_i^2} 4KT R_i + 4KT R_f + \left(1 + \frac{R_f}{R_i}\right)^2 e_n^2 + R_f^2 \cdot i_n^2}$

$e_{n, \text{out}} = 118.36 \text{ nV}/\sqrt{\text{Hz}}$

$e_{n, \text{in}} = \frac{e_{n, \text{out}}}{A_{CL}} = \underline{\underline{11.8 \text{ nV}/\sqrt{\text{Hz}}}}$

b) $f_{ENB} = ?$

$\beta = \frac{R_i}{R_i + R_f} = \frac{1}{11}$

$f_{ENB} = \frac{f_T}{2} \beta = \underline{\underline{1.43 \text{ MHz}}}$

$V_{n, \text{out(rms)}} = \sqrt{e_{n, \text{out}}^2 f_{ENB}} = 141 \mu\text{V}$

$V_{n, \text{in(rms)}} = \frac{V_{n, \text{out(rms)}}}{A_{CL}} = \frac{141 \mu\text{V}}{10} = \underline{\underline{14.1 \mu\text{V}}}$

② ①

Datasheet

ADA 4898

$$e_n = 0.9 \text{ nV}/\sqrt{\text{Hz}} @ f = 1 \text{ KHz}$$

$$i_n = 2.4 \text{ pA}/\sqrt{\text{Hz}} @ f = 1 \text{ KHz}$$

$$\text{Current Noise density} = 10 \cdot \text{Voltage Noise} = R_S$$

$$R_S i_n = 10 \cdot e_n$$

$$R_S = \frac{9 \text{ nV}/\sqrt{\text{Hz}}}{2.4 \text{ pA}/\sqrt{\text{Hz}}} = 3750 \Omega$$

$$\Rightarrow e_{n,\text{out}} = i_n R_S \quad \text{--- ①}$$

From simulation $e_{n,\text{out}} = 11.04 \text{ nV}/\sqrt{\text{Hz}}$
from ①, $i_n = \underline{2.94 \text{ pA}/\sqrt{\text{Hz}}}$

The simulated value of input current noise density exceeds the expected value. This is most likely due to the frequency dependence of noise density

④ i) AD 8691 :

$$e_{n,\text{out}} = e_{na} = 0.8 \text{ nV}/\sqrt{\text{Hz}} @ f = 10 \text{ KHz}, \beta = 1, f_T = 1 \text{ MHz}$$

$$V_{n,\text{out}} = \sqrt{e_{n,\text{out}}^2 \times 10^6} = 8.0 \mu\text{V}$$

$$\text{Simulated Value} = 8.32 \mu\text{V}$$

ii) ADA 4898:

$$e_{n,\text{out}} = 0.9 \text{ nV}/\sqrt{\text{Hz}}$$

$$V_{n,\text{out}} = \sqrt{e_{n,\text{out}}^2 \times 10^6} = 0.9 \mu\text{V} = 900 \text{ nV}$$

$$\text{Simulated Value} = 919.86 \text{ nV}$$

The error is most likely from ignoring the '1/f' contribution

Problem 1)

c)

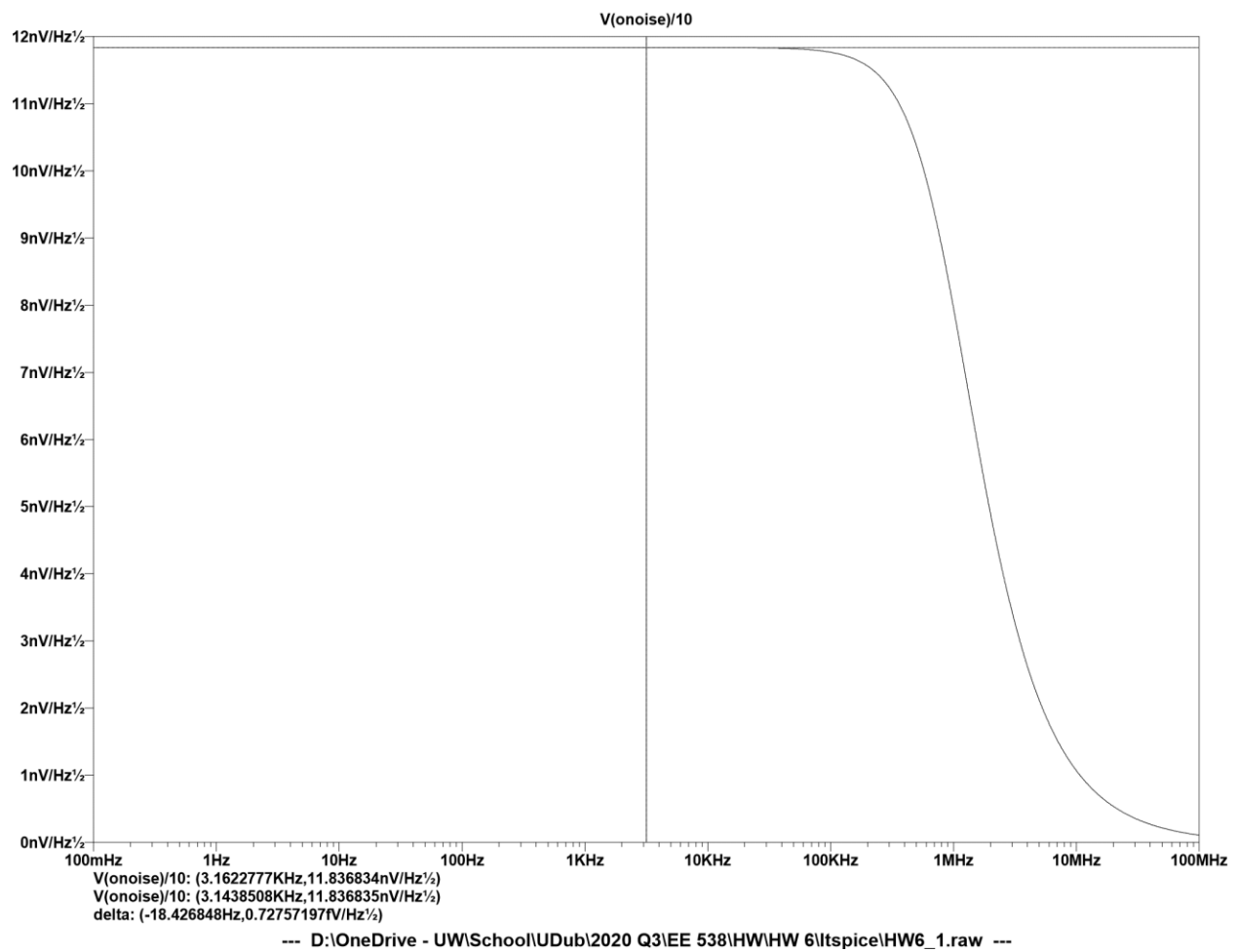


Fig 1. Input Referred Noise Voltage Density plot

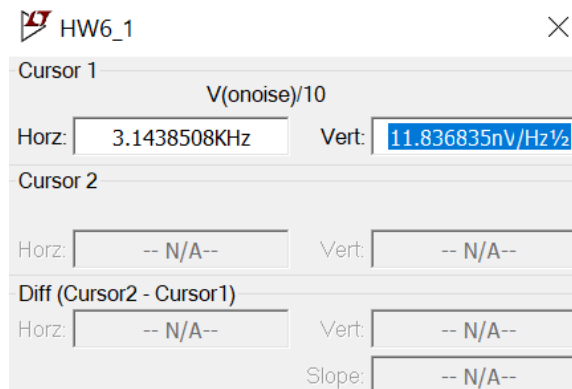


Fig 2. Input Referred Noise Voltage Density

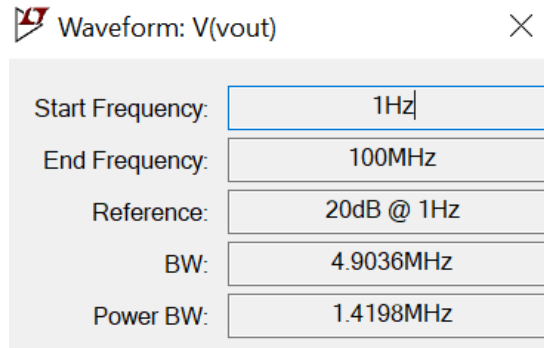


Fig 3. Equivalent Noise Bandwidth (F_{ENB})

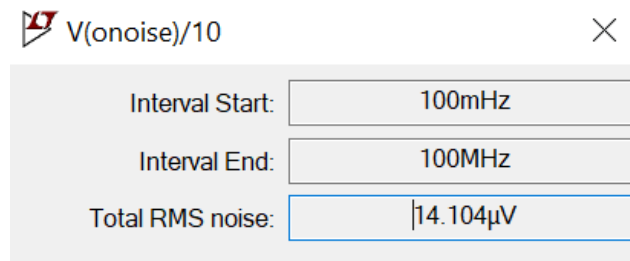


Fig 4. Input referred RMS noise voltage

Problem 2)

a)

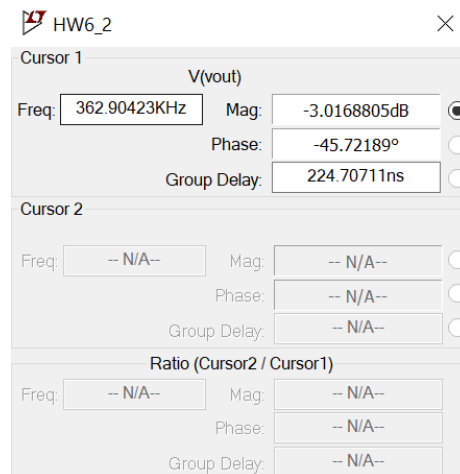


Fig 5. F_{3dB} frequency of AD8691

$$\text{Noise Bandwidth} = \pi/2 * f_{3dB} = 570 \text{ KHz}$$

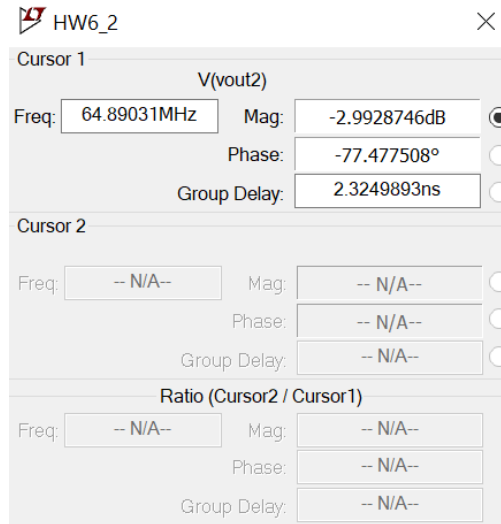


Fig 6. F_{3dB} frequency of ADA4898

$$\text{Noise Bandwidth} = \pi/2 * f_{3dB} = 102 \text{ MHz}$$

b)

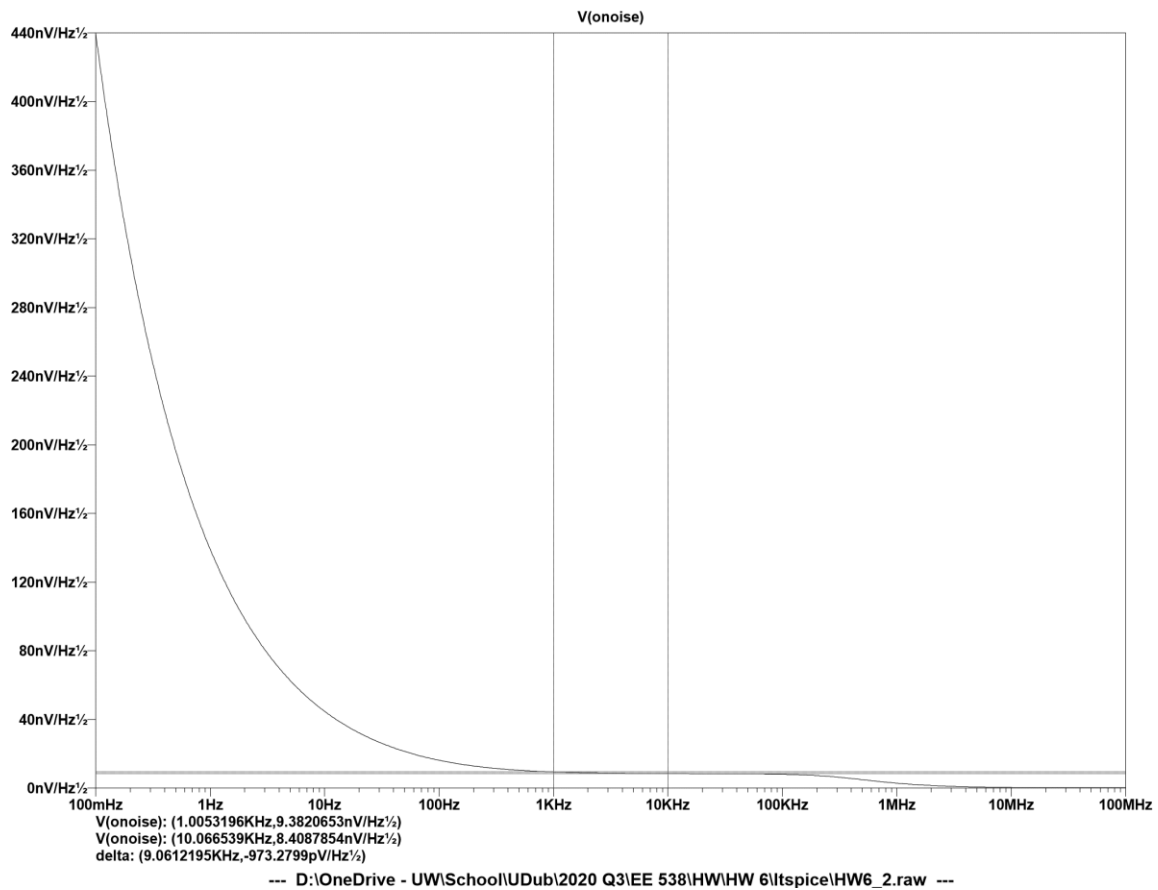


Fig 7. Noise voltage density of AD8691

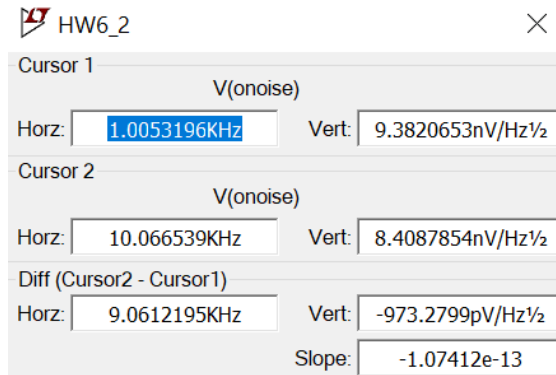


Fig 8. Noise voltage density of AD8691 at 1KHz and 10KHz

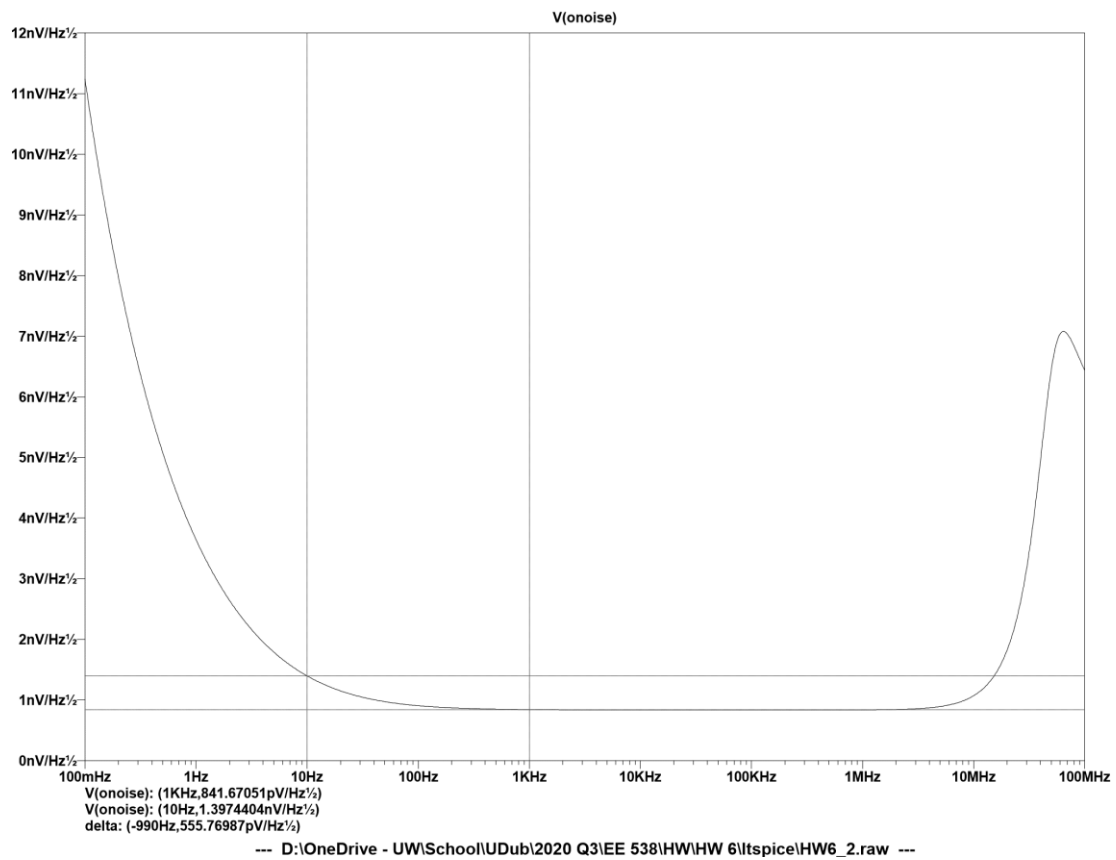


Fig 9. Noise voltage density of ADA4898


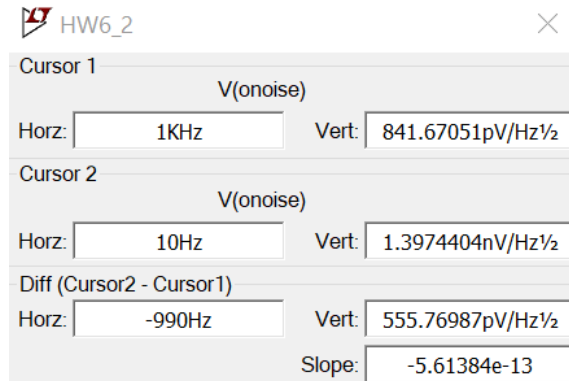


Fig 10. Noise voltage density of ADA4898 at 10Hz and 1KHz

c)

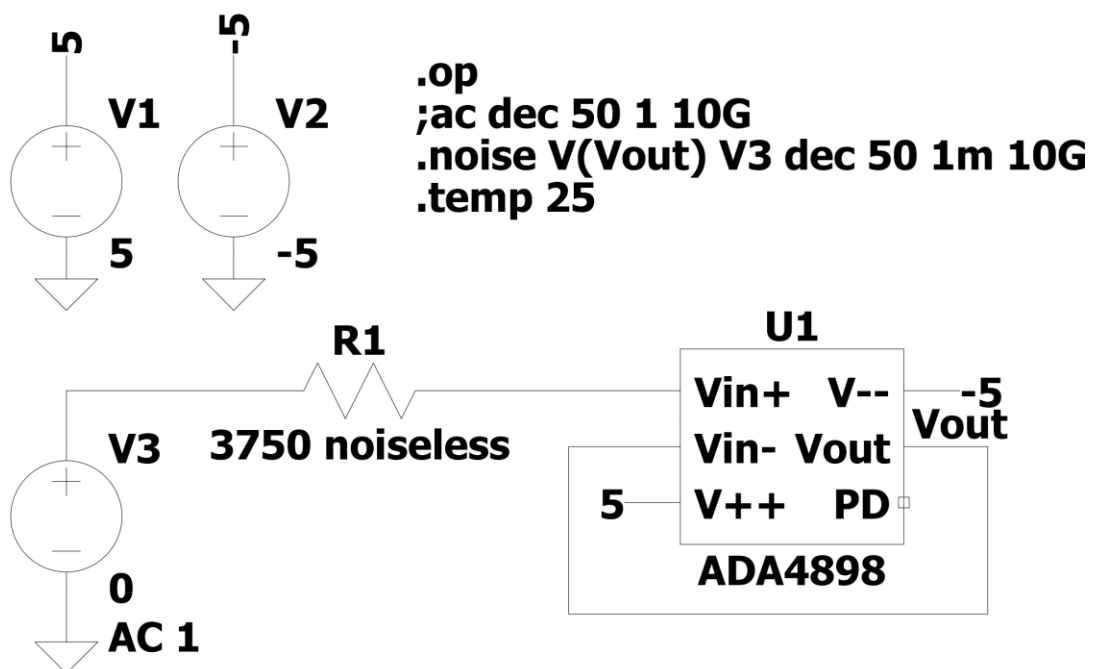

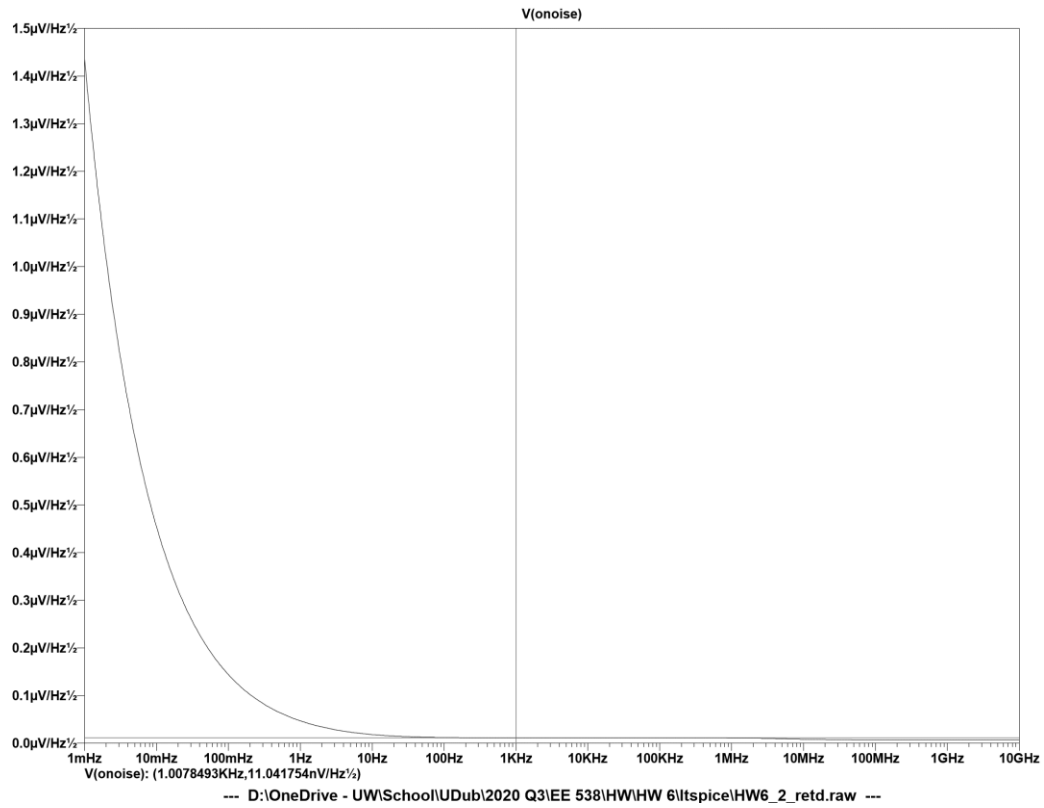


Fig 12. Noise voltage density of ADA4898

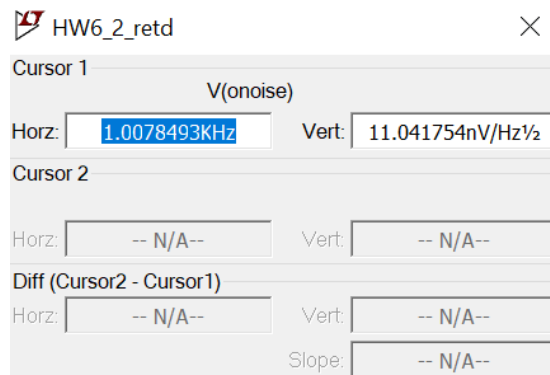


Fig 13. Noise voltage density of ADA4898 at 1KHz

d)

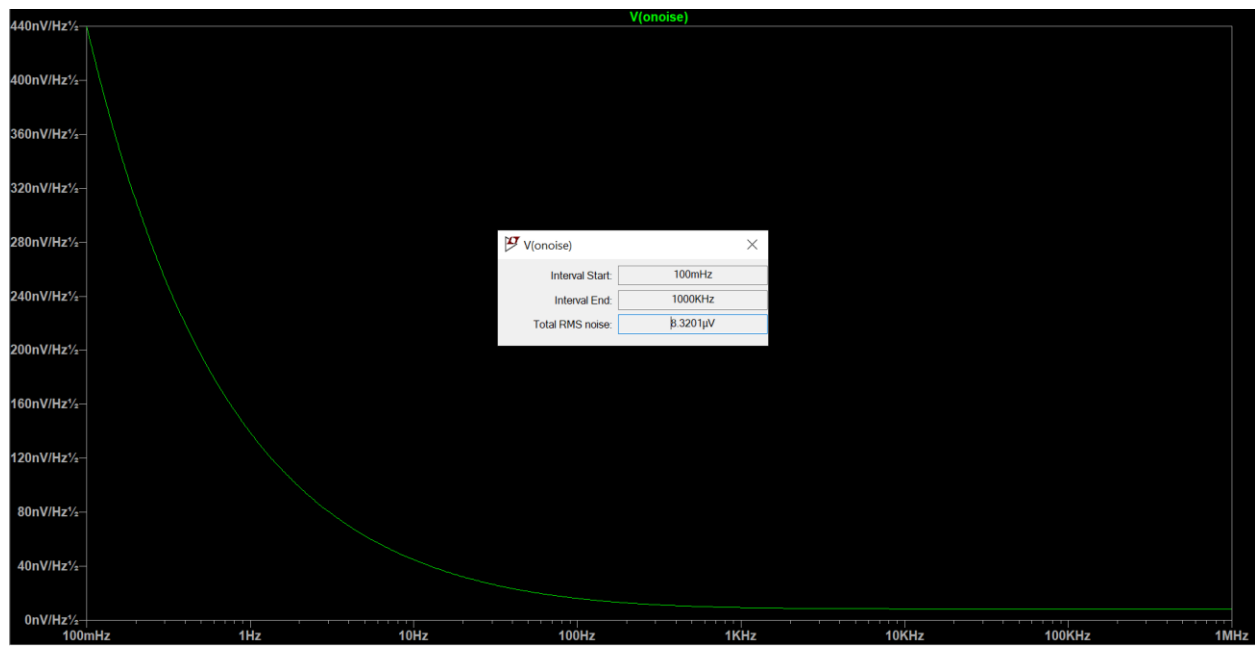


Fig 14. RMS output noise of AD8691

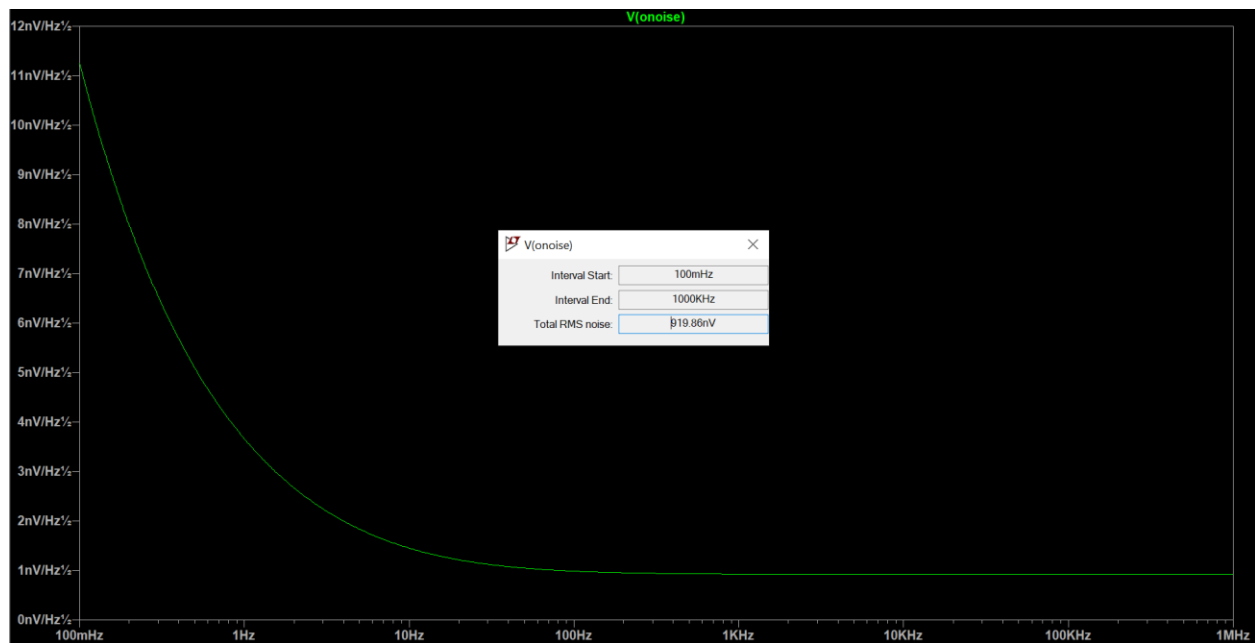


Fig 15. RMS output noise of ADA4898