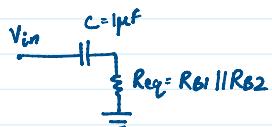


- (i) $V_{CC} = 5V, C = 1\mu F, \beta = 100$
 (a) $V_B = 1V, f_{3dB} = 10Hz$



$$f_{3dB} = \frac{1}{2\pi R_{eq} C}$$

$$R_{eq} = \frac{1}{2\pi \times 10 \times 1\mu F} = 15.915 \text{ k}\Omega = \frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}} \quad \textcircled{1}$$

$$V_B = V_{CC} \left(\frac{R_{B2}}{R_{B2} + R_{B1}} \right)$$

$$\Rightarrow \frac{R_{B2}}{R_{B2} + R_{B1}} = \frac{1}{5} \quad \textcircled{2}$$

Choose $R_{B1} = 80\text{k}\Omega, R_{B2} = 20\text{k}\Omega$

$$\Rightarrow R_{eq} = 16\text{k}\Omega \Rightarrow f_{3dB} < 10\text{Hz}$$

- (b) For Simplified model $V_{BE} = 0.6V, I_c = 1mA$

$$I_E = I_C + \frac{I_C}{\beta} = I_C \left(1 + \frac{1}{\beta} \right)$$

$$I_E = 1m \left(1 + \frac{1}{100} \right)$$

$$I_E = 1.01mA$$

$$V_E = V_B - V_{BE} = 1 - 0.6V = 0.4V$$

$$R_E = \frac{V_E}{I_E} = \frac{0.4}{1.01m} = 396\Omega$$



$$a_{V_V} = -\frac{R_C}{R_E} = -10V/V \Rightarrow R_C = 3.96\text{k}\Omega$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$

$$= 5 - 3.96 - 1.01(3.96)$$

$$V_{CE} = 0.64V$$

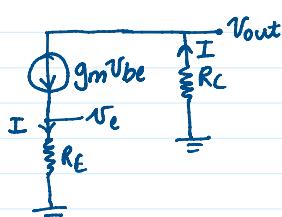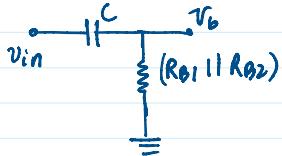(c) $\frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_B} \cdot \frac{V_B}{V_{in}}$




$$\frac{V_B}{V_{in}} = \frac{(R_{B1} || R_{B2})}{(R_{B1} || R_{B2}) + (\frac{1}{sC})}$$

$$\frac{V_B}{V_{in}} = \frac{j\omega C (R_{B1} || R_{B2})}{1 + j\omega C (R_{B1} || R_{B2})} \quad \textcircled{1}$$

$$I = -\frac{V_{out}}{R_C} = \frac{V_E}{R_E}$$

$$V_E = -V_{out} \frac{R_E}{R_C} \quad \textcircled{2}$$

Simplified Model

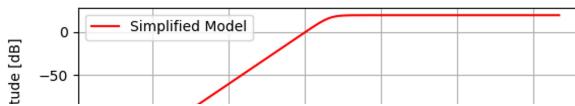

$$g_m V_{be} = -\frac{V_{out}}{R_C}$$

$$g_m (V_B + V_{out} \frac{R_E}{R_C}) = -\frac{V_{out}}{R_C}$$


$$g_m v_{be} = -\frac{v_{out}}{R_C}$$

$$g_m (V_b + V_{out} \frac{R_E}{R_C}) = -\frac{V_{out}}{R_C}$$

$$g_m V_b = V_{out} \left[g_m \frac{R_E}{R_C} - \frac{1}{R_C} \right]$$

$$\frac{V_{out}}{V_b} = -\frac{1}{\frac{R_E}{R_C} + \frac{1}{R_C g_m}} \Rightarrow \frac{V_{out}}{V_b} = -\frac{R_C}{\frac{1}{g_m} + R_E} \quad \text{--- (3)}$$

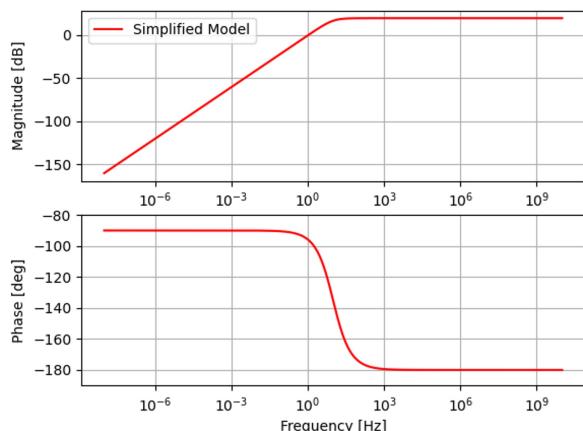
$$\frac{V_{out}}{V_{in}} = -j\omega C \left(R_{B1} \parallel R_{B2} \right) \cdot \frac{R_C}{1 + j\omega C \left(R_{B1} \parallel R_{B2} \right) \left(\frac{1}{g_m} + R_E \right)} \quad \text{--- (4)}$$



④ Simplified Model appears to have a higher gain & lower cut off frequency

One of the reasons is due to the presence of finite input resistance at the base of the BJT. Also the Base emitter junction is assumed to be a constant (0.6V) which is not the case for a real BJT. These two factors have introduced error into our estimations.

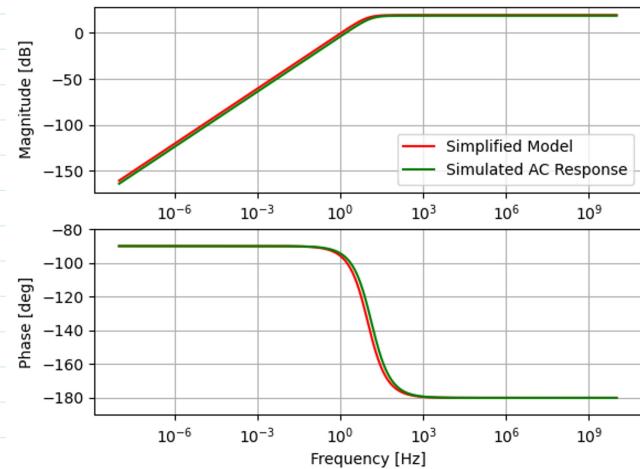Simplified Model vs Simulated AC Response



$$② V_{CC} = 5V, I_S = 10^{-16}, \beta = 100$$

$$a) V_{in} = ? \quad R_E = ? \quad I_C = 1mA \quad V_{out} = 1V$$

$$I_E = I_C \left(1 + \frac{1}{\beta} \right)$$


$$I_E = 1m \left(1 + \frac{1}{100} \right) \Rightarrow I_E = \underline{1.01mA}$$

$$R_E = \frac{V_{out}}{I_E} = \frac{1}{1.01m} = \underline{990.1\Omega}$$

$$V_{BE} = V_T \ln \frac{I_C}{I_S} = 25.85m \cdot \ln \frac{10^{-3}}{10^{-16}} = \underline{0.4738V}$$

$$V_{in} = V_{BE} + V_{out} = 0.4738 + 1 = \underline{1.4738V}$$

⑤

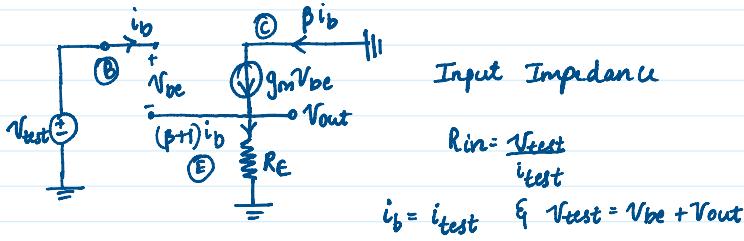

Input Impedance

$$R_{in} = \frac{V_{test}}{i_{test}}$$

$$i_b = i_{test} \quad \& \quad V_{test} = V_{be} + V_{out}$$


$$a) V_{be} = B i_L$$

$$\stackrel{+}{=} i_b = i_{test} \quad \text{if } V_{test} = V_{be} + V_{out}$$

$$g_m V_{be} = \beta i_b$$

$$\begin{aligned} g_m (V_{test} - V_{out}) &= \beta i_{test} \quad \text{if } V_{out} = (\beta+1) i_b R_E \\ g_m (V_{test} - (\beta+1) i_b R_E) &= \beta i_{test} \\ g_m V_{test} &= \beta i_{test} + (\beta+1) i_{test} R_E g_m \end{aligned}$$
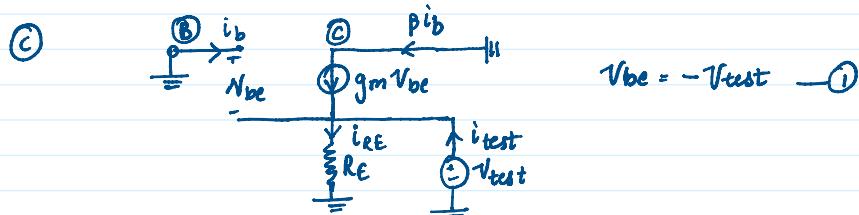
$$R_{in} = \frac{V_{test}}{i_{test}} = \frac{\beta}{g_m} + (\beta+1) R_E = 100 (25.85) + (101)(990 \cdot 1) = 102.585 \text{ k}\Omega$$



$$g_m V_{be} = \beta i_b$$

$$\frac{V_{test}}{R_E} = i_{RE}$$

$$-g_m V_{test} = \beta i_b$$

$$\frac{V_{test}}{R_E} = (\beta+1) i_b + i_{test}$$

$$\Rightarrow i_b = -\frac{g_m V_{test}}{\beta} \quad \text{--- (1)}$$

$$\frac{V_{test}}{R_E} = (\beta+1) \left(-\frac{g_m V_{test}}{\beta} \right) + i_{test}$$

$$V_{test} \left[\frac{1}{R_E} + \left(\frac{\beta+1}{\beta} \right) g_m \right] = i_{test}$$

$$R_o = \frac{V_{test}}{i_{test}} = \frac{1}{\frac{1}{R_E} + g_m}$$

$$\Rightarrow R_o = R_E \parallel \frac{1}{g_m} = \frac{990 \cdot 1 \times 25.85}{990 \cdot 1 + 25.85} = 25.192 \text{ }\Omega$$

$$\frac{\beta+1}{\beta} = 1 + \frac{1}{\beta} \approx 1$$

(d) 1. DC Simulation results


--- Operating Point ---		
V(vout) :	0.999579	voltage
V(vc) :	5	voltage
V(vb) :	1.7738	voltage
Ic(Q1) :	0.000999583	device_current
Ib(Q1) :	9.99582e-06	device_current
Ie(Q1) :	-0.00100958	device_current
I(I1) :	0	device_current
I(R4) :	0.00100957	device_current
I(V2) :	-9.99578e-06	device_current
I(V1) :	-0.000999579	device_current

Simulation Result

$$I_C = 0.999 \text{ mA} \quad (0.1\% \text{ error})$$


$$V_{out} = 0.999 \text{ V} \quad (0.1\% \text{ error})$$

2. Input Resistance

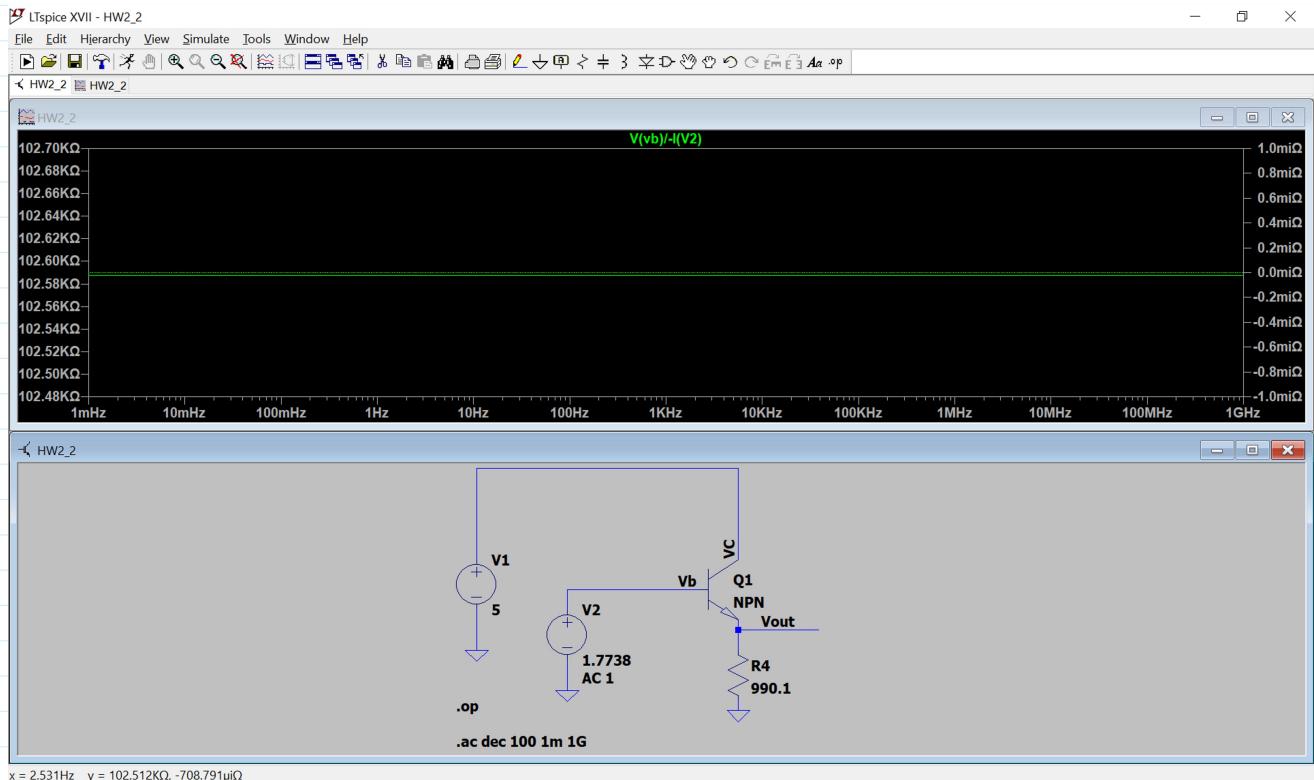

$$\text{Input resistance} = 102.512\text{K}\Omega \quad (\text{error} = \frac{102.585 - 102.512}{102.585} \cdot 100\% = 0.07\%)$$

3. Output resistance

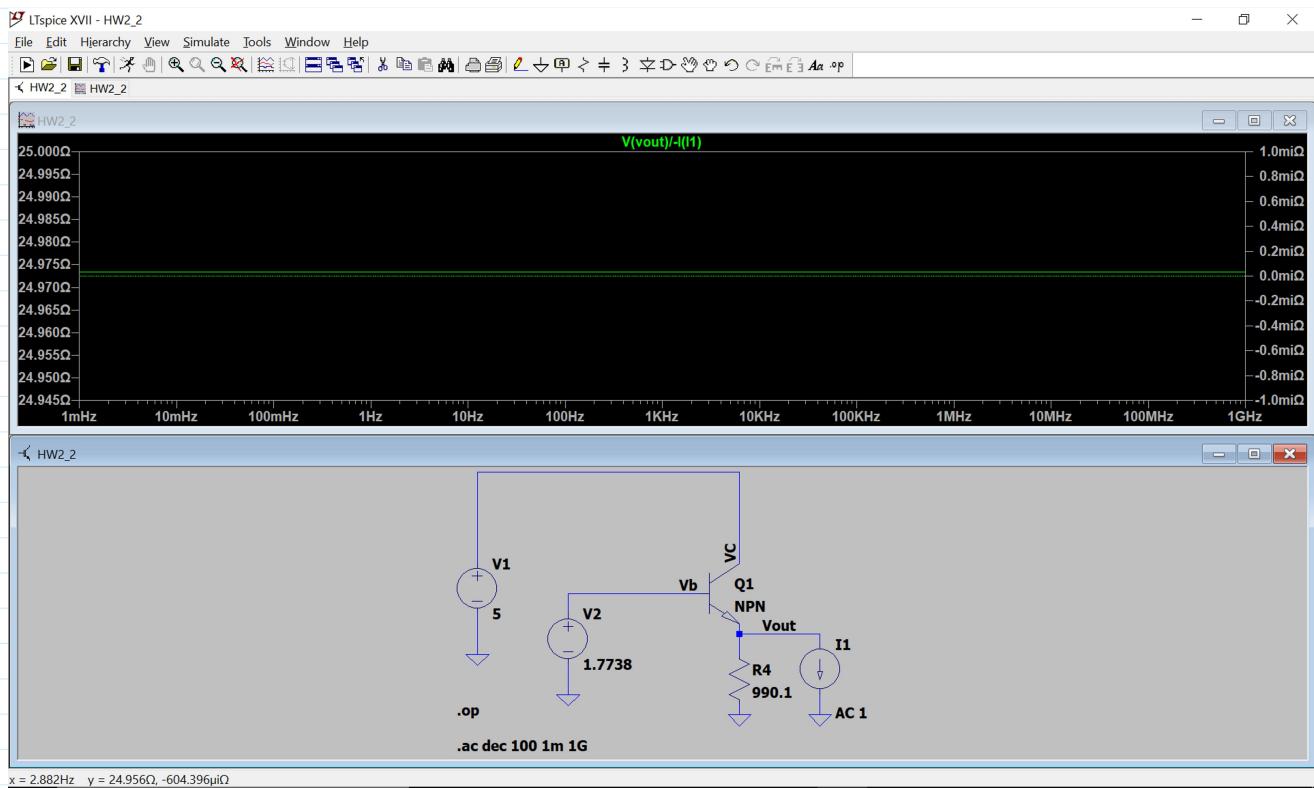

$$\text{output resistance} = 24.956\Omega \quad (\text{error} = \frac{25.192 - 24.956}{25.192} \times 100\% = 0.93\%)$$