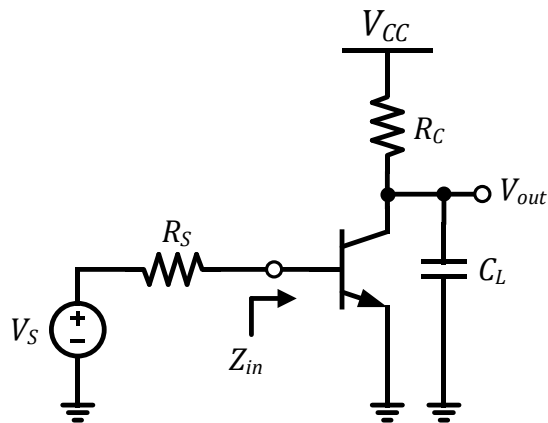


**EE 538 Spring 2020**  
**Analog Circuits for Sensor Systems**  
**University of Washington Electrical & Computer Engineering**

**Instructor: Jason Silver**  
**Midterm**

*Please show your work.*


**Problem 1: Common-emitter amplifier**



For the following,  $V_{CC} = 5\text{V}$ ,  $V_S = 1\text{V}$ ,  $R_S = 1\text{k}\Omega$ ,  $I_{bias} = 100\mu\text{A}$ ,  $R_C = 10\text{k}\Omega$ ,  $C_L = 10\text{pF}$ ,  $\beta = 100$ ,  $V_A = 100\text{V}$ ,  $V_T = 25\text{mV}$ , and  $I_S = 10^{-16}\text{A}$ .

- (10 points) Calculate the input impedance of the amplifier,  $Z_{in}$ . *Note: This does not include  $R_S$ .*
- (10 points) Find an expression for the transfer function,  $V_{out}/V_S$ . Be sure to account for attenuation due to  $Z_{in}$ .
- (10 points) Calculate the DC gain and transit frequency  $f_T$ .

## Problem 2: Opamp nonidealities

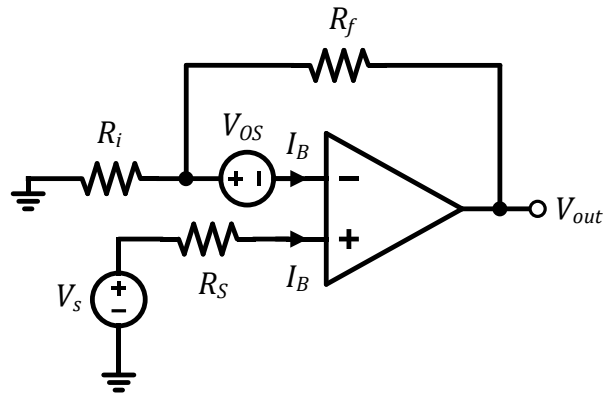

Assume the opamp has infinite gain and bandwidth.  $V_{OS} = 1\text{mV}$ , and  $I_B = -1\text{nA}$ .  $R_f = 10R_i$ .

- (15 points) Determine an expression for the output offset voltage, including the contributions from both  $V_{OS}$  and  $I_B$ .
- (10 points) Assuming  $R_S = 0$ , calculate values for  $R_i$  and  $R_f$  that result in zero output offset.
- (10 points) Assuming  $R_S = 1\text{k}$  and  $V_{OS} = 0$ , calculate values for  $R_i$  and  $R_f$  that result in zero output offset.

### Problem 3. Opamp AC and transient analysis

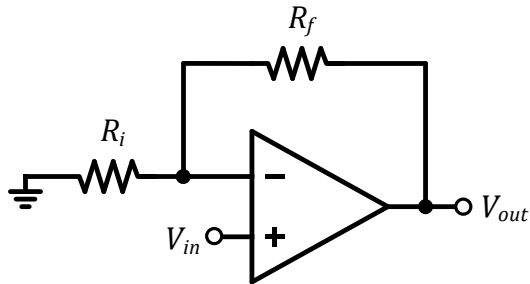


Figure 3a. Non-inverting amplifier

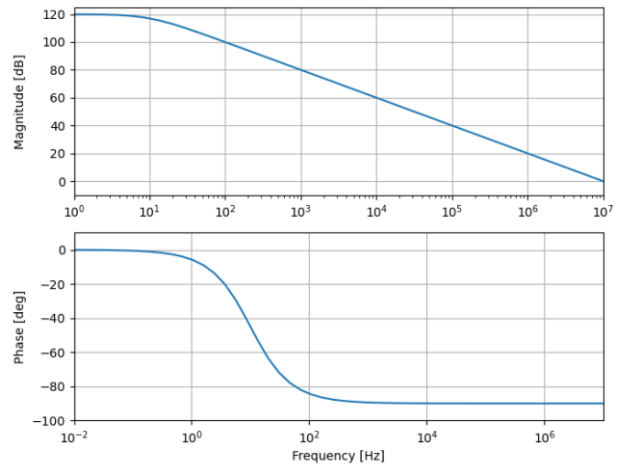


Figure 3b. Opamp open-loop frequency response

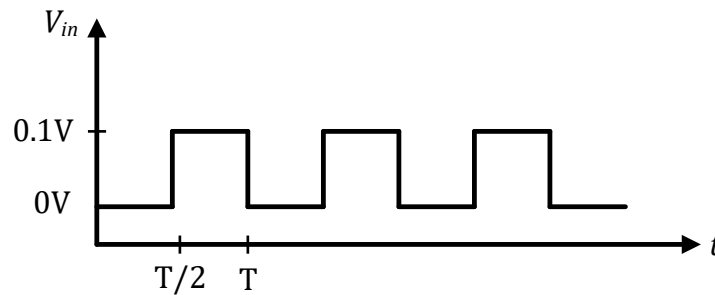


Figure 3. Input waveform for c) and d)

Assume ideal input/output resistances ( $R_{in}$  and  $R_o$ ) for the opamp. Let  $R_f = 10R_{in}$ .

- (10 points) Determine the DC gain and the 3dB frequency of the closed loop transfer function ( $V_{out}/V_{in}$ ).
- (7.5 points) Provide an expression for the transient response of the amplifier for a voltage step input of 0 to 100mV. Sketch the response and label all relevant times/voltages.
- (10 points) Assume the amplifier is driven by the input waveform shown in Fig 3c. Determine the minimum period  $T$  for which 0.1% settling is achieved during each half-period (integer multiples of  $T/2$ ). Sketch the output waveform.
- (7.5 points) Calculate the total worst-case error in the output voltage (at the end of each half-period) if the resistors have a tolerance of 0.1%.