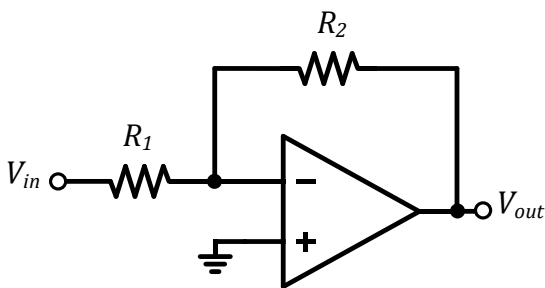


EE 538 Spring 2020  
Analog Circuits for Sensor Systems  
University of Washington Electrical & Computer Engineering


Instructor: Jason Silver  
Homework #4 (40 points)  
Due Saturday, May 2, Submit on Canvas

*Please show your work.*

**Problem 1: DC analysis of inverting and non-inverting amplifiers**



**Figure 1a. Inverting amplifier**

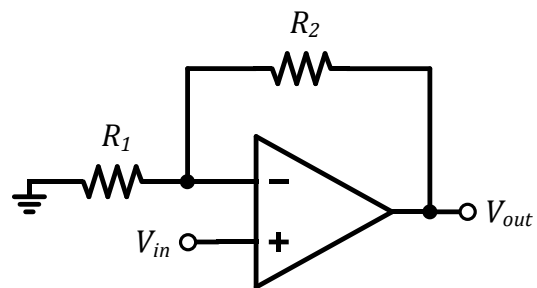

**Figure 1b. Non-inverting amplifier**

For the two amplifiers shown above, the opamp has open-loop DC gain  $A_0$ , input resistance  $R_{in}$ , and output resistance  $R_{out}$ . For the Ltpspice parts, use the UniversalOpamp2 (SpiceModel level.1), with  $R_1 = 1\text{k}\Omega$  and  $R_2 = 10\text{k}\Omega$ . The default open-loop output resistance for the opamp model is  $0.1\Omega$ . You can use the 'DC Transfer' analysis.

- a) (5 points) For the inverting and non-inverting amplifiers shown in Fig 1a and 1b, determine *expressions* for each of the following assuming  $A_0 \rightarrow \infty$  (infinite open-loop gain). Provide comments on how each closed-loop parameter compares to its open-loop counterpart.
  1. Closed-loop gain ( $V_{out}/V_{in}$ ).
  2. Closed-loop output resistance.
  3. Closed-loop input resistance.
- b) (5 points) Repeat Part a assuming  $A_0$  is finite. Try to develop some intuition regarding how each parameter depends on  $A_0$  and the feedback factor  $\beta$ . Check your answer by setting  $A_0 \rightarrow \infty$  and comparing to your answer in Part a.
- c) (2.5 points) Assuming the opamp has a voltage offset  $v_{OS}$ , what is the resulting output offset for each structure? Assume  $A_0 \rightarrow \infty$ . Check your answer in Ltpspice.
- d) (2.5 points) Assuming the opamp has input bias current  $I_B$ , what is the resulting output offset for each structure? Assume  $A_0 \rightarrow \infty$ .

## Problem 2: Opamp circuit transient response

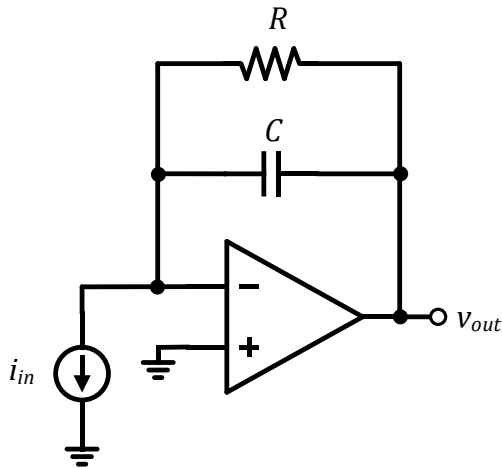


Figure 2a. Current-input integrator

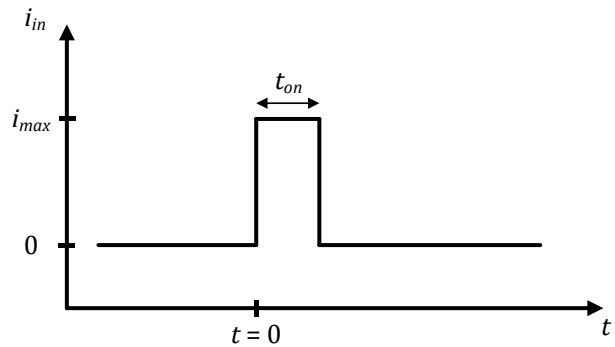


Figure 2b. Input current pulse

For the following, assume ideal opamp behavior.

- (2.5 points) Determine an expression for the transfer function  $v_{out}/i_{in}$ .
- (5 points) Determine an expression for the transient response of the circuit. What is the value of  $v_{out}$  (in terms of  $R$ ,  $C$ ,  $i_{max}$ , and  $t_{on}$ ) at time  $t = t_{on}$ ?

**Bonus (2 points):** Design the circuit (i.e. determine  $R$  and  $C$ ) to function as an integrator, such that  $v_{out}(t_{on}) = i_{max}/C$  with less than 0.1% error. Use  $i_{max} = 10\mu\text{A}$  and ensure  $v_{out}$  doesn't exceed a bipolar supply voltage of  $\pm 2.5\text{V}$ . Verify your design in Ltspice.

### Problem 3. Difference amplifier

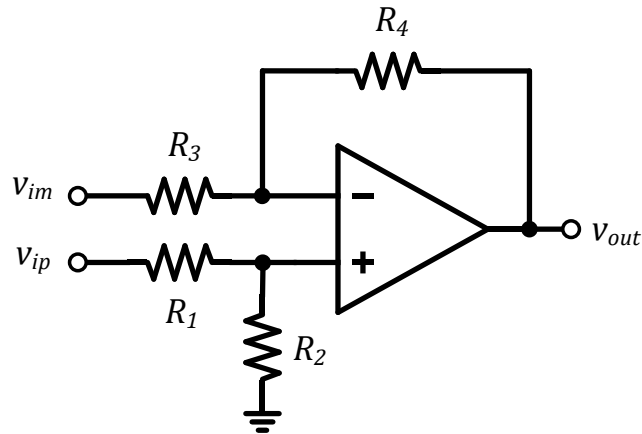


Figure 3. Difference amplifier

For the following, the opamp has a DC gain ( $A_0$ ) of 100 dB and a unity-gain bandwidth ( $f_T$ ) of 10MHz but is otherwise ideal ( $R_{in} = \infty$  and  $R_{out} = 0$ ).  $R_1 = R_2 = R_3 = R_4 = 10\text{k}\Omega$ .

- (2.5 points) Sketch the Bode magnitude and use the graph to approximate the 3dB bandwidth. Sketch the Bode phase plot.
- (5 points) Calculate the DC gain and 3dB bandwidth of the closed-loop transfer function  $v_{out}/(v_{ip} - v_{im})$ . Sketch the Bode magnitude and phase of the closed-loop transfer function.
- (5 points) What is the resistance “looking into” each input ( $v_{im}$  and  $v_{ip}$ )?
- (5 points) Check your answers to Parts b and c in Ltspice using the Analog Devices opamp model for the AD8691.